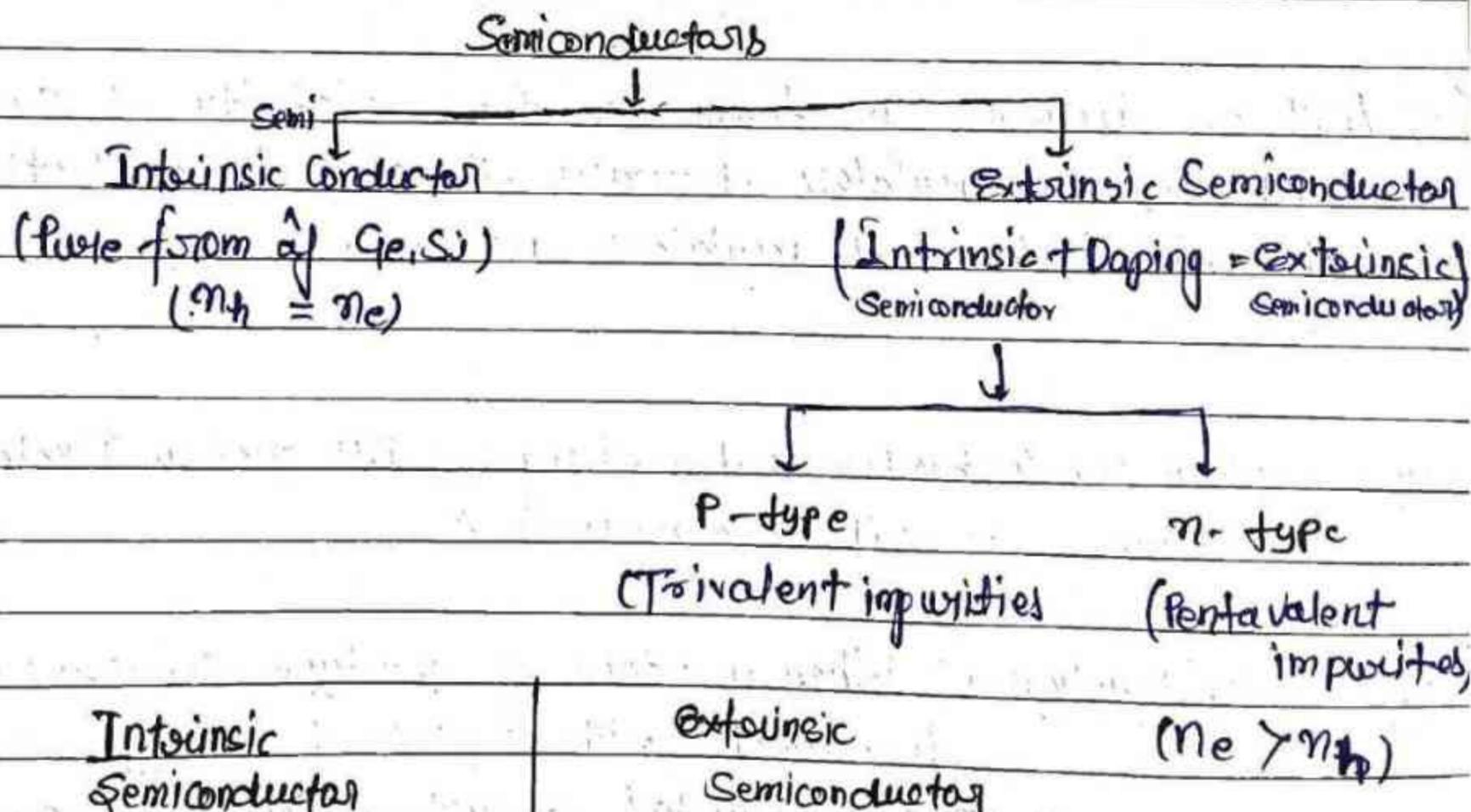


Unit - 01Semiconductor Diode & its applications.

⇒ Semiconductors are materials which have electrical conductivity between the conductors and insulators. Semiconductors are classified as:

- Intrinsic Semiconductor.
- Extrinsic Semiconductor.



Intrinsic Semiconductor	Extrinsic Semiconductor
① Pure form	Impure form
② Number of holes and number of electrons are equal	② Number of holes and number of electrons are not equal
③ Low conductivity	③ High conductivity.

Que → What do you mean by doping and why it is required?

Ans → Doping is the process of adding impurities to the intrinsic semiconductor to change their properties. Doping is required to control conductivity.


* Effect of temperature on conductors, semiconductor and insulator:-

① With an increase in temperature the resistivity of conductors increases. therefore the conductivity of conductors decreases.

② With an increase in temperature the resistivity of semiconductors and insulators decreases. therefore the conductivity of semiconductor and insulators increases.

Que → Explain the construction and working of P.N. junction Diode. Also draw its V.I. characteristics.

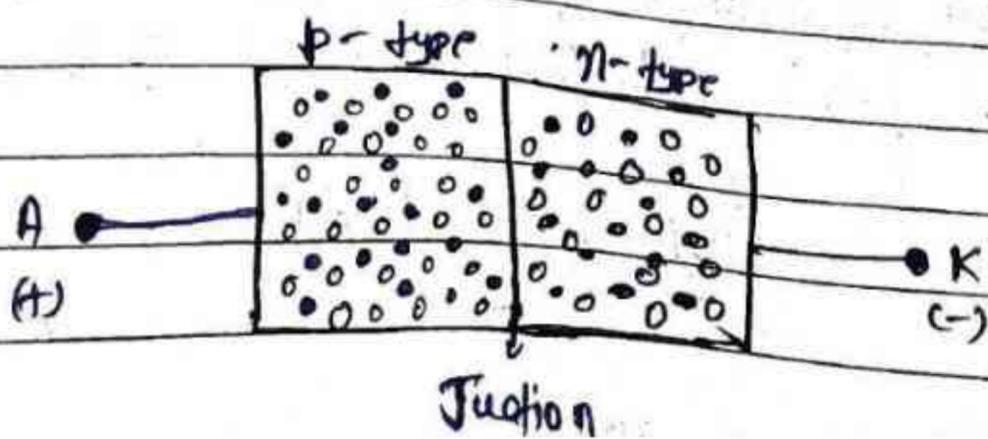Ans → Construction → When a piece of p-type semiconductor is joined with a piece of n-type semiconductor such that the crystal structure remains continuous at the boundary. then a junction is formed and the device so formed is known as p-n junction diode.



By the Diffusion Process (i.e. the charge will move from their higher density towards their lower density) a region becomes created where no mobile charge ions are present is known as Depletion region or Depletion layer and it acts as Depletion barrier which opposes the flow of holes from p-side to n-side and the flow of electrons from n-side to p-side.


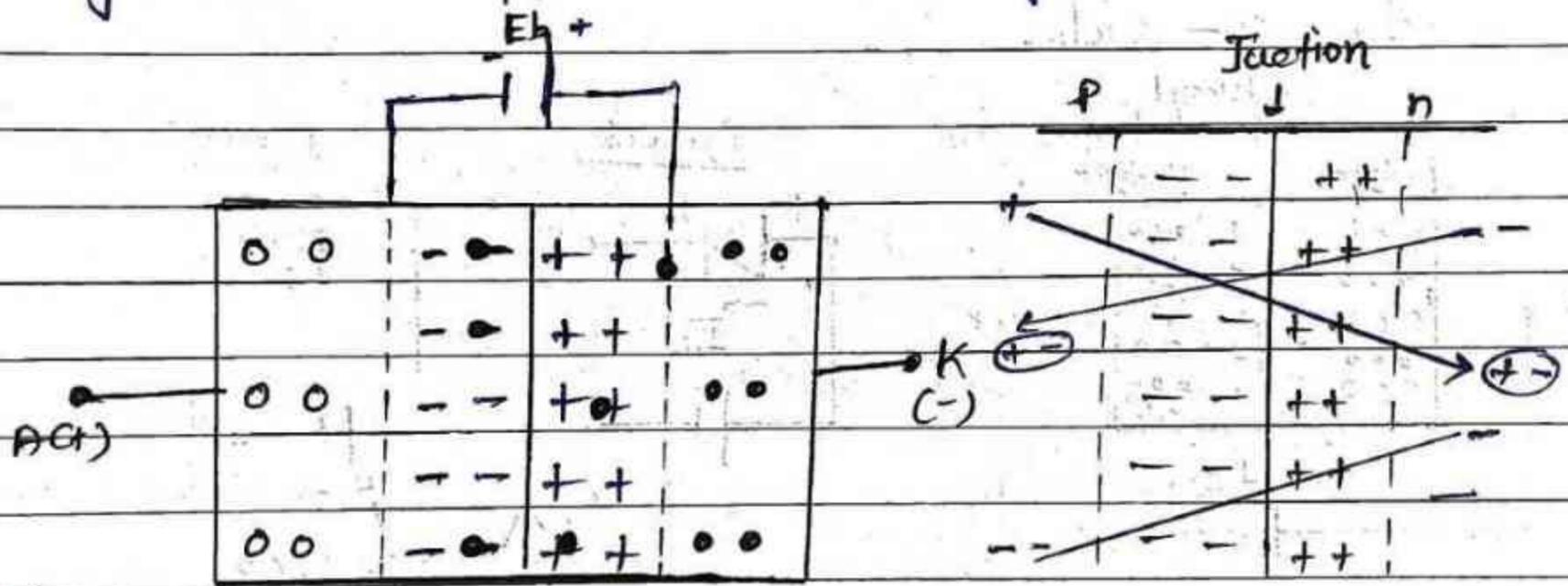


Fig. → Diffusion Process.

Depletion region

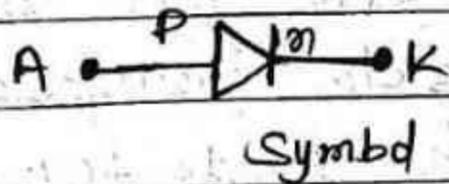


* Working :-

Case - I :- No Bias Condition (i.e. $V_D = 0V$) :-

Under no bias condition, no external voltage is applied to the anode and cathode terminals.

Case-II \rightarrow Forward bias condition (ie. $V_D > 0V$)

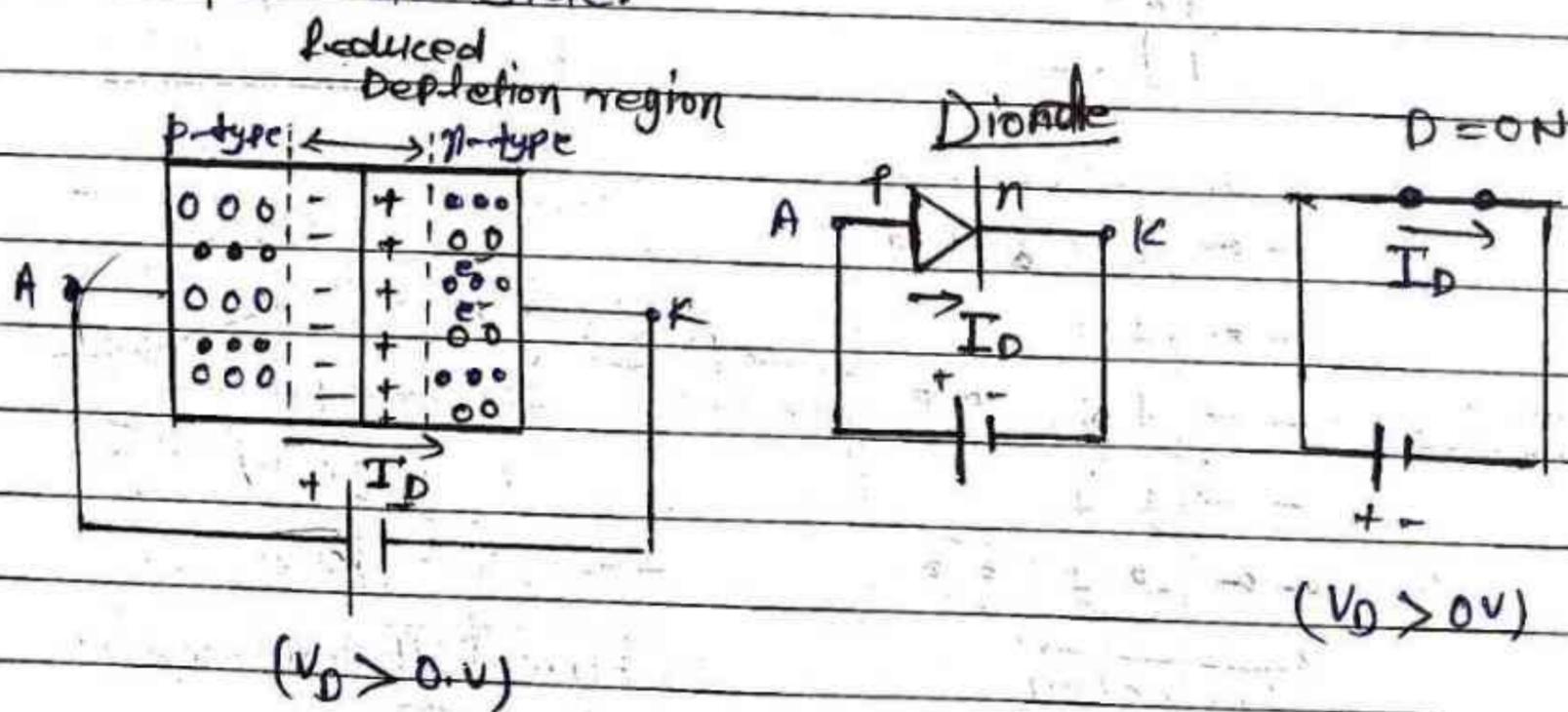\Rightarrow Under forward bias condition, some positive volts is applied b/w the anode and the cathode terminals. Such that the positive terminal of the battery is connected with the p-side and the negative terminal of the battery is connected with the n-side.



In this condition the electrons which are the majority charge carriers of the n-side will move from the n-side towards the p-side therefore, a conventional current will flow from the Anode terminal towards the cathode terminal. This current is known as forward current of a diode and is given by the eqⁿ which is known as diode current eqⁿ

Where- I_D = Diode current or forward current
 I_0 = Reverse saturation current

Diode current eqⁿ :-

$$I_D = I_0 \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$$

Where,

I_D = Diode current or forward current

I_0 = Reverse saturation current

V_D = Applied voltage across a diode

η = Constant

1 (Ge)

2 (Si)

V_T = Voltage equivalent of temperature

$$V_T = \frac{kT}{q} = \frac{T}{11600}$$

K = Boltzmann's Constant = 1.38×10^{-23} J/K

q = Electric charge 1.6×10^{-19} C

T = Diode junction temp (°K)

$$V_T = 26 \text{ mV (at room temp.)}$$


* Note :- Under forward bias condition the width of Depletion region decreases.

$$I_D = I_0 \left[e^{\frac{V_D}{\eta K T}} - 1 \right]$$

$$= I_0 \left[e^{\frac{q V_D}{\eta K T}} - 1 \right]$$

Case-III → Reverse Bias Condition. (ie, $V_D < 0V$)

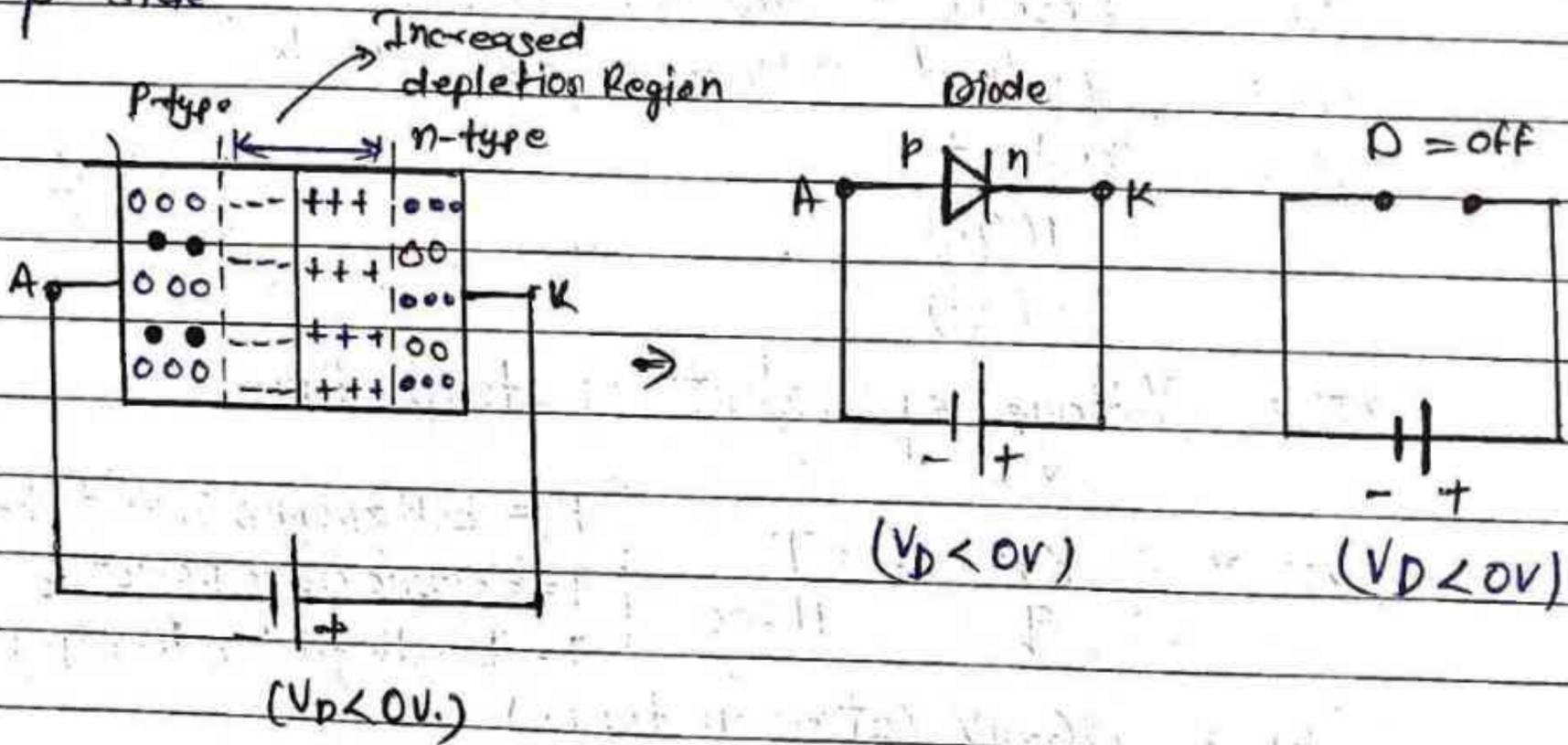Under reverse bias condition, some -ve voltage is applied within b/w the anode terminals and the cathode terminals. Such that, the (+ve terminal of the battery is connected to ϕ with n-side and the -ve terminal of the battery is connected with the p-side



* Note :- Under reverse bias condition, the width of depletion region increases.



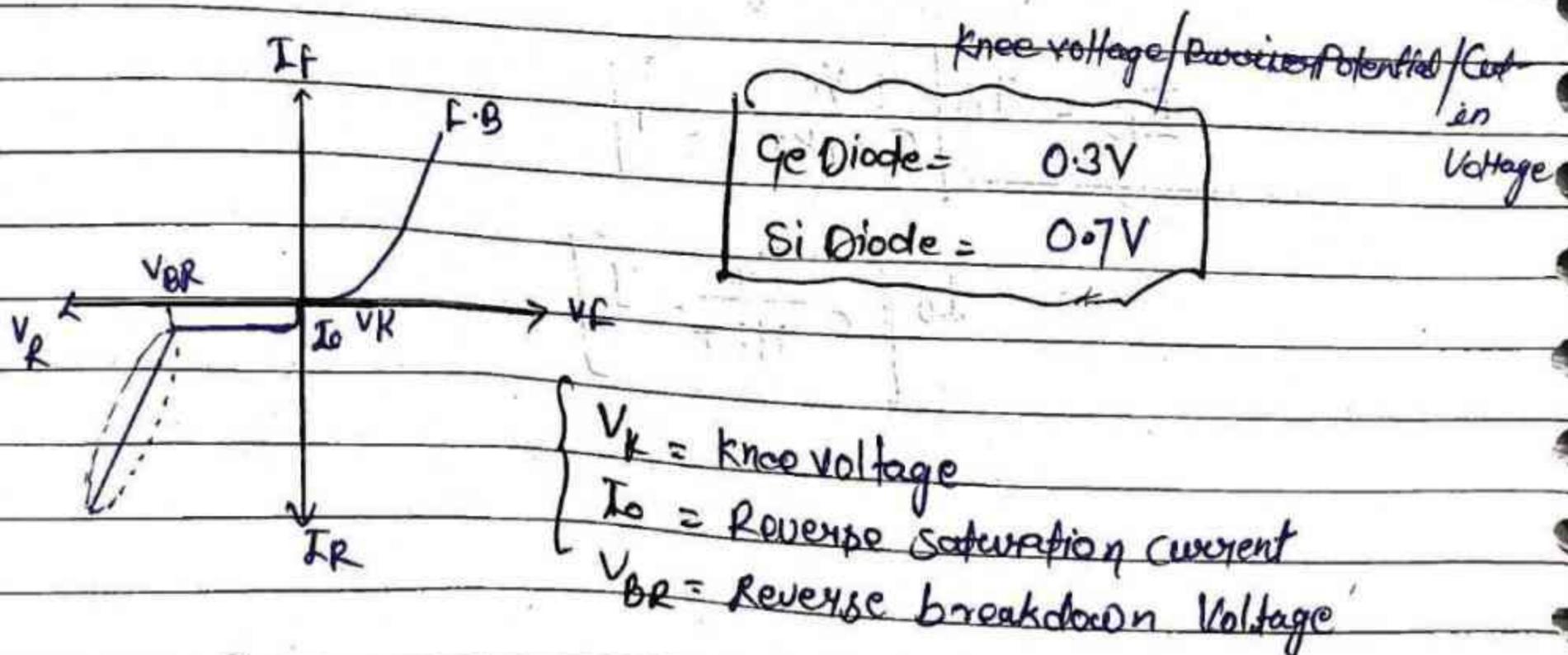


Fig → V-I characteristic of P-n junction Diode

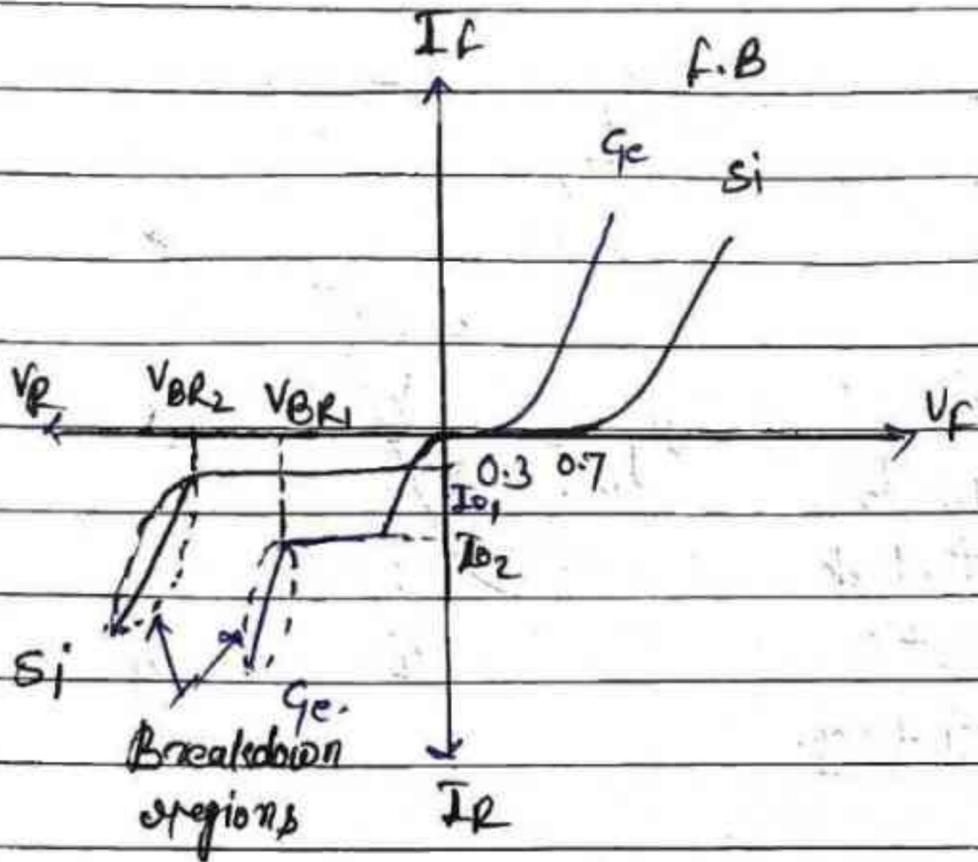

Ge Diode \rightarrow 0.3V, I_{02} , V_{BR1}
 Si Diode \rightarrow 0.7V, I_{01} , V_{BR2}


Fig:- V-I characteristic of Semiconductor Diode (Ge & Si)

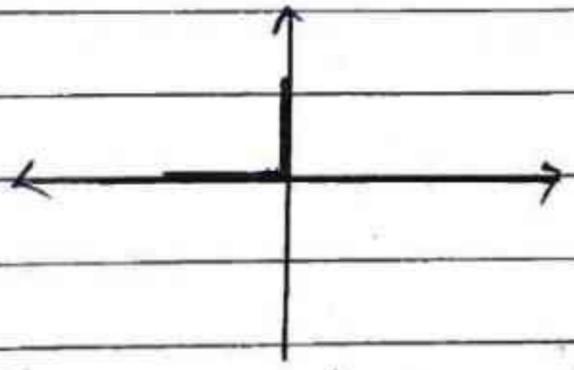

- * Infinite amount of current
- * Zero knee voltage
- * Zero voltage saturation current

Fig:- characteristic of an Ideal Diode.


Diode Equivalent Circuit :-

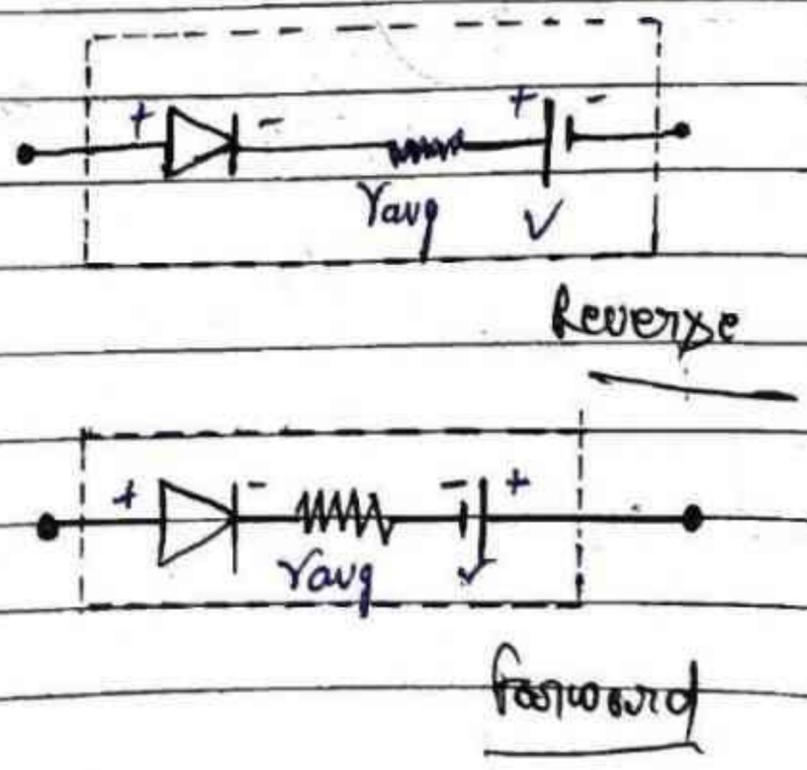

② Transition Capacitance :- It is observed across a diode under reverse bias condition.

It is denoted by C_T and is also known as Depletion Capacitance of a diode.

$$C_T = \frac{K}{\sqrt{V}}$$

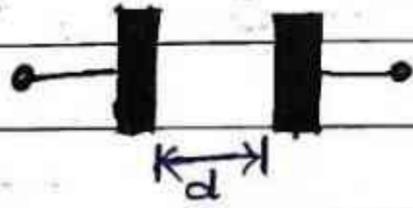

$$C = \frac{\epsilon A}{d}$$


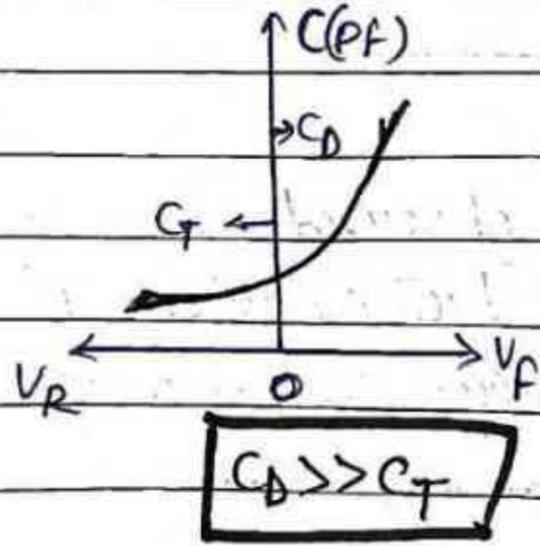


Fig. Capacitance Vs Applied Voltage across a diode.

* Average a.c. resistance :-

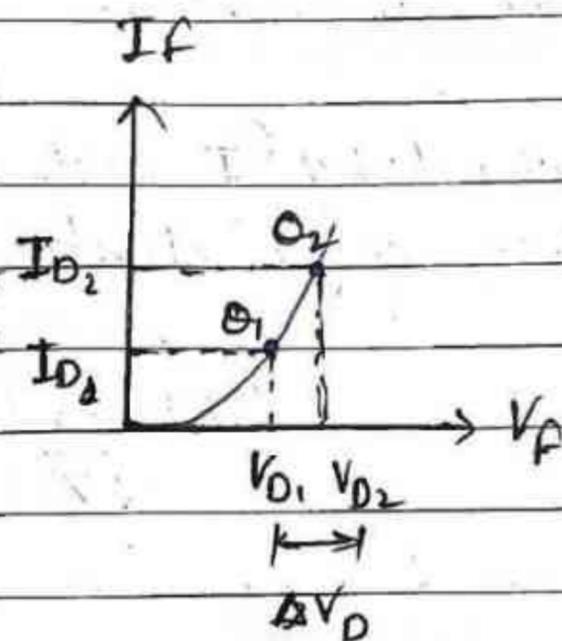It is defined as the ratio of change in voltage across a diode (ΔV_D) to the change in current across a diode (ΔI_D) b/c of two operating points Q_1 and Q_2



$$r_{avg} = \frac{\Delta V_D}{\Delta I_D} \quad \text{b/c of } Q_1 \text{ and } Q_2$$

Diode Capacitances :-

① Diffusion Capacitance :- It is observed across a diode under forward bias condition. It is denoted by C_D and it is also known as Storage capacitance of a diode.

$$C_D = \frac{\tau I_D}{\eta V_T}$$

Where

τ = mean life time period of carriers

I_D = forward current or diode current

η = constant

= 1 (Ge)

= 2 (Si)

V_T = voltage equivalent of Temp²


Q → Quiescent / operating

* Diode Resistances :-

Q → Quiescent

① Static Resistance :-

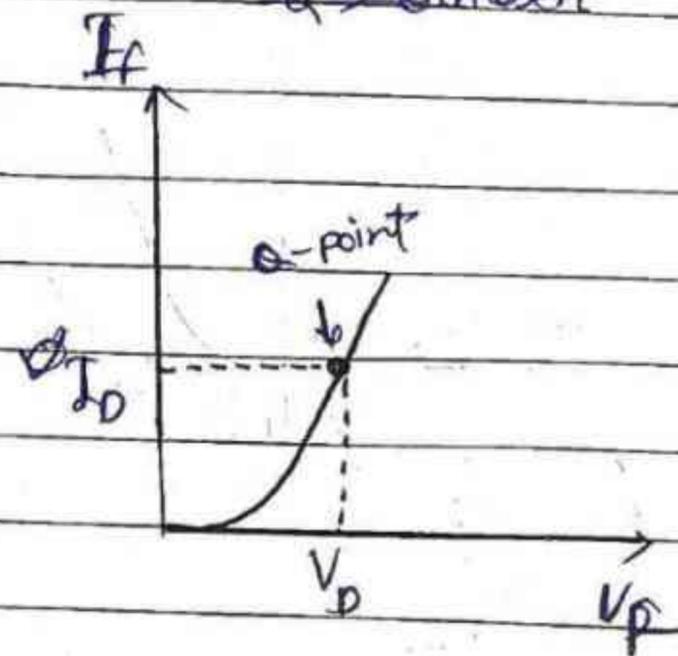
It is defined as the ratio of voltage across a diode (V_D) to the current across a diode (I_D) at a single operating point Q. It is also known as D.C. resistance of a diode.



$$R_D = \frac{V_D}{I_D} \quad \text{at Q. Point}$$

② Dynamic Resistance :-


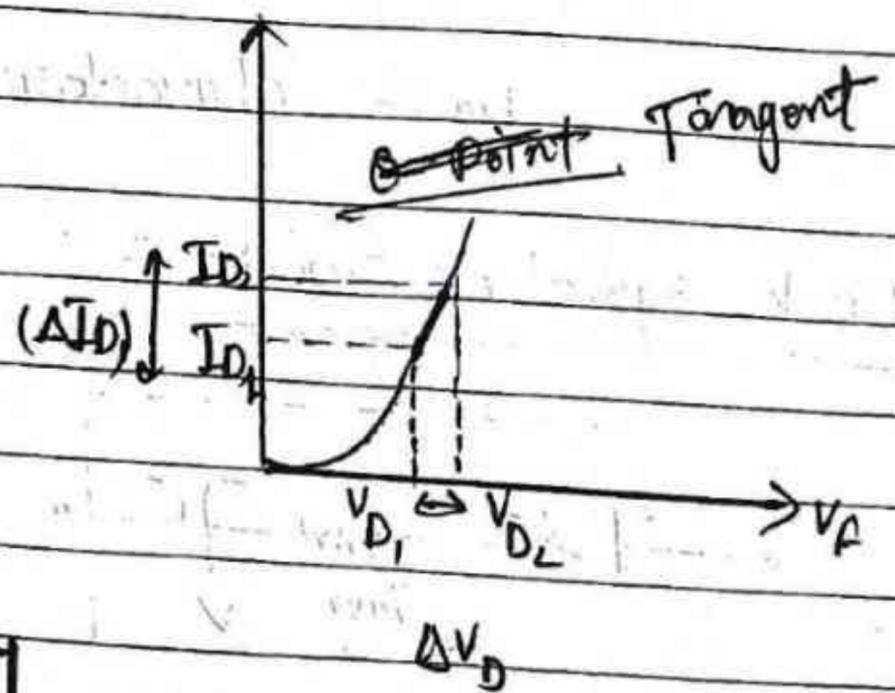
It is defined as the ratio of change in voltage across a diode (ΔV_D) to the change in current across a diode (ΔI_D) because of tangent drawn at Q-Point. It is also known as a.c. resistance of a diode.



$$r_D = \frac{\Delta V_D}{\Delta I_D} \quad \text{b/c of tangent drawn at a point}$$

$$r_D = \frac{\eta V_T}{I_0 + I_D}$$

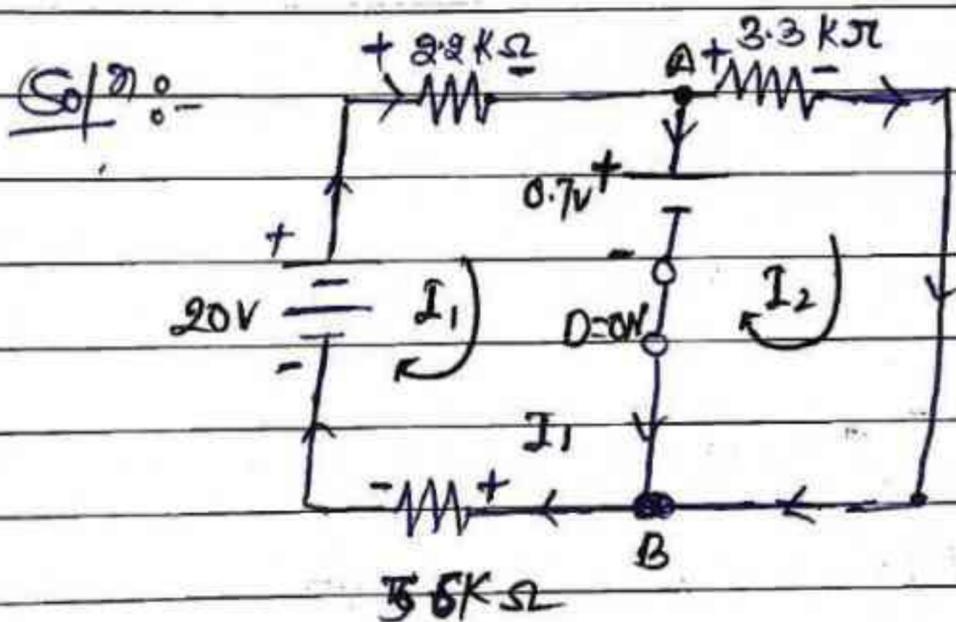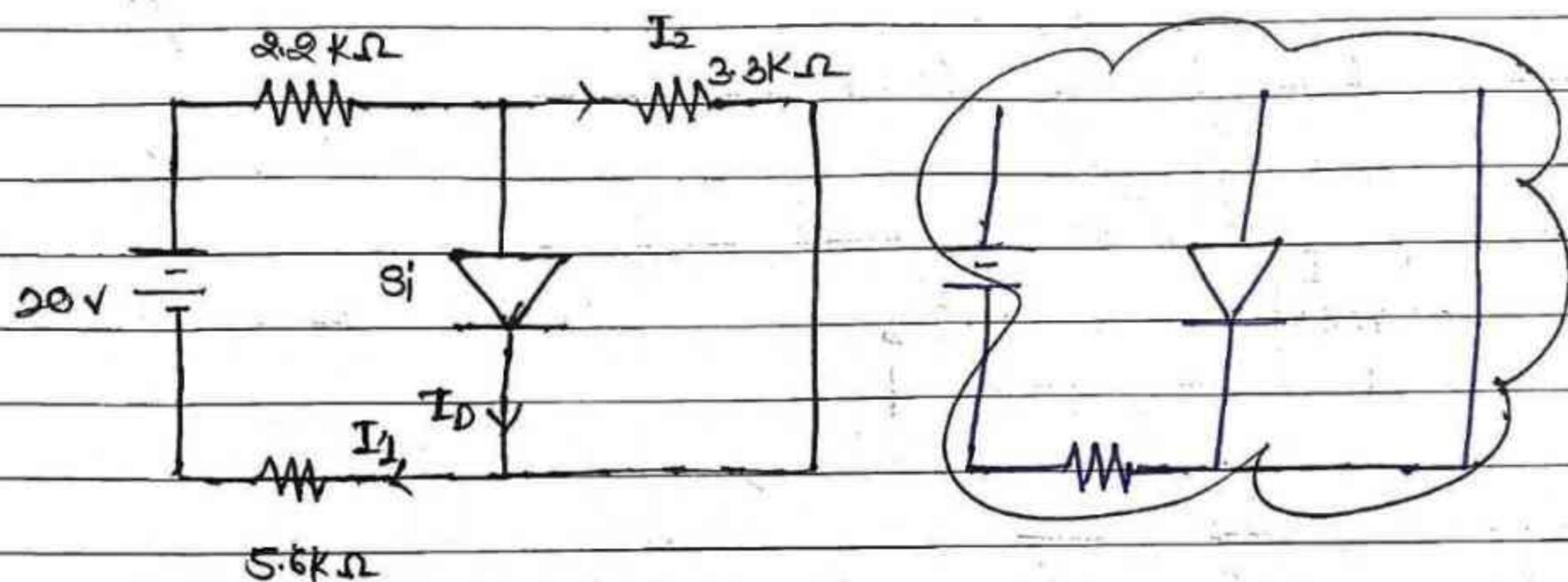Ques 8 Determine I_1 , I_2 and I_D for the given circuit.



Using KVL.

$$20 - 2.2I_1 - 0.7 - 5.6I_1 = 0$$

$$19.3 - 7.8I_1 = 0$$

$$I_1 = \frac{19.3}{7} = 2.47 \text{ mA}$$

and

$$-3.3I_2 + 0.7 = 0$$

$$I_2 = \frac{0.7}{3.3} = 0.21 \text{ mA}$$



Now, by using KCL at point A

$$I_1 = I_2 + I_D$$

$$2.47 = 0.21 + I_D$$

$$2.26 = I_D$$
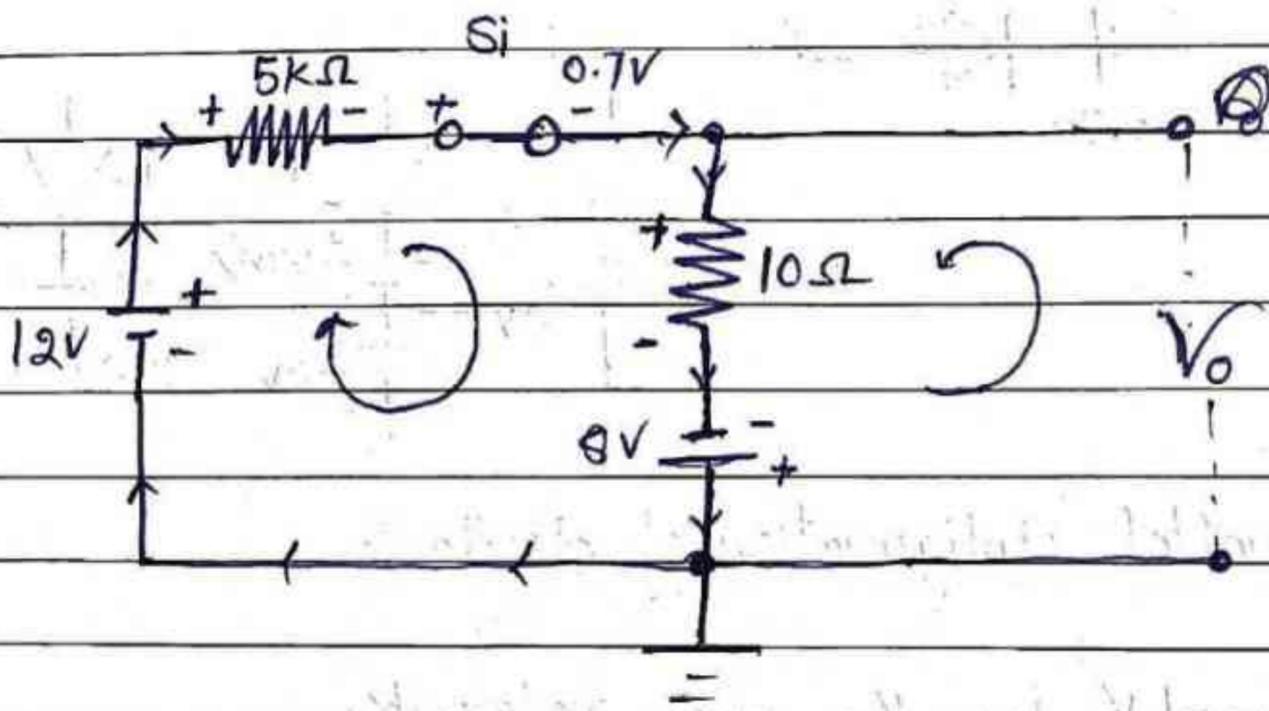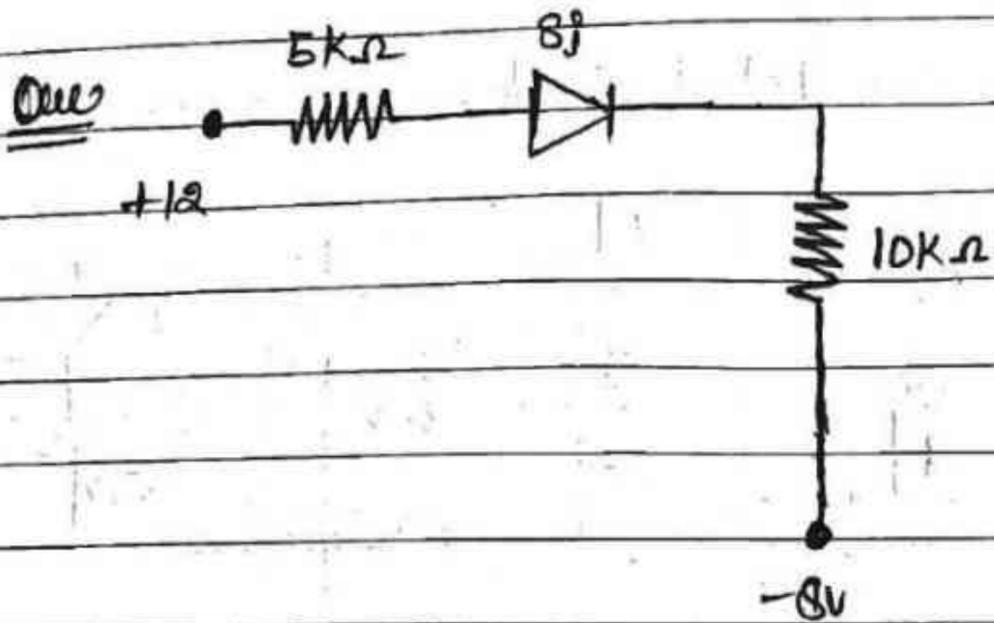
$$I_D = 2.26 \text{ mA} \quad \underline{\underline{\text{Ans}}}$$



$$12 - 5I_D - 0.7 - 10I_D + 8 = 0$$

$$20 - 15I_D - 0.7 = 0$$

$$+15I_D = +19.3$$

$$I_D = \frac{19.3}{15} = 1.28$$


$$-10I_D + 8 + V_0 = 0$$

$$-10 \times 1.28 + 8 + V_0 = 0$$

$$-12.8 + 8 + V_0 = 0$$



$$V_0 = +4.8 \text{ Ans}$$

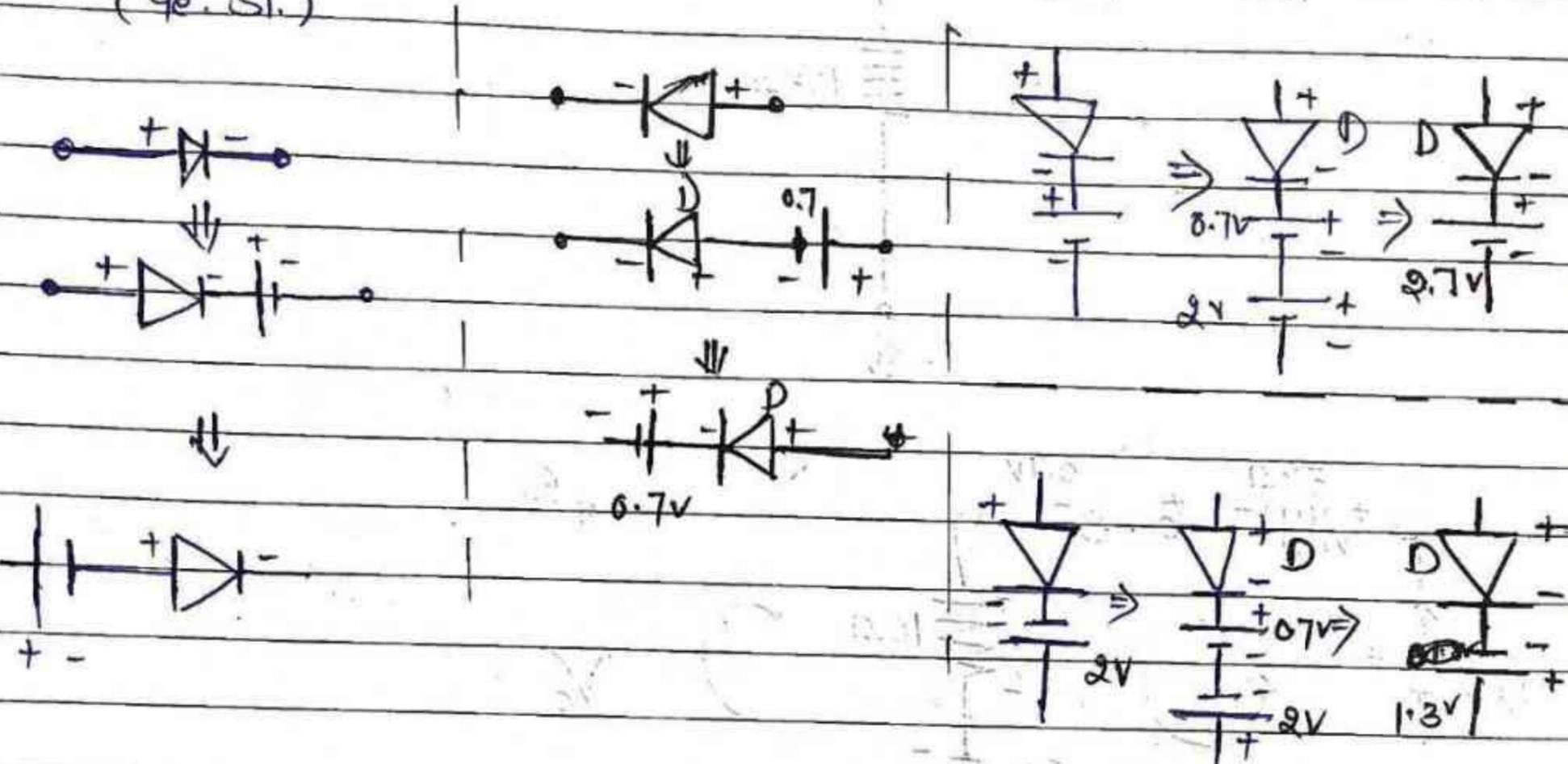* Practical Diode :- (Change) → Ideal diode
(Ge, Si.)



* Series and parallel Configuration of diode :-

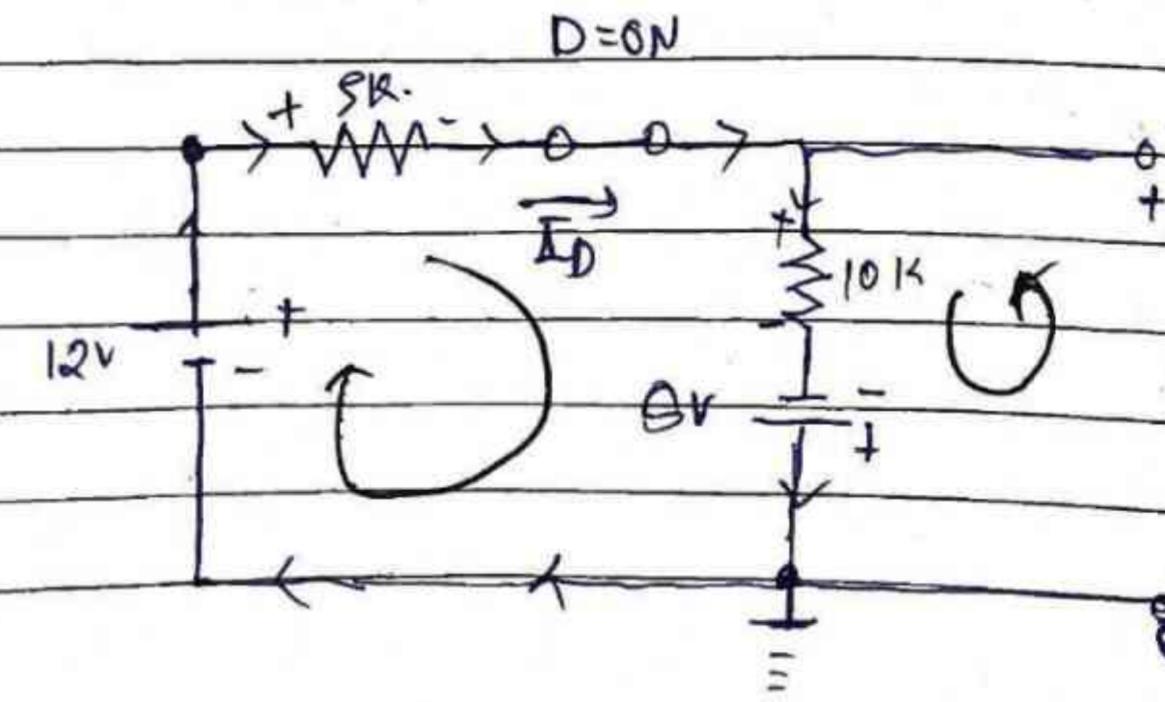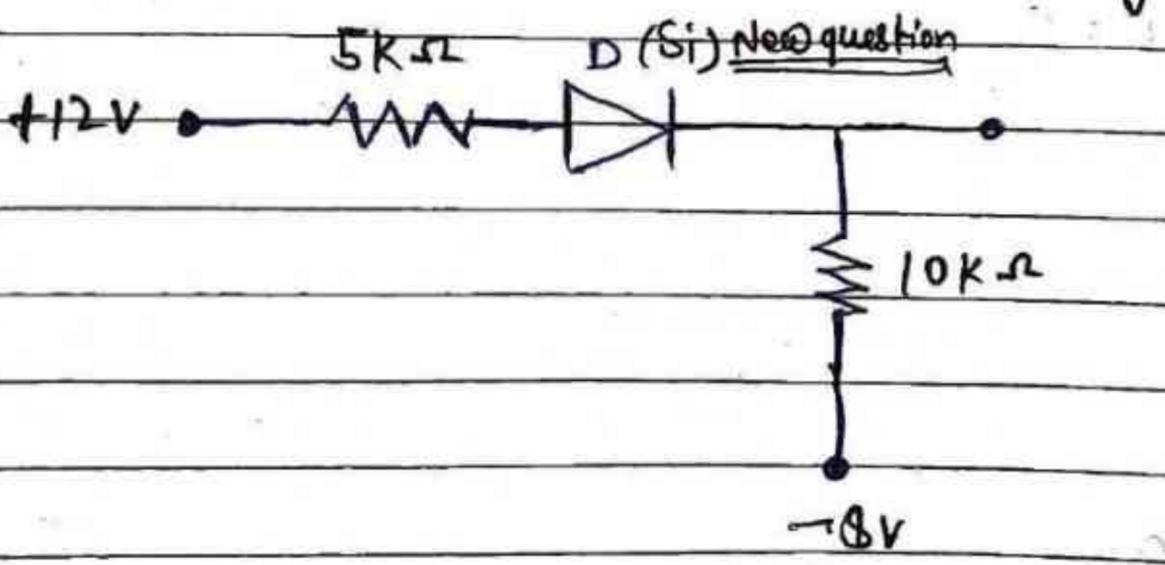Que :- Determine I_D and V_o for the given network.



Using KVL

$$12 - 5I_D - 10I_D + 0 = 0$$

$$20 - 15I_D = 0$$

$$15I_D = 20$$

$$I_D = \frac{20}{15} = 1.33 \text{ mA}$$

and

$$-10I_D + 0 + V_o = 0$$



$$V_o = 10I_D = 0$$

$$= (10 \times 1.33) - 8$$

$$= 13.3 - 8$$

$$V_o = 5.3 \text{ V}$$

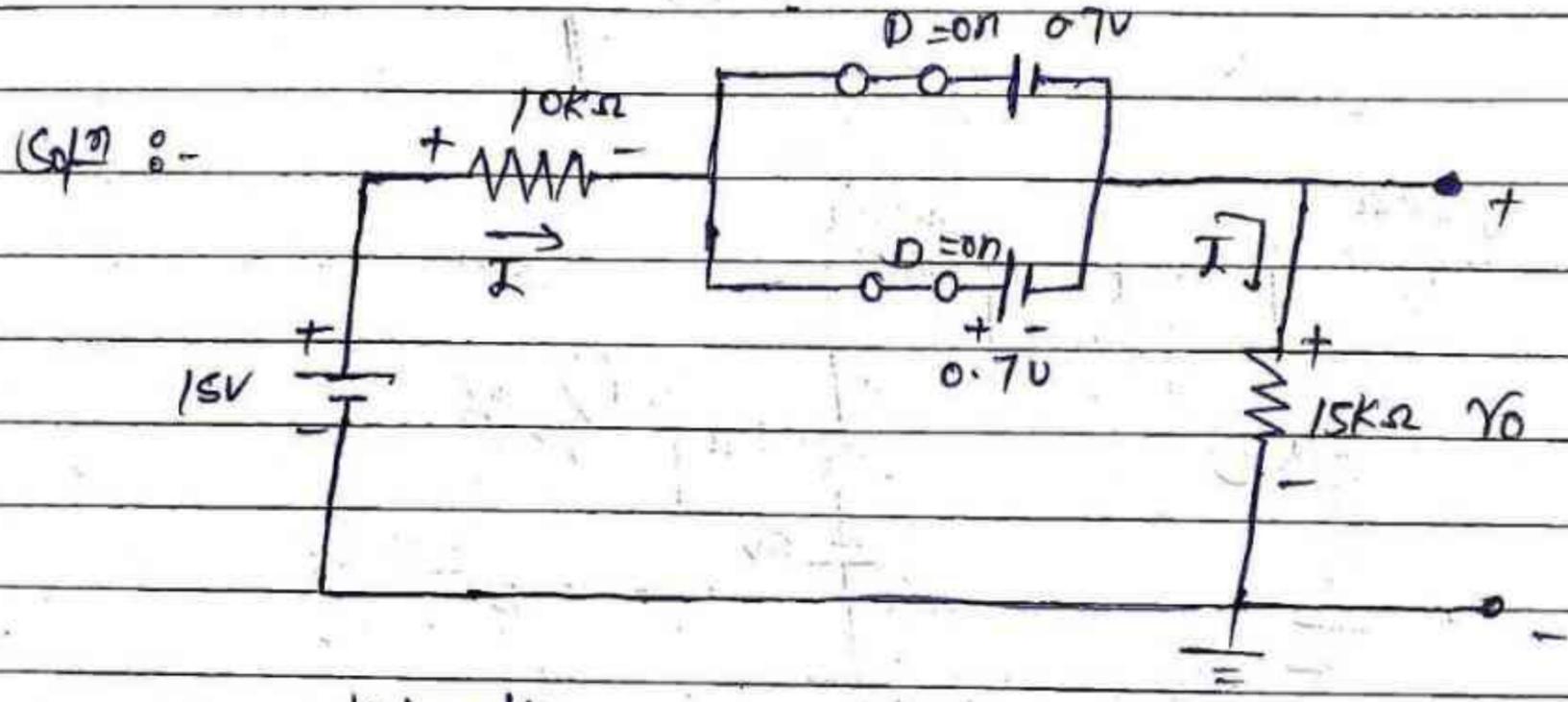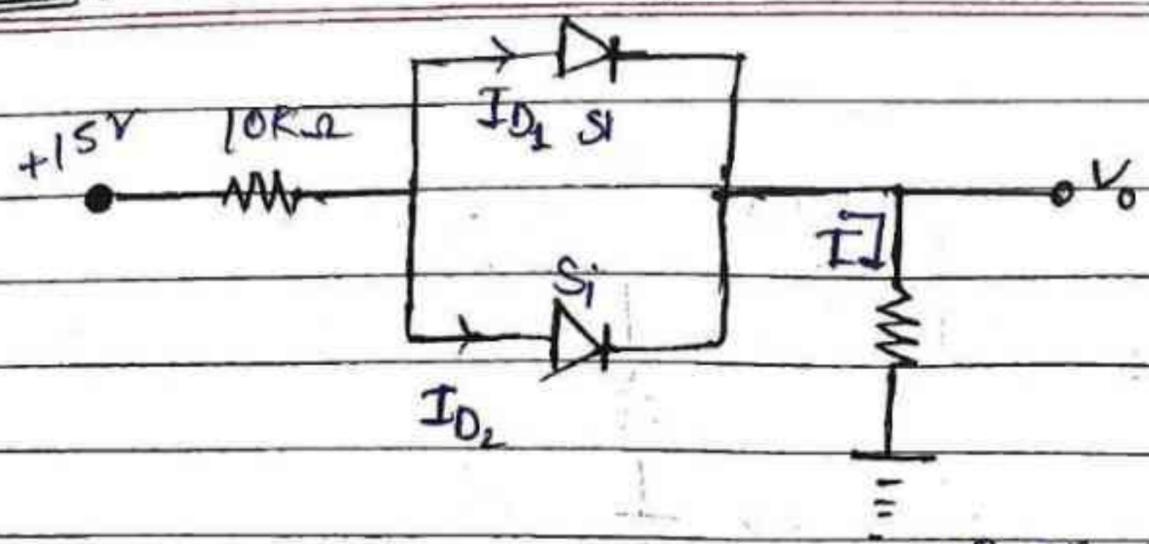Ques :- Determine the I_{D1} , I_{D2} and V_o for the given network



Using KVL

$$15 - 10I - 0.7 - 15I = 0$$

$$25I = 14.3$$



$$I = 0.572$$

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.572}{2} = \boxed{0.286 \text{ mA}}$$

$$-15I + V_o = 0$$

$$-15 \times 0.572 = -V_o$$

$$\boxed{V_o = 8.58 \text{ V}}$$

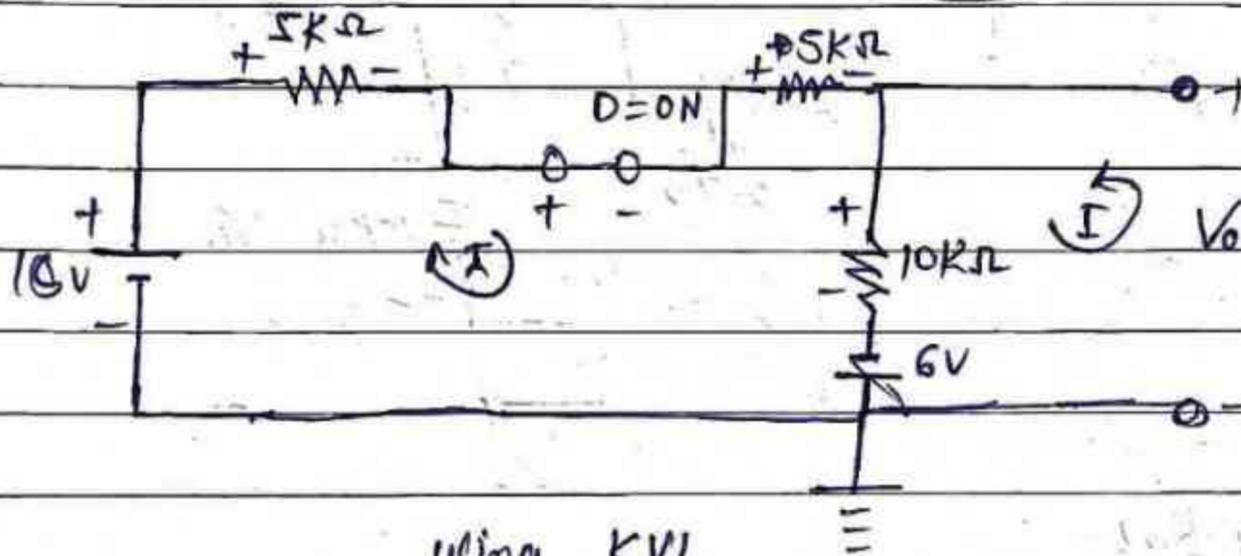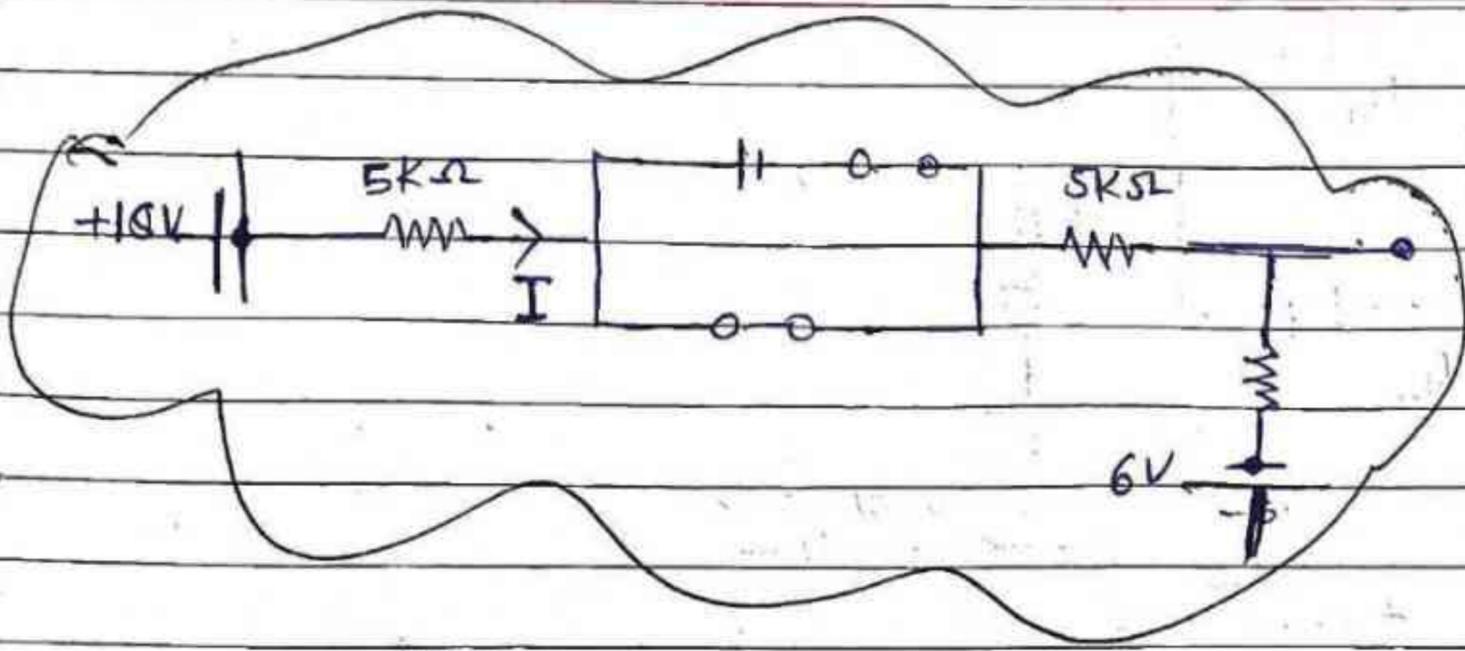

Using KVL

$$10 - 5I - 5I - 10I + 6 = 0$$

$$I = \frac{24}{20} = 1.2 \text{ mA}$$

$$\text{and } -10I + 6 + V_o = 0$$


$$V_o = 10I - 6$$

$$= (10 \times 1.2) - 6 = 12 - 6$$

$$\underline{\underline{V_o = 6}}$$

~~Case 1~~


* Current divider rule (CDR)

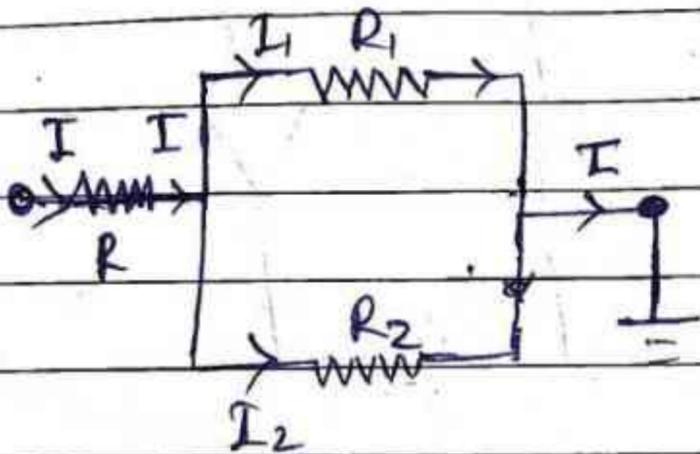

$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$


$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$

* Voltage divider rule (VDR)

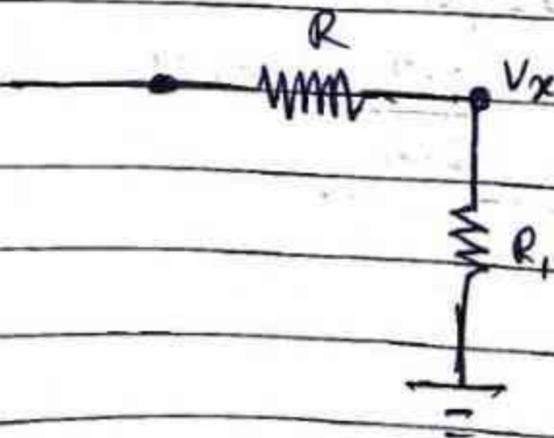

$$V_x = \frac{R_1}{R + R_1} \times V$$

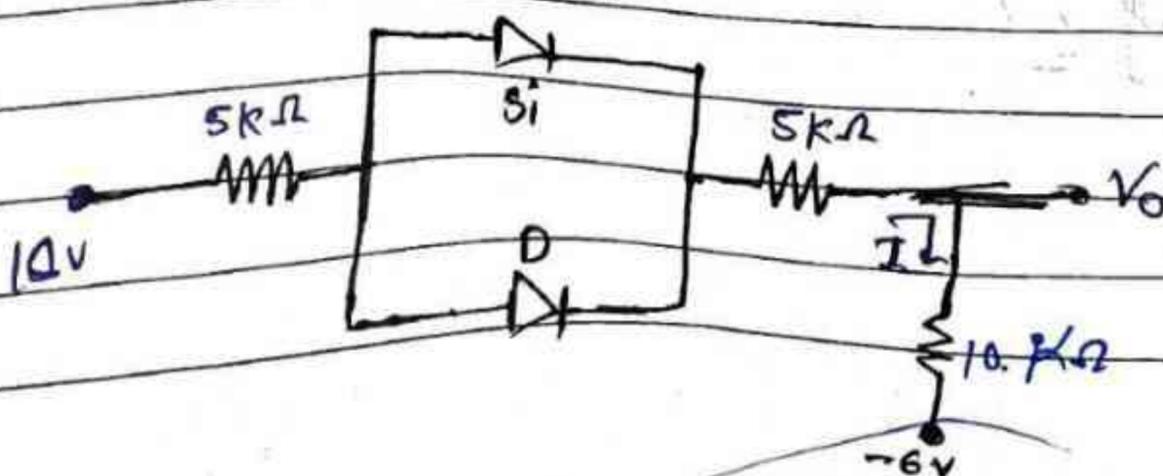Que :- Determine I and V_0 for the given circuit



Rectifier

Half wave Rectifier (HWR)

Full wave Rectifier (FWR)

uses 1 diode


Center-Tapped (FWR)
(CT-FWR)

Bridge-Type FWR
(BT-FWR)

uses 2 diode

uses 4 diode

* Half Wave Rectifier

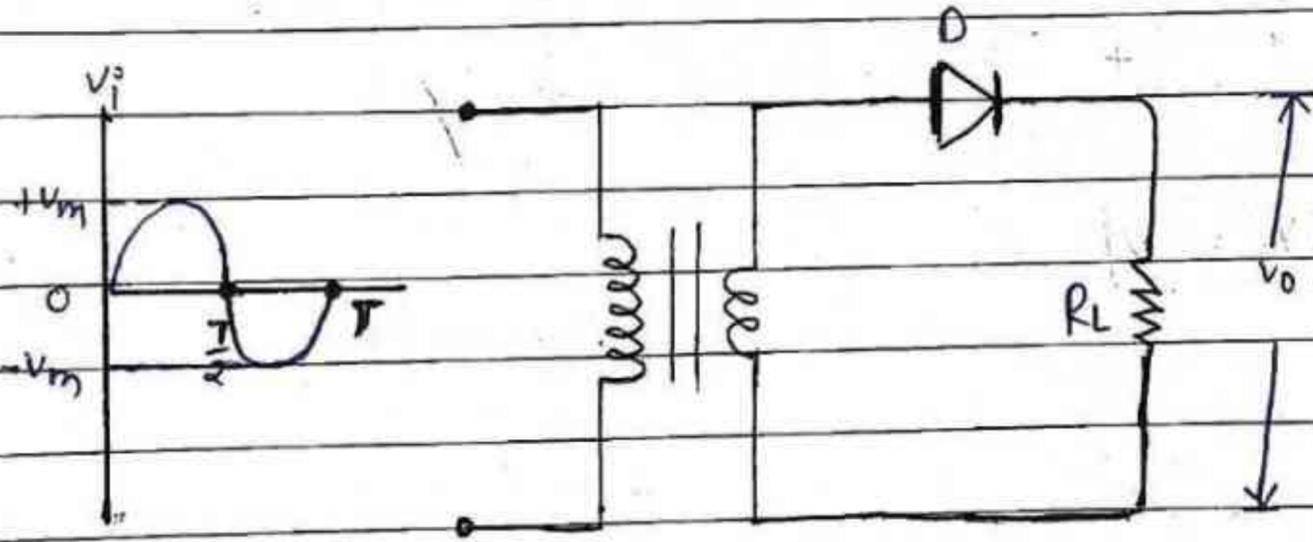


* Working

* Case I: During +ve half wave cycle:-

$$V_i = +V_m$$

$D = ON$

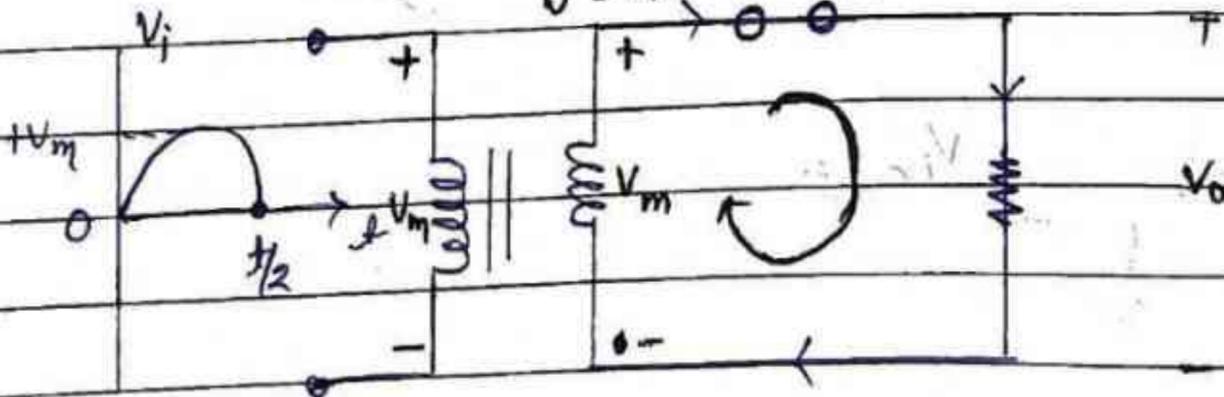

using KVL



$$V_m - V_o = 0$$

$$+V_o = +V_m$$



$$V_o = V_m$$

* Rectifier:

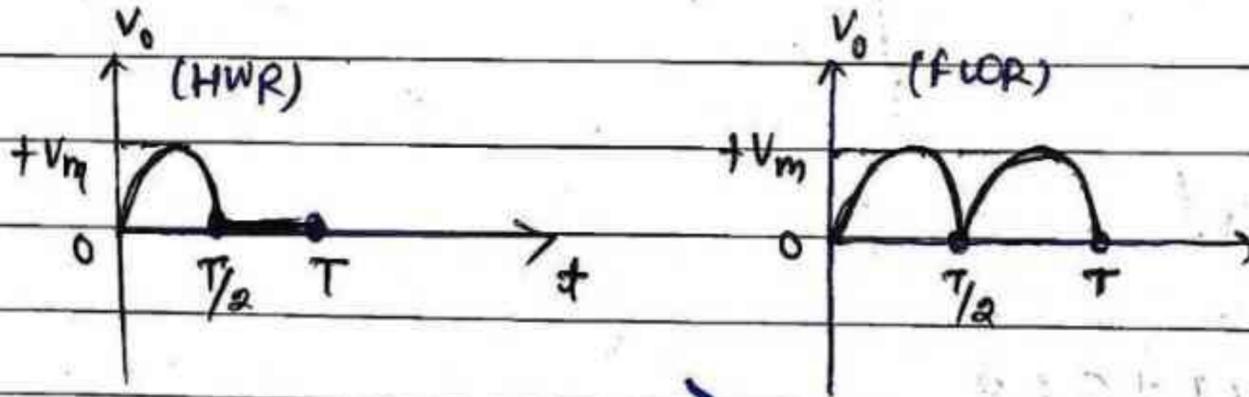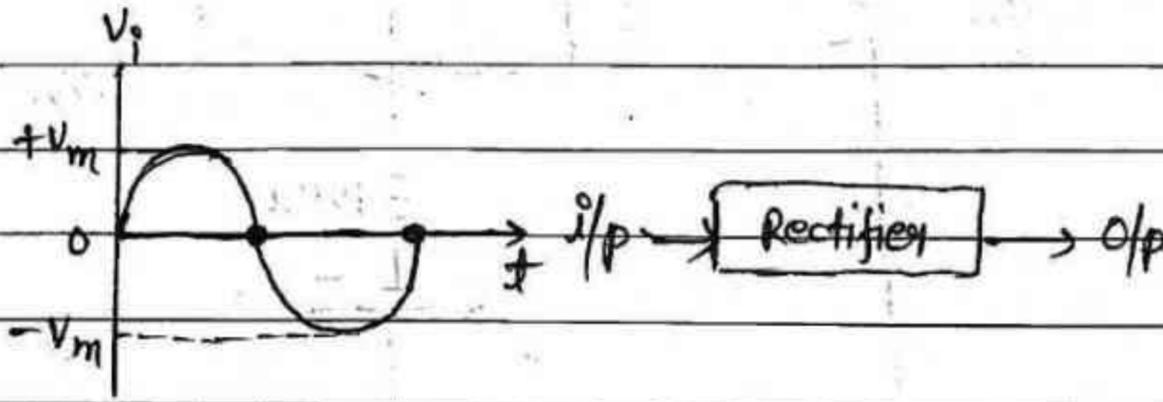Rectifier :- Rectifier is a circuit which is used to convert ac. signal into pulsating D.C. signal.



Classification of Rectifier.

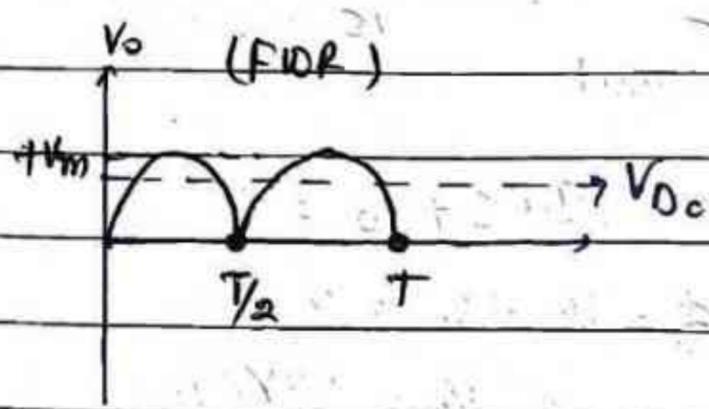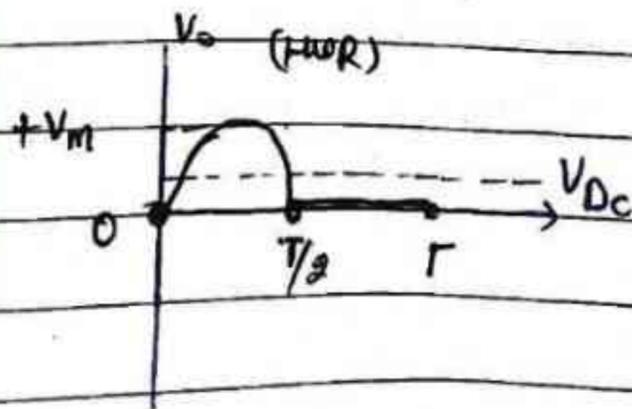


$$V_{DC} = \frac{V_m}{\pi} = 0.318 V_m$$

(HWR)

$$V_{DC} = \frac{2V_m}{\pi} = 0.636 V_m$$

(FWR)

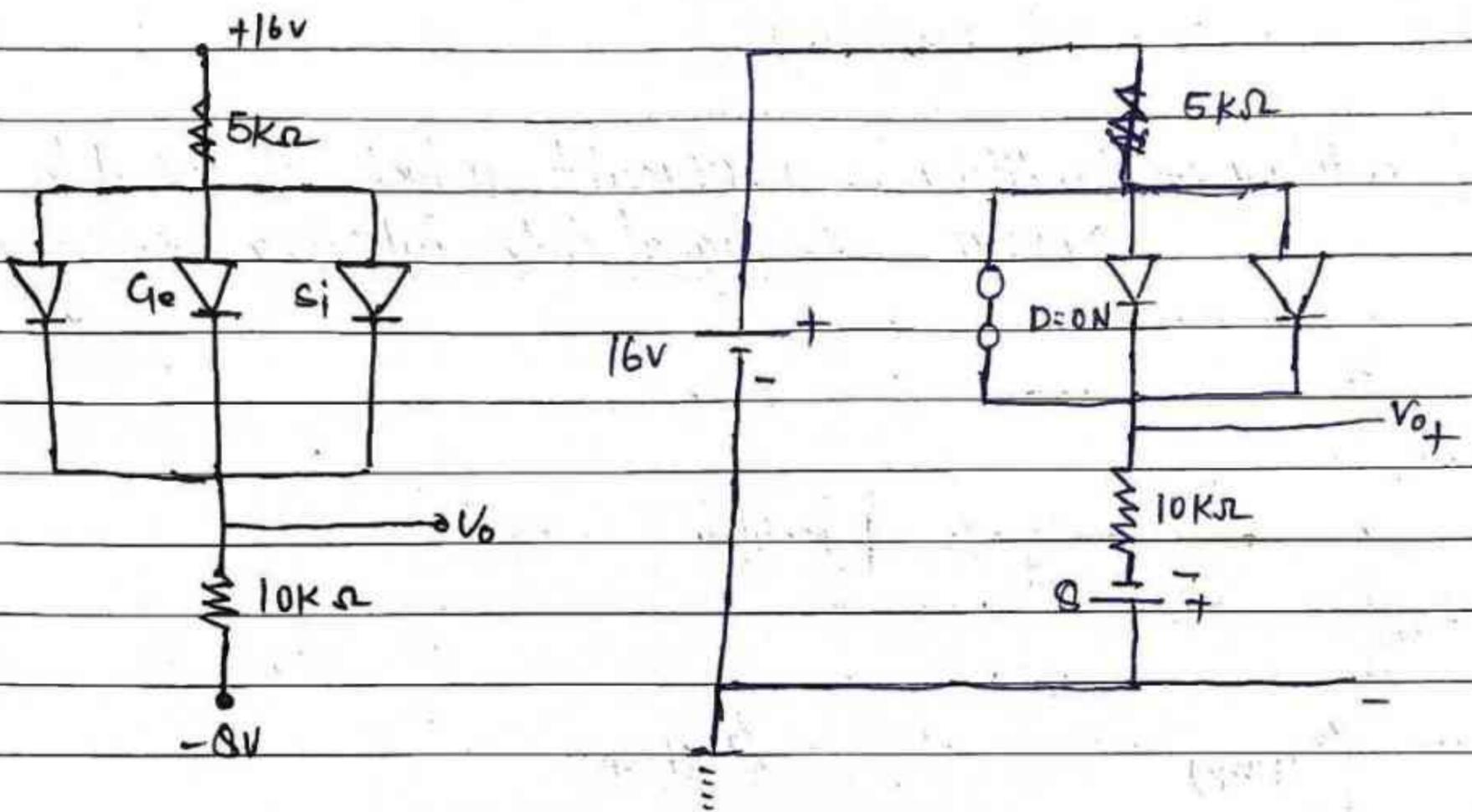Ques

using KVL

$$16 - 5I - 10I + 0 = 0$$

$$15I = 16$$

$$I = \frac{16}{15} = 1.06 \text{ mA}$$

and

$$-10I + 0 + V_o = 0$$

$$-16 + V_o = 0$$

$$V_o = 16 \text{ V}$$

CASE - II During -ve Half Cycle


$V_i = -V_m$

$D_1 = \text{OFF}$

$D_2 = \text{ON}$

Page _____

Date _____

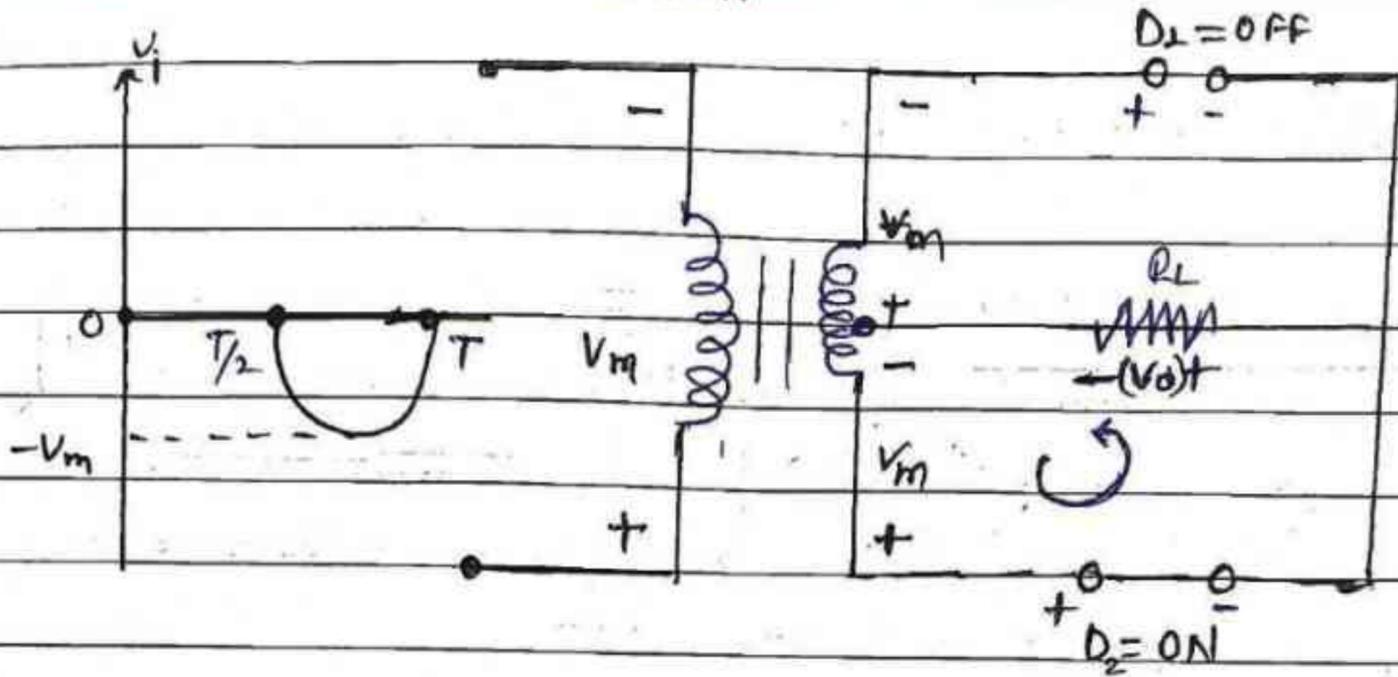

using KVL

$V_m - V_o = 0$

$+V_o = +V_m$

$V_o = V_m$


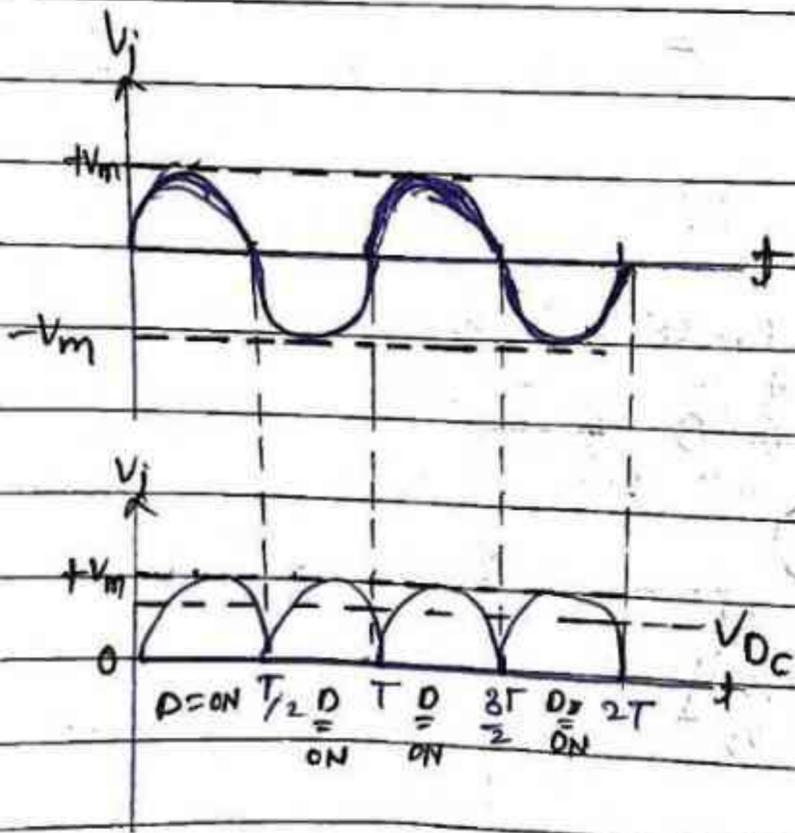


fig:- Input + output voltage wave from of CT-FWR


* Full Wave Rectifier (F.W.R.)

A) Center-Tapped FWR (CT-FWR)

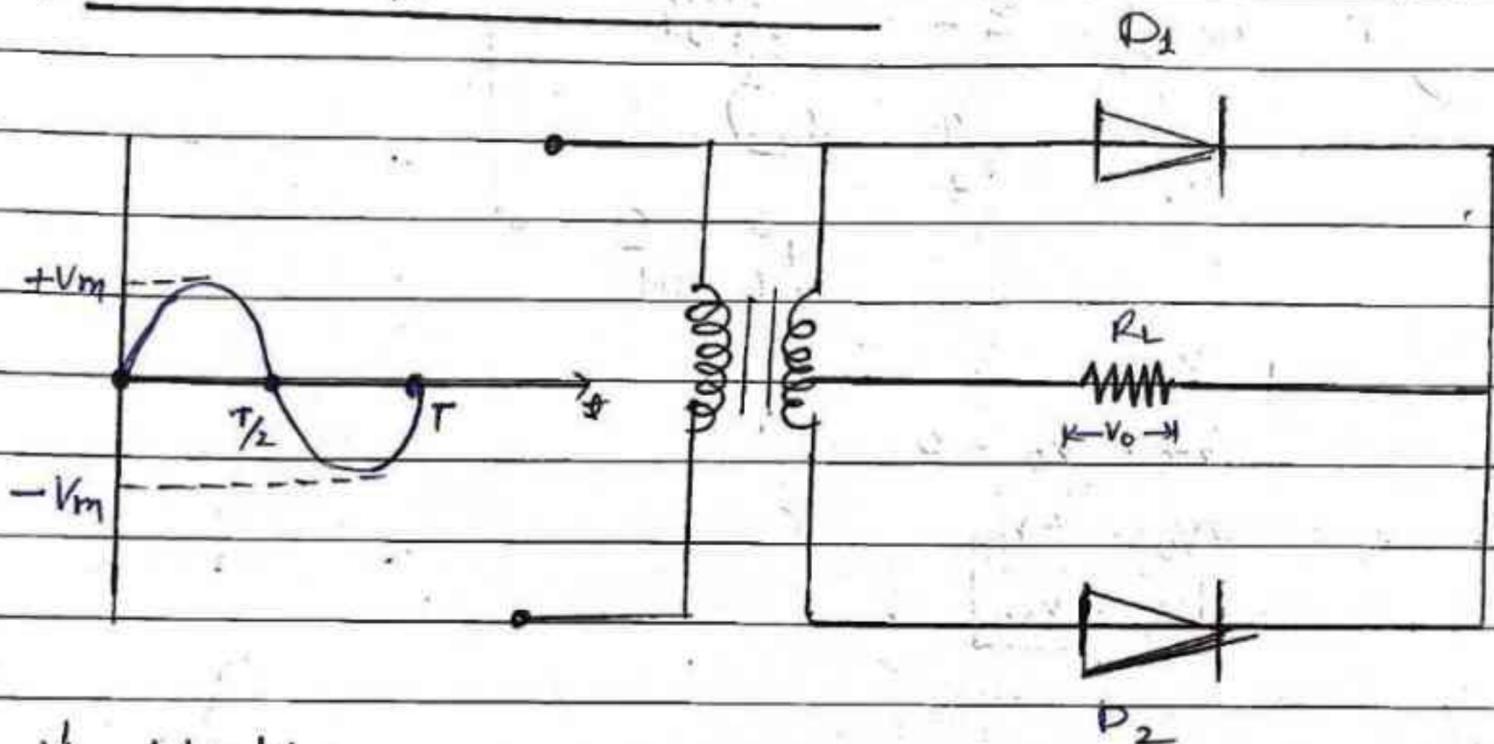

* ~~Blanking~~

* Case I : During +ve half cycle:

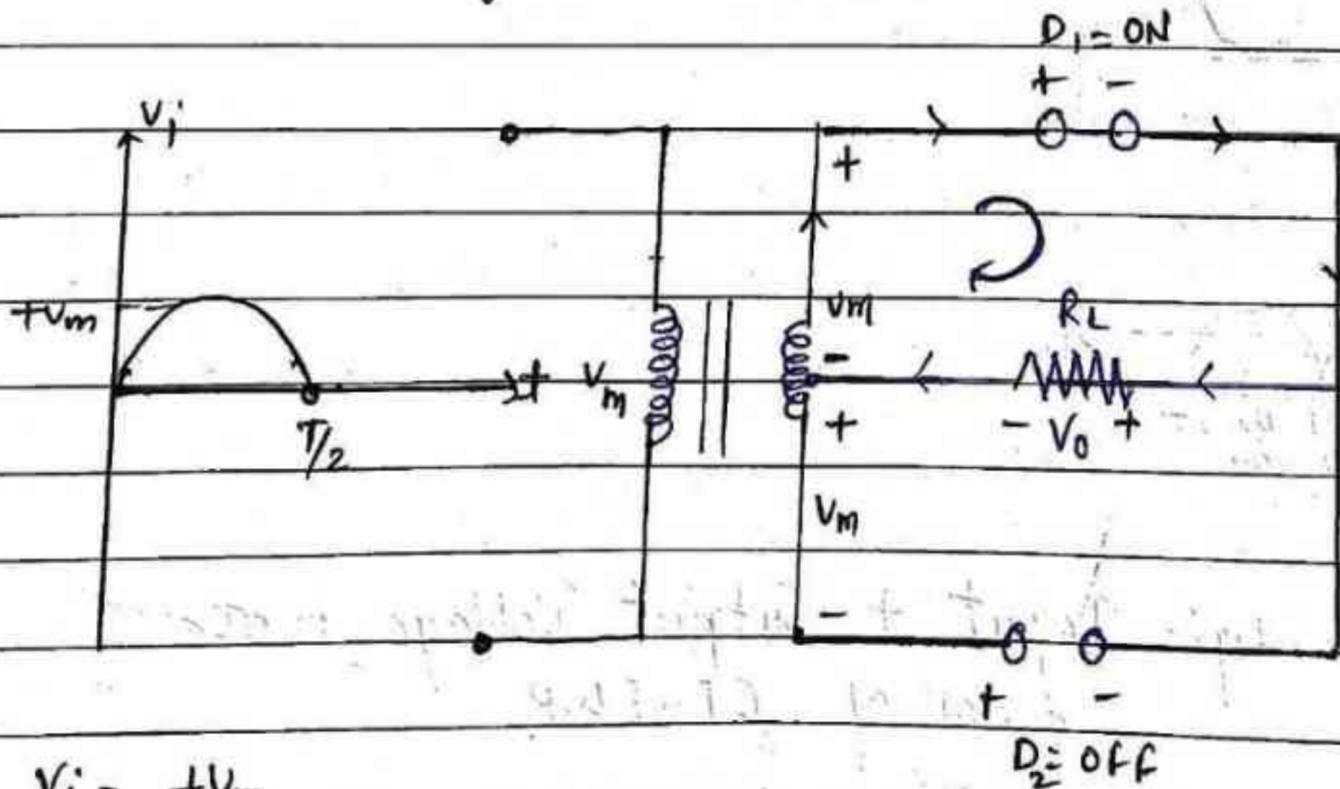

$$V_i = +V_m$$

$$D_1 = \text{ON}$$

$$D_2 = \text{OFF}$$

using KVL

$$V_m - V_o = 0$$


$$+V_o = +V_m$$

$$\boxed{V_o = V_m}$$


* Case-II ϕ - During -ve half cycle:

$$V_i = -V_m$$

$$D = \text{OFF}$$

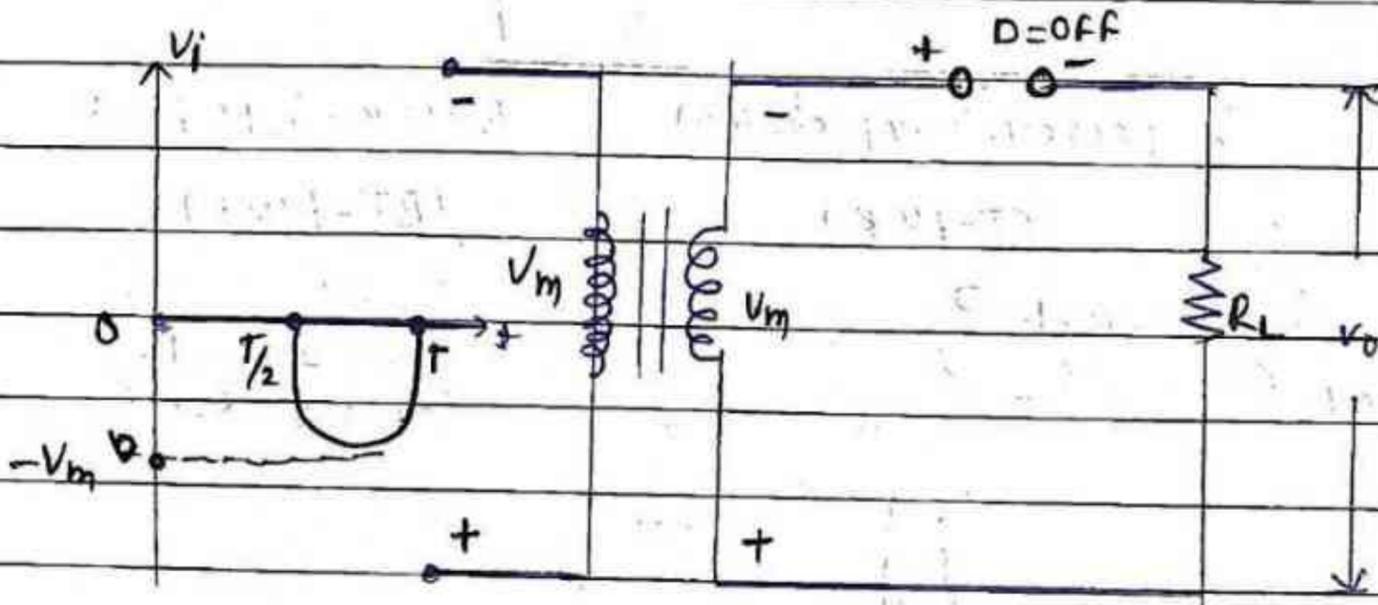

$$V_o = 0V$$

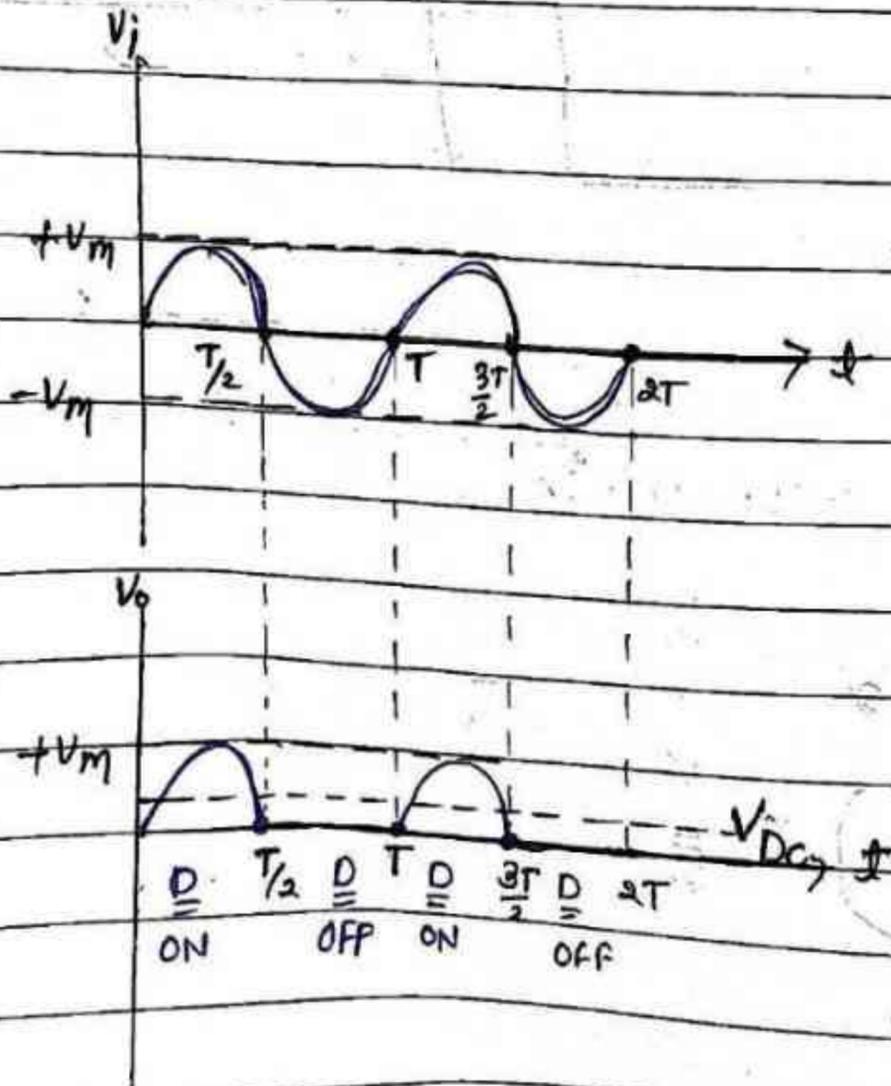

Ripple factor (R.F.) - It is define as the ratio of the r.m.s. value of the a.c. component of the output to the D.C. value of the output.

$$R.F. = \frac{\text{r.m.s. value of a.c. component of the output}}{\text{D.C. value of the output}}$$

$$R.F. = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}}$$

0.3854

0.118

* For HWR

$$R.F._{HWR} = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}}$$

$$\therefore V_{rms} = \frac{V_m}{2}$$

$$\therefore V_{DC} = \frac{V_m}{\pi}$$

$$R.F._{HWR} = \frac{\sqrt{\left(\frac{V_m}{2}\right)^2 - \left(\frac{V_m}{\pi}\right)^2}}{\frac{V_m}{\pi}}$$

$$\frac{V_m}{\pi}$$

$$= \frac{\sqrt{\frac{V_m^2}{4} - \frac{V_m^2}{\pi^2}}}{\frac{V_m}{\pi}}$$

$$\frac{V_m}{\pi}$$

$$= \sqrt{V_m^2 \left(\frac{1}{4} - \frac{1}{\pi^2} \right)}$$

$$\frac{V_m}{\pi}$$

$$= V_m \sqrt{\frac{1}{4} - \frac{1}{\pi^2}}$$

$$\frac{V_m}{\pi}$$

$$= \sqrt{\frac{1}{4} - \frac{1}{\pi^2}}$$


$$= \sqrt{\frac{1}{4} - \frac{1}{\pi^2}} \times \frac{\pi}{V_m} \times V_m$$

$$= \sqrt{\frac{1}{4} - \frac{1}{3.14^2}} \times 3.14 = 1.212330$$

$$R.F._{HWR} = 1.21$$

$$R.F._{HWR} = 121\%$$

Case-II During -ve half cycle.

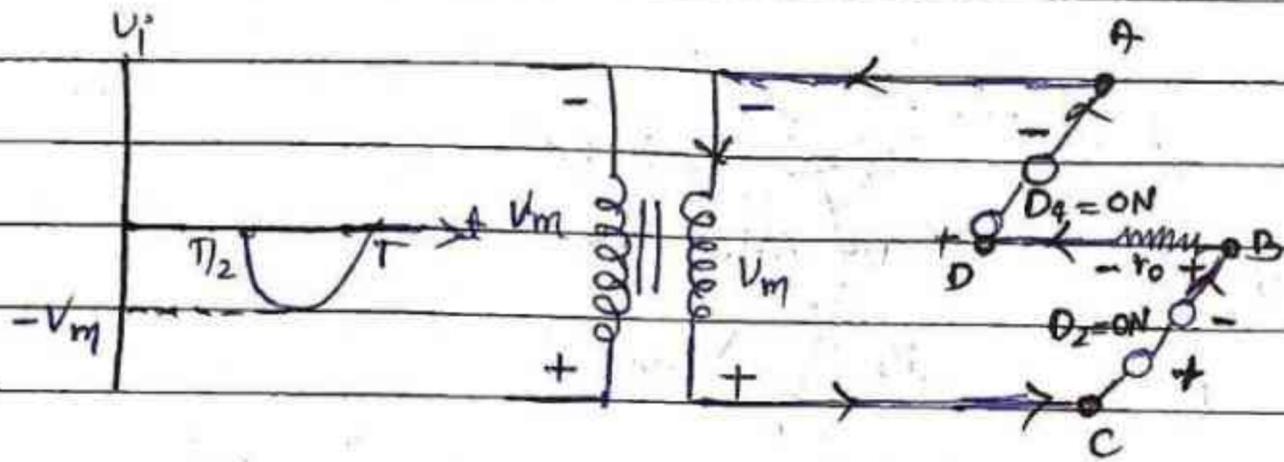

- $V_i = -V_m$
- $D_1 = \text{OFF}$
- $D_2 = \text{ON}$
- $D_3 = \text{OFF}$
- $D_4 = \text{ON}$

Using KVL

$$V_m - V_o = 0$$

$$+V_o = +V_m$$

$V_o = V_m$


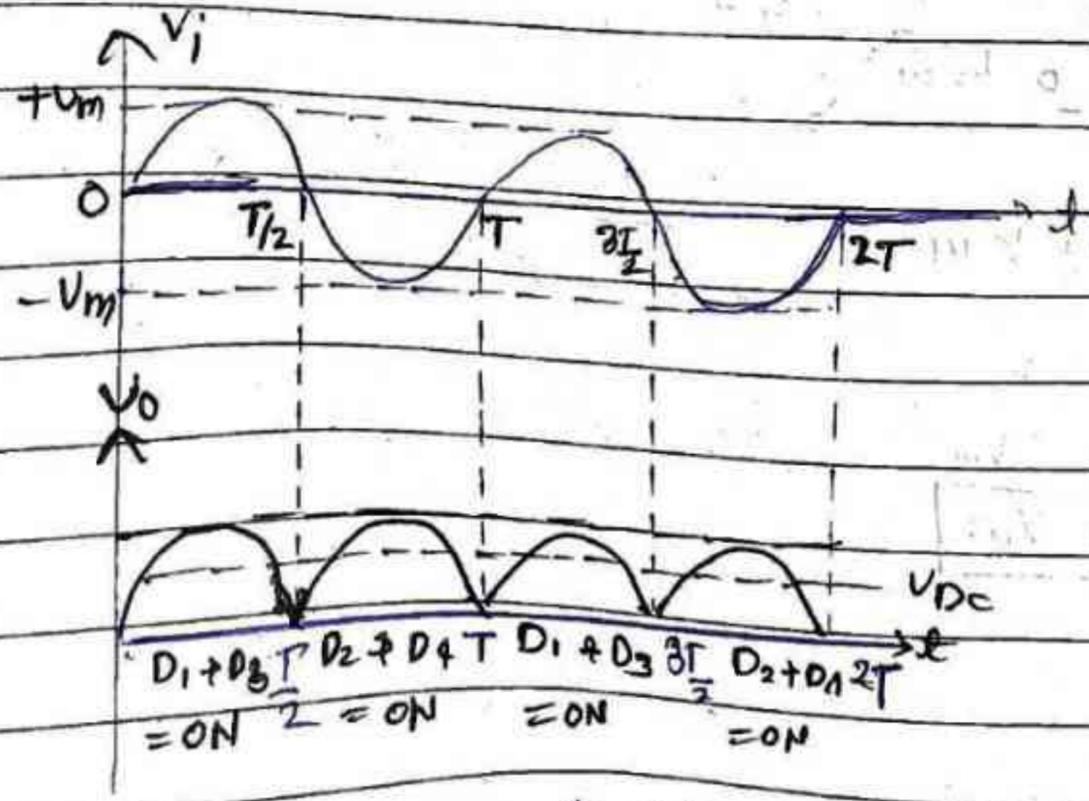


Fig 6- Input & output voltage waveform of BR-FWR

B. Bridge-type FWR (BT-FWR)

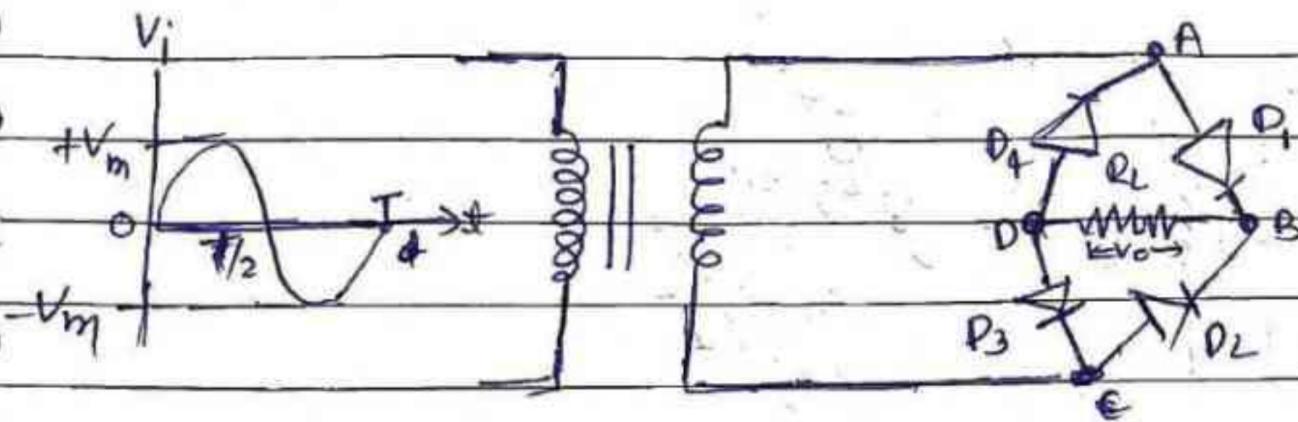

Working :-

Case - 1 During +ve half cycle.


$$V_i = +V_m$$

$$D_1 = \text{ON}$$

$$D_2 = \text{OFF}$$

$$D_3 = \text{ON}$$

$$D_4 = \text{OFF}$$

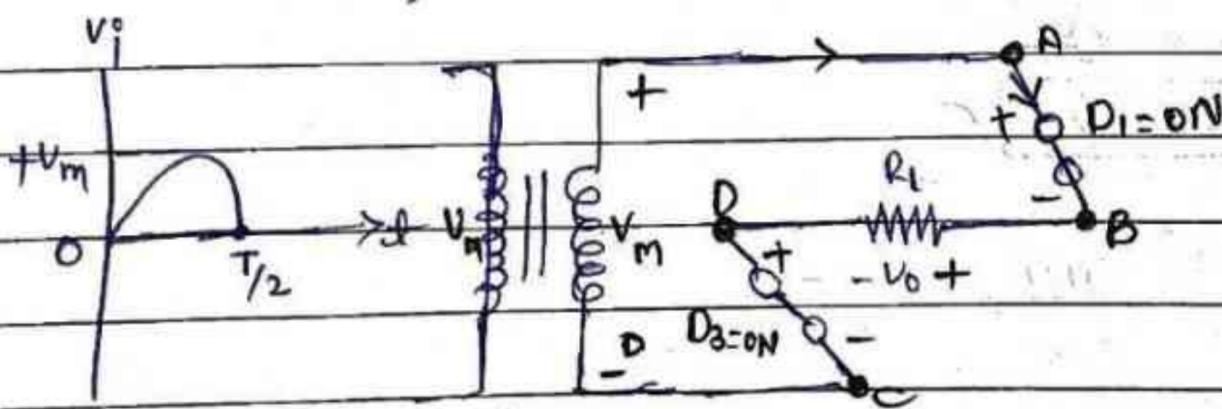

Using KVL

$$V_m - V_o = 0$$

$$+V_o = +V_m$$

$$\boxed{V_o = V_m}$$

For F.W.R \rightarrow (C.T-FWR \rightarrow B.T-FWR)

As,

$$\eta_{FWR} = \frac{I_{DC}^2 \cdot R_L}{I_{rms}^2 \cdot R_L} \left[\text{As, } (R_s + R_f) \ll R_L \right]$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\therefore \eta_{FWR} = \frac{\left(\frac{2I_m}{\pi}\right)^2 \cdot R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 \cdot R_L} = \frac{4I_m^2 \cdot R_L}{\pi^2} \cdot \frac{2}{I_m^2 \cdot R_L}$$

$$= \frac{4I_m^2 \cdot R_L}{\pi^2} \times \frac{2}{I_m^2 \cdot R_L} = \frac{8}{\pi^2} = \frac{8}{3.14^2} = 0.811391942$$

$$\eta_{FWR} = 0.811$$

or

$$\eta_{FWR} = 81.1\%$$

Key

Efficiency :- It is define as the ratio of output power to the input power. It is denoted by η and it is also known as rectification efficiency.

$$\eta = \frac{\text{out power}}{\text{input power}}$$

$$\eta = \frac{I_{DC}^2 \cdot R_L}{I_{rms}^2 \cdot R_L}$$

$$\eta = \frac{P_{DC}}{P_{AC}}$$

$$P = VI$$

$$P = I \cdot R \cdot I$$

$$P = I^2 R$$

$$\eta = \frac{I_{DC}^2 \cdot R_L}{I_{rms}^2 \cdot (R_s + R_f + R_L)}$$

$$\text{As } (R_s + R_f) \ll R_L$$

* For HWR :-

As,

$$\eta_{HWR} = \frac{I_{DC}^2 \cdot R_L}{I_{rms}^2 \cdot R_L} \left[\text{As } (R_s + R_f) \ll R_L \right]$$

$$I_{DC} = \frac{I_m}{\pi}$$

$$I_{rms} = \frac{I_m}{2}$$

$$\eta_{HWR} = \frac{(I_m/\pi)^2 \cdot R_L}{(I_m/2)^2 \cdot R_L} = \frac{I_m^2/\pi^2 \cdot R_L}{I_m^2/4 \cdot R_L} = \frac{4}{\pi^2} = 0.40569597$$

$$\eta_{HWR} = 0.406$$

$$\text{or } \eta_{HWR} = 40.6\%$$

FOR: FWR (CT-FWR \neq BT-FWR)

$$PF_{FWR} = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{DC} = \frac{2V_m}{\pi}$$

~~WRONG~~

$$PF_{FWR} = \frac{\sqrt{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2}}{\frac{2V_m}{\pi}}$$

$$\frac{\sqrt{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2}}{\frac{2V_m}{\pi}} = \frac{\sqrt{\frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}}}{\frac{2V_m}{\pi}}$$

$$= \frac{\sqrt{V_m^2 \left(\frac{1}{2} - \frac{4}{\pi^2}\right)}}{\frac{2V_m}{\pi}} = \frac{V_m \sqrt{\left(\frac{1}{2} - \frac{4}{\pi^2}\right)} \times \frac{\pi}{2V_m}}$$

$$= \sqrt{\frac{1}{2} - \frac{4}{3.14^2}} \times \frac{3.14}{2} \Rightarrow 0.482130687$$

$$PF_{FWR} = 0.482$$

or,

$$PF_{FWR} = 48.2\%$$



For CT-FWR

$$\text{As, } \boxed{\frac{TUF_{CT-FWR}}{2} = \frac{TUF_{primary} + TUF_{secondary}}{2}} \quad \text{--- (1)}$$

$$\therefore TUF_{primary} = 2 \times TUF_{HWR} = 2 \times 0.287 = 0.574 \quad \text{--- (2)}$$

and

$$TUF_{secondary} = \frac{V_{DC} \cdot I_{DC}}{V_{rms} \cdot I_{m}} = \frac{2V_m}{\pi} \cdot \frac{2I_m}{\pi} = 0.911 \quad \text{--- (3)}$$

$$\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

Now, using eqⁿ (1) (2) & (3)

$$\therefore TUF_{CT-FWR} = \frac{0.574 + 0.911}{2} = 0.6925$$

$$\therefore \boxed{\frac{TUF_{CT-FWR}}{2} = 0.693}$$

$$\boxed{\frac{TUF_{CT-FWR}}{2} = 69.3\%}$$

For BT-FWR

$$\text{As, } T_{UF} \text{ BT-FWR} = \frac{V_{LDC} \cdot I_{LDC}}{V_{s,rms} \cdot I_{s,rms}} \left[\infty (R_s + R_f) \gg R_L \right]$$

$$\infty V_{LDC} = \frac{2V_m}{\pi}, \quad I_{LDC} = \frac{2I_m}{\pi}$$

$$V_{s,rms} = \frac{V_m}{\sqrt{2}}, \quad I_{s,rms} = \frac{I_m}{\sqrt{2}}$$

$$T_{UF} \text{ BT-FWR} = \frac{\frac{2V_m}{\pi} \cdot \frac{2I_m}{\pi}}{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}} = \frac{4V_m I_m}{\pi^2} = \frac{4}{\pi^2} = \frac{4}{2.14^2} = 0.811391942$$

$$\infty T_{UF} \text{ BT-FWR} = 0.811$$

or

$$T_{UF} \text{ BT-FWR} = 81.1\%$$

Peak Inverse Voltage (PIV)

It is the maximum reverse voltage across a diode with which a diode can withstand without damaging to the junction itself.

* For HWR -

$$PIV = V_m$$

* For CT-FWR -

$$PIV = 2V_m$$

* For BT-FWR -

$$PIV = V_m$$

Transformer Utilization Factor (TUF) :-

TUF indicates that "how well the input transformer is being utilized". It is defined as the ratio of D.C. Power available across the load to the ac power rating of the secondary coil of the transformer.

$TUF = \frac{\text{D.C. power available across the load}}{\text{a.c. power rating of secondary coil of the transformer}}$

$$TUF = \frac{V_{LDC} \cdot I_{LDC}}{V_{SRMS} \cdot I_{SRMS}} \quad \left[\text{As } (R_s + R_f) \ll R_L \right]$$

For HWR :-

$$\text{As } TUF_{HWR} = \frac{V_{LDC} \cdot I_{LDC}}{V_{SRMS} \cdot I_{SRMS}} \quad \left[\because (R_s + R_f) \ll R_L \right]$$

$$\because V_{LDC} = \frac{V_m}{\pi}, \quad I_{LDC} = \frac{I_m}{\pi}$$

$$= \frac{2\sqrt{2}}{\pi^2} = \frac{2\sqrt{2}}{3.14^2} = 0.286870372$$

$$* V_{SRMS} = \frac{V_m}{\sqrt{2}}, \quad I_{SRMS} = \frac{I_m}{2}$$

$$\therefore TUF_{HWR} = 0.287$$


or

$$\therefore TUF_{HWR} = \frac{\frac{V_m \cdot I_m}{\pi} \cdot \frac{I_m}{\pi}}{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{2}} = \frac{V_m I_m}{\pi^2} \cdot \frac{2\sqrt{2}}{V_m I_m}$$


$$TUF_{HWR} = 28.7\%$$

$$TUF_{HWR} = \frac{V_m I_m}{\pi^2} \times \frac{2\sqrt{2}}{V_m I_m} =$$

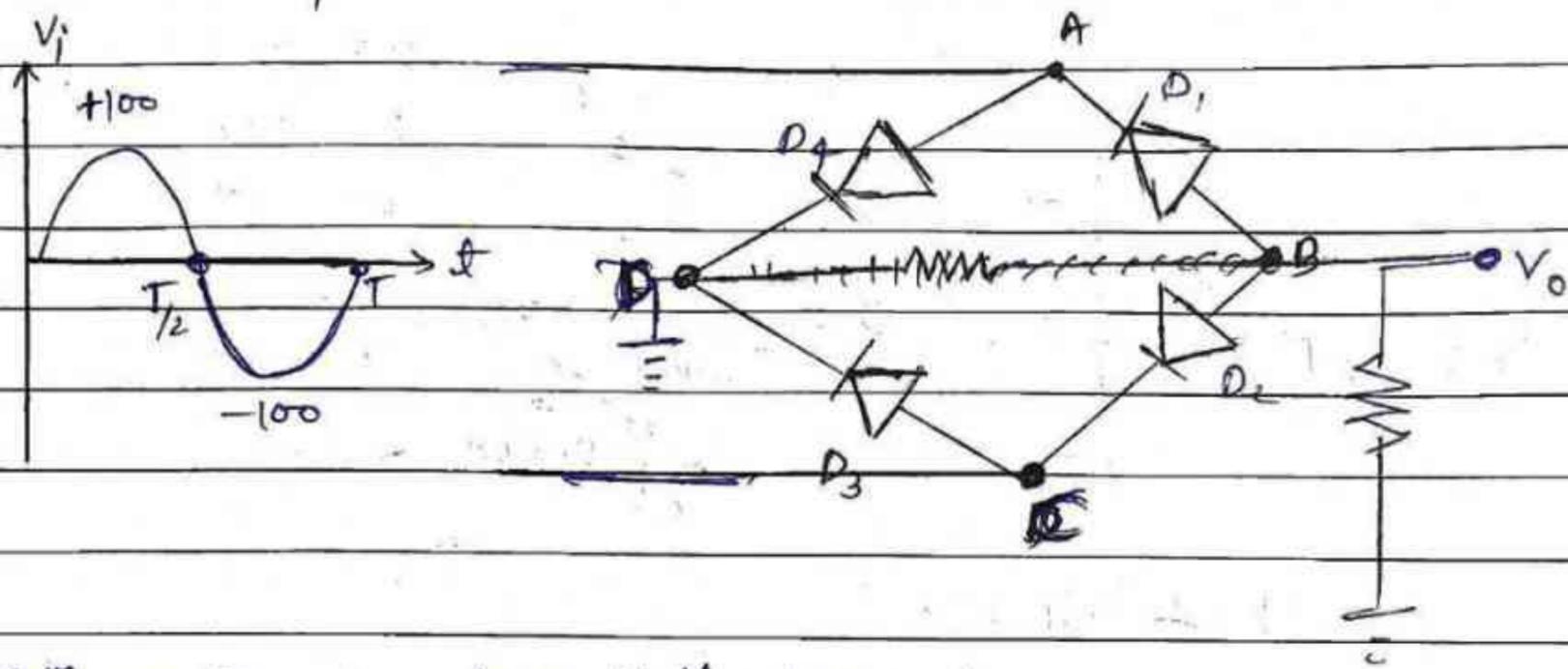Ques - Determine the output voltage and describe its output wave form :-



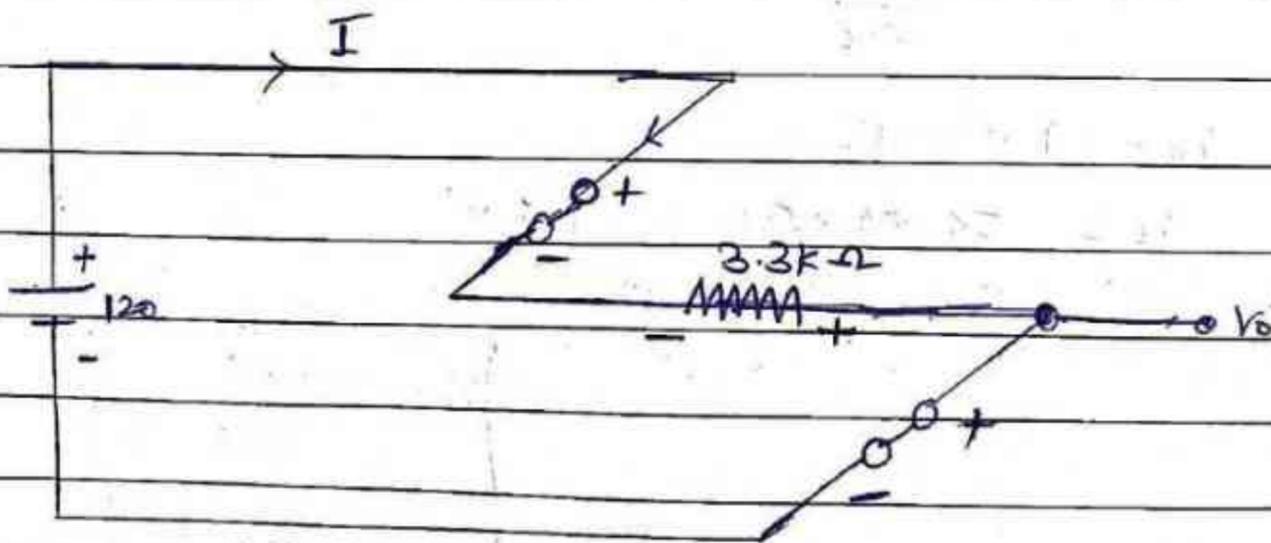... Solⁿ → During +ve Half ~~wave~~ cycle.



$$120 + 3.3I = 0$$

$$I = \frac{120}{3.3}$$

$$I = 30.3 \text{ mA}$$


$$\text{then } V_o = V_R = 3.3 \times I$$

$$3.3 \times 30.3$$

$$V_o = 99.99 \text{ V}$$

$$V_o \approx 100 \text{ V}$$

Case - II During -ve half cycle.

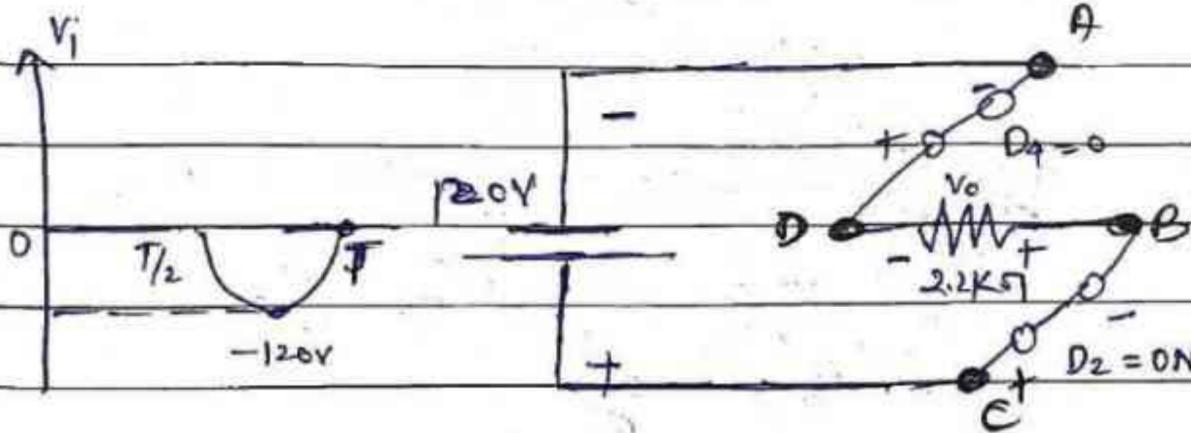

$$V_1 = -120V$$

$$D_1 = \text{OFF}$$

$$D_2 = \text{ON}$$

$$D_3 = \text{OFF}$$

$$D_4 = \text{ON}$$


$$120 + 2.2I = 0$$

$$2.2I = -120$$


$$I = \frac{-120}{2.2} = -54.54$$

$$V_0 = I \times 2.2k\Omega$$


$$V_0 = 54.54 \times 2.2 = 120V$$

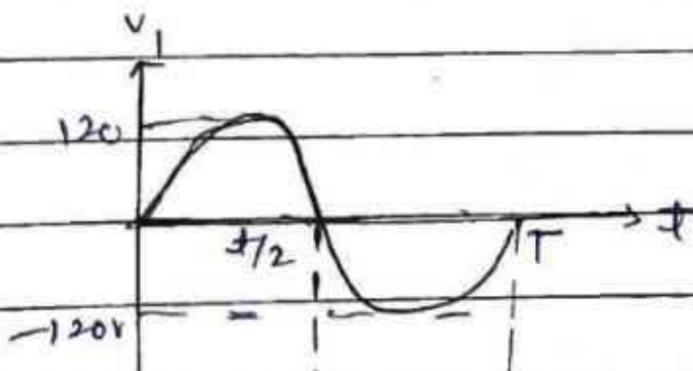


$$V_{0c} = \frac{290}{3.14} = 76.43$$

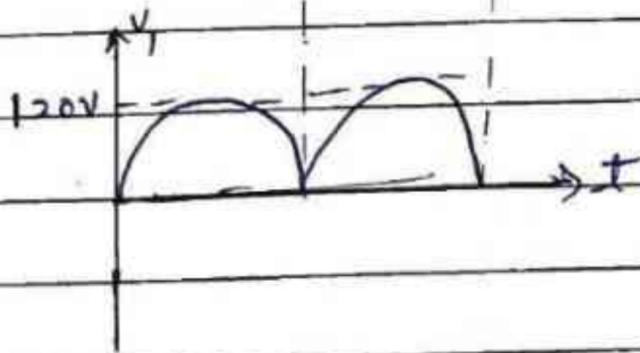

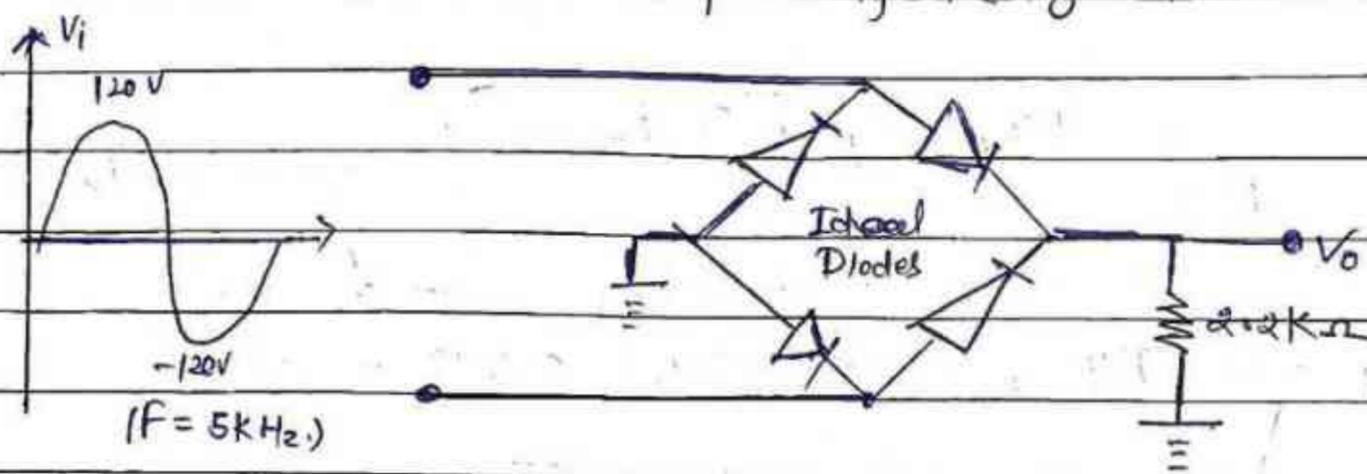Ques → Sketch the V_o waveform of the given circuit.



Solⁿ ⇒ Case I : During +ve Half Cycle :-

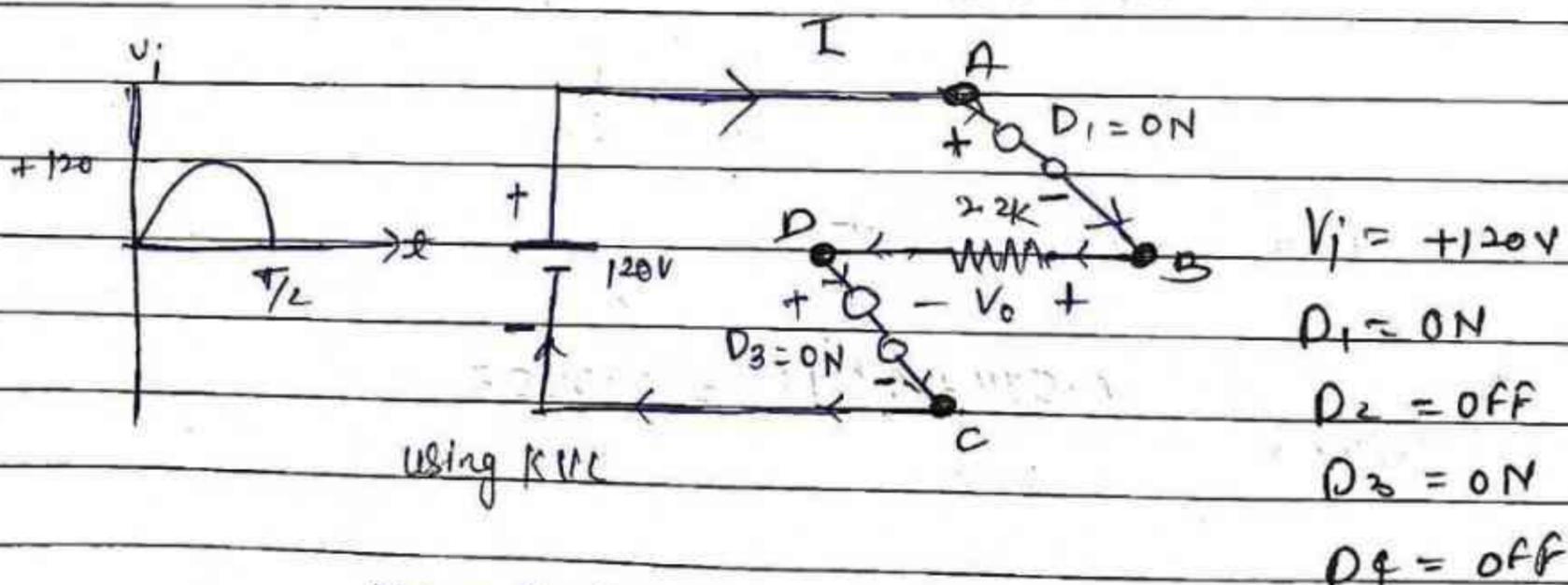

$$120 - 2.2I = 0$$


$$+ 2.2I = +120$$

$$I = \frac{120}{2.2} = 54.54 \text{ mA}$$

and

$$V_o = 2.2 \times I = 2.2 \times 54.54 = 120V$$

Case II During -ve Half cycle:-

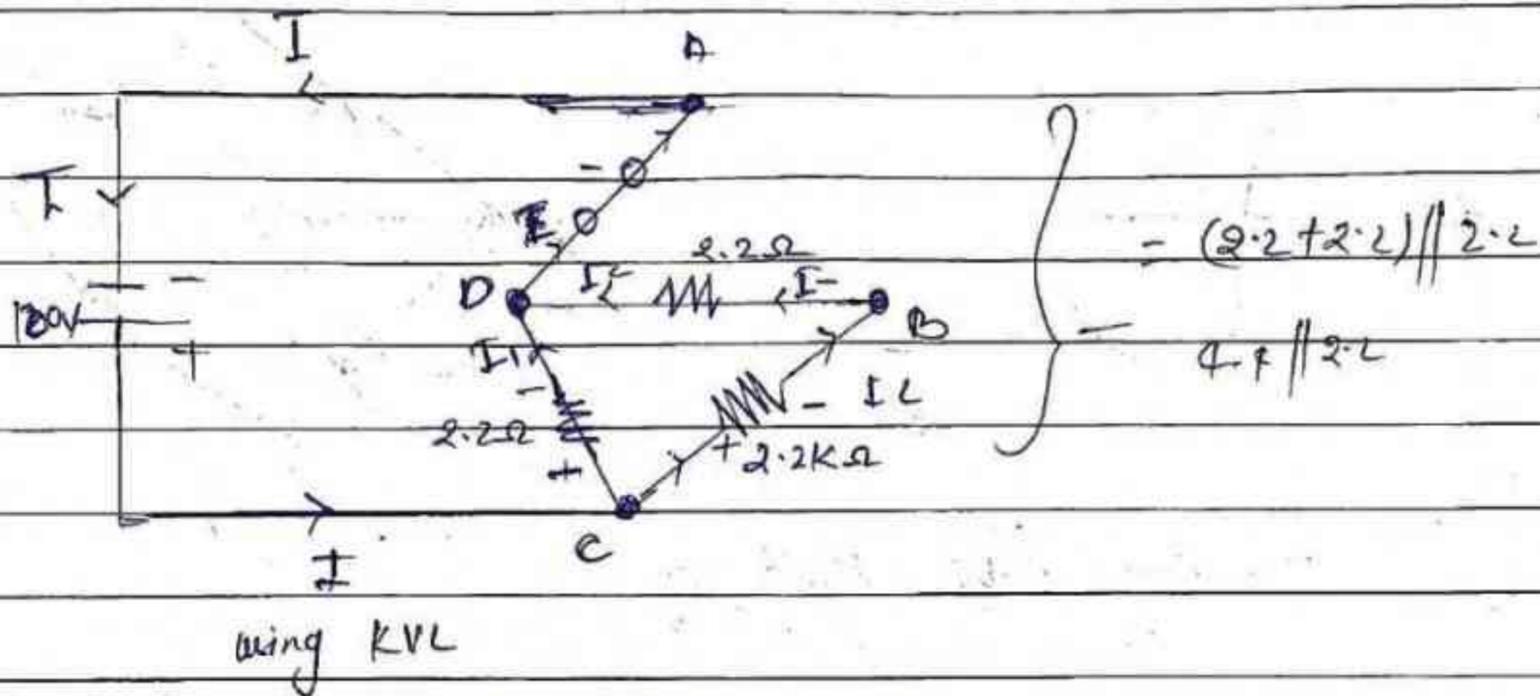

$$I = \frac{100}{1.46} = 68.49 \text{ mA}$$

using CDR


$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_2 = 9 \times 2.2$$


$$(4 \parallel 2.2 \times 2.2)$$

$$I_L = \frac{68.49 \times 2.2}{6.6} = 22.83 \text{ Am}$$

$$V_o = 50.226 \text{ V}$$

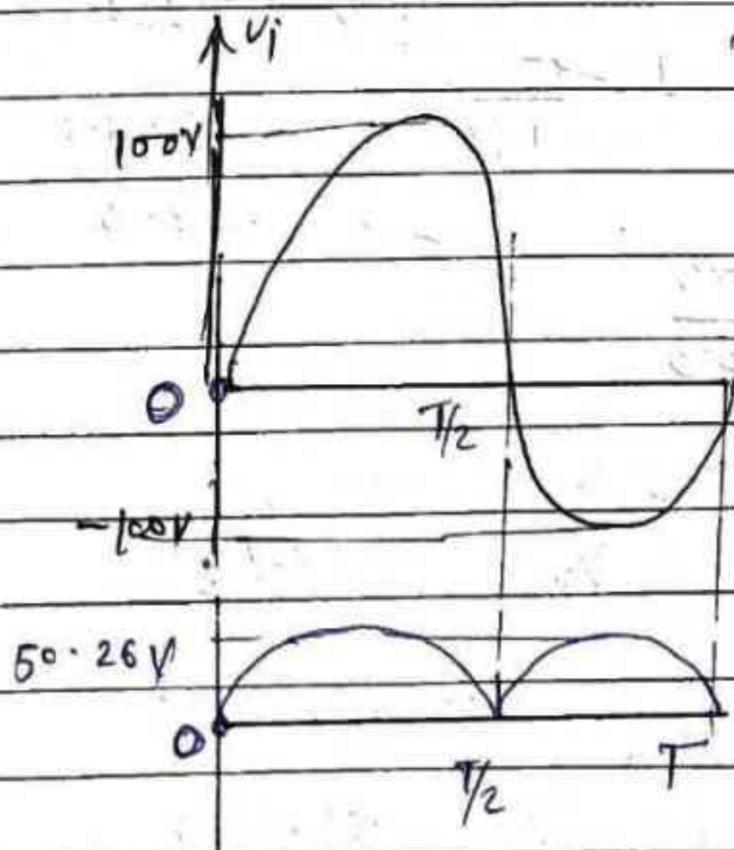


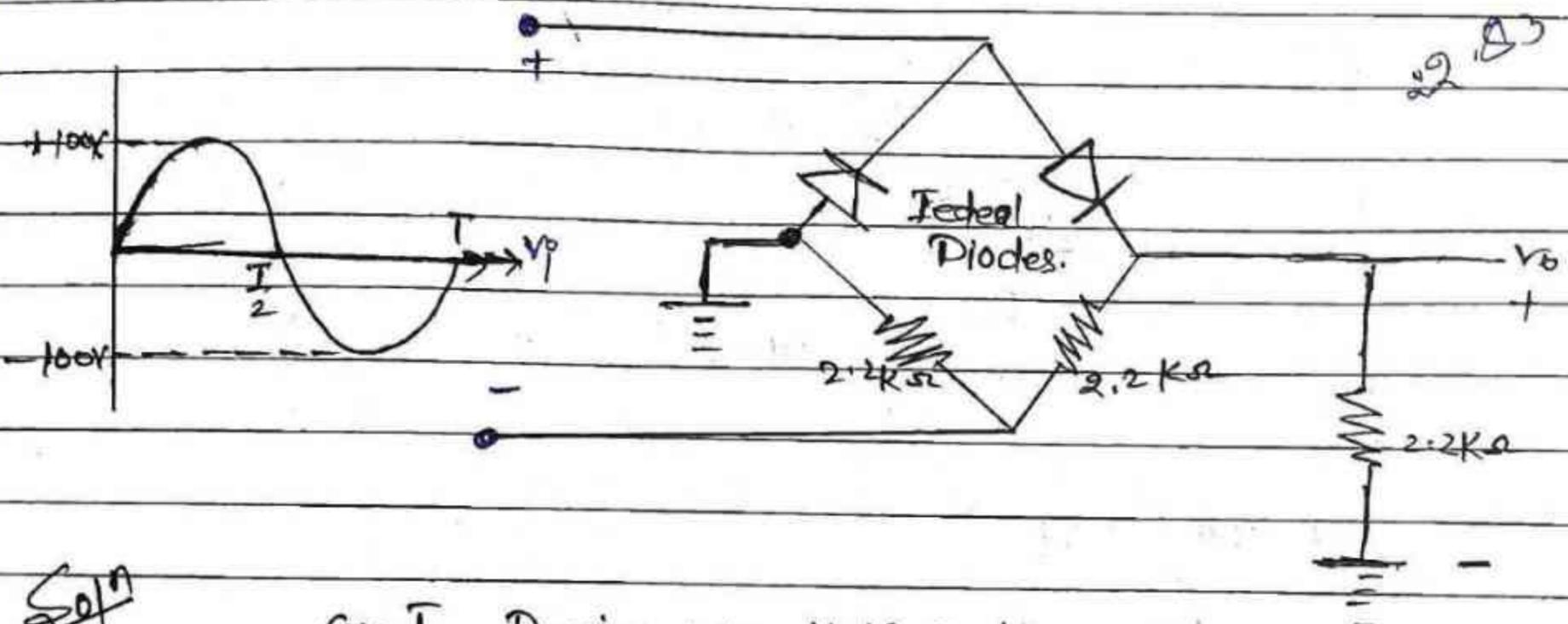Sketch the V_o waveform of the given network.



Soln

Case I During +ve Half Cycle

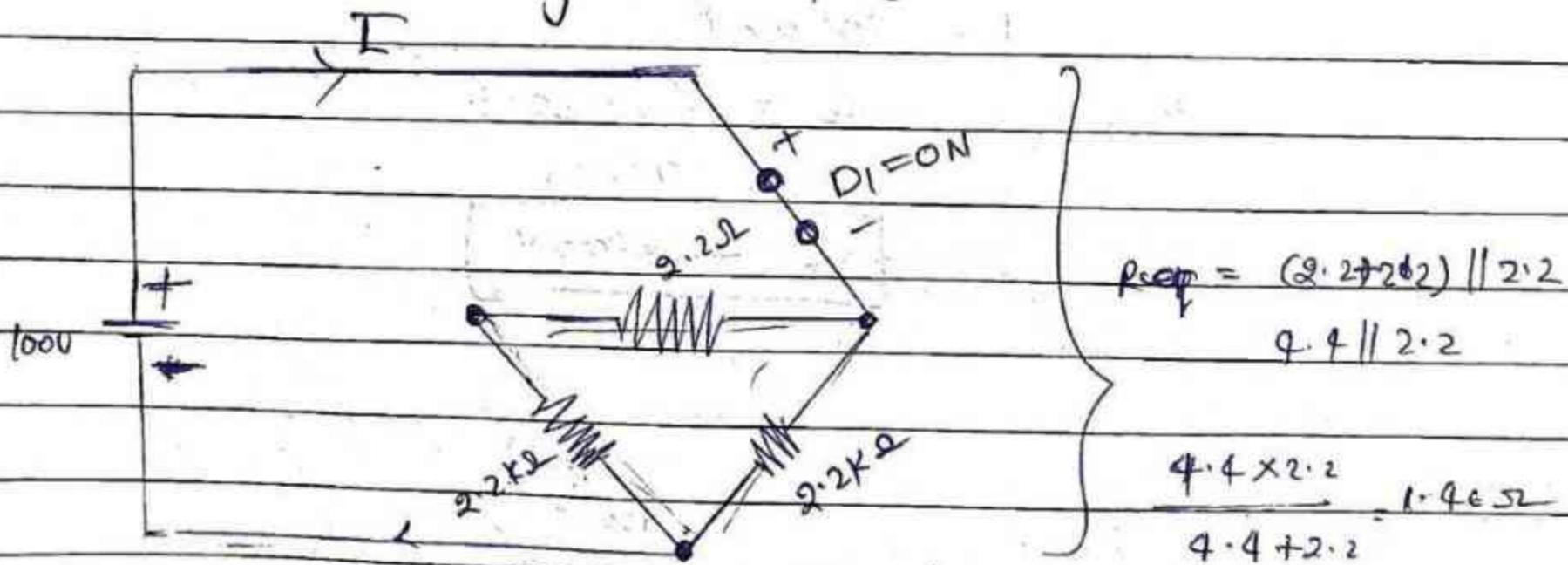

$$I = \frac{100}{1.46} = 68.49 \text{ mA}$$

using CDR


$$I_1 = I \times \frac{2.2}{(2.2 + 2.2 + 2.2)}$$

$$I_1 = 68.49 \times \frac{2.2}{6.6} = 22.83 \text{ mA}$$

$$V_o = 2.2 \times I_1 = 2.2 \times 22.83$$

$$V_o = 50.226 \text{ V}$$

Case II during -ve half cycle.

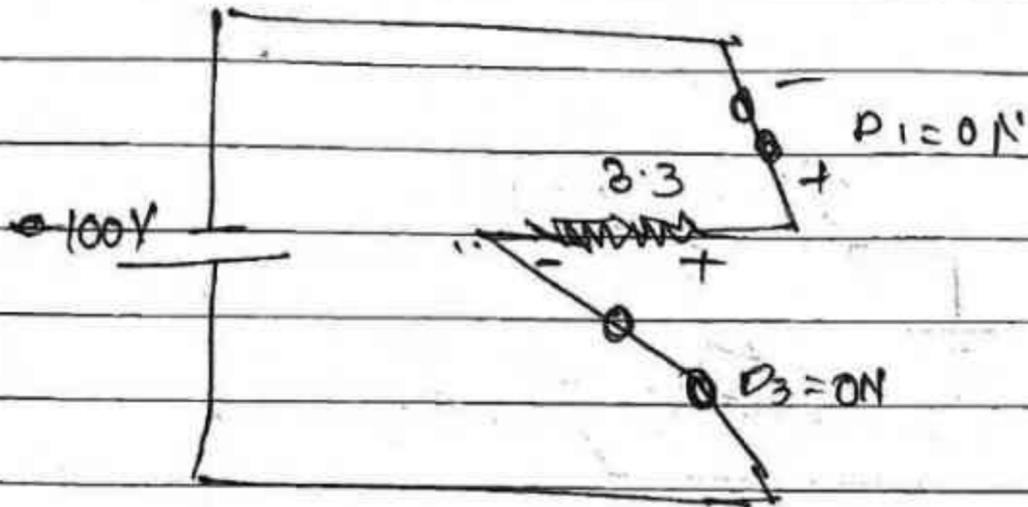

by using KVL


$$100 - 3.3I = 0$$

$$I = 30.3 \text{ mA}$$

$$\text{then } V_o = V_o = 3.3 \times 30.3$$

$$= 99.99$$

$$V_o \approx 100 \text{ V}$$

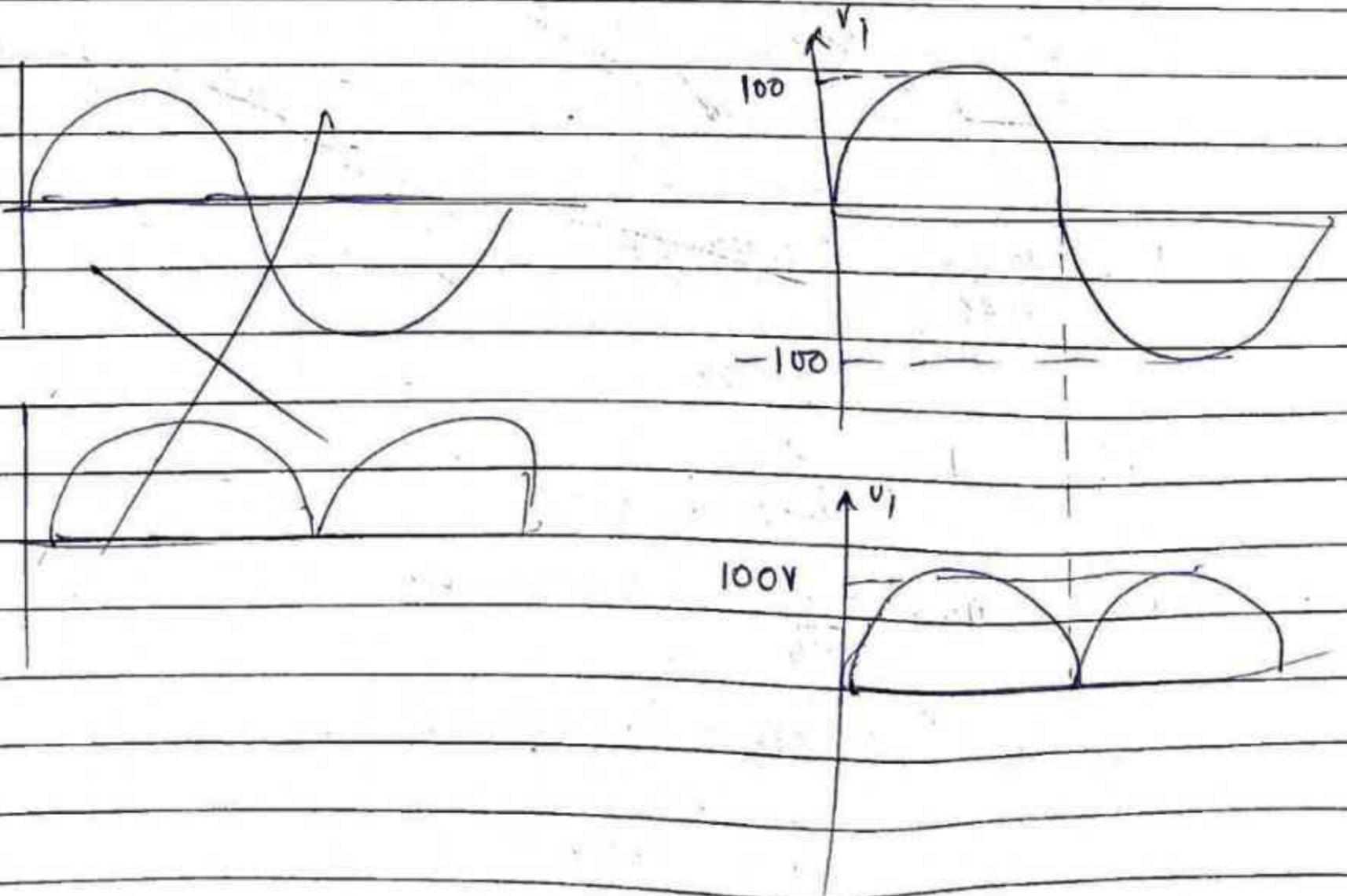

V_r Imp

Que :- In the bridge rectifier circuit, the secondary voltage

$$V_s = 100 \sin 50t \text{ and load resistance is } 1k\Omega$$

Calculate i) DC current ii) RMS value of current

iii) Efficiency (iv) Ripple factor. $\rightarrow 0.482$

$\rightarrow 0.811$

Solⁿ

$$V_m = I_m R_L$$

$$I_m = \frac{100}{1}$$

$$I_m = 100 \text{ mA}$$

$$(i) I_{DC} = \frac{2 \times 100}{3.14} = 63.69 \text{ mA}$$

$$(ii) R_{MS} = \frac{I_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71$$

$$(iii) \frac{I_{DC}^2 \times R_L}{I_{RMS}^2 \times R_L} = \frac{(63.69)^2 \times 1}{\frac{I_m^2}{2}} \Rightarrow \frac{(63.69)^2 \times \sqrt{2}}{100} \rightarrow \frac{5736.63}{100}$$

(iv)

$$\sqrt{V_{RMS}^2 - V_{DC}^2}$$

V_{DC}


$$\sqrt{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2} \Rightarrow \frac{2V_m}{\pi}$$

$$\sqrt{\frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}} \Rightarrow \frac{2V_m}{\pi}$$

$$\sqrt{V_m^2 \left(\frac{1}{2} - \frac{4}{\pi^2}\right)}$$

$$\frac{2V_m}{\pi}$$

Drawing @ -ve Half cycle.

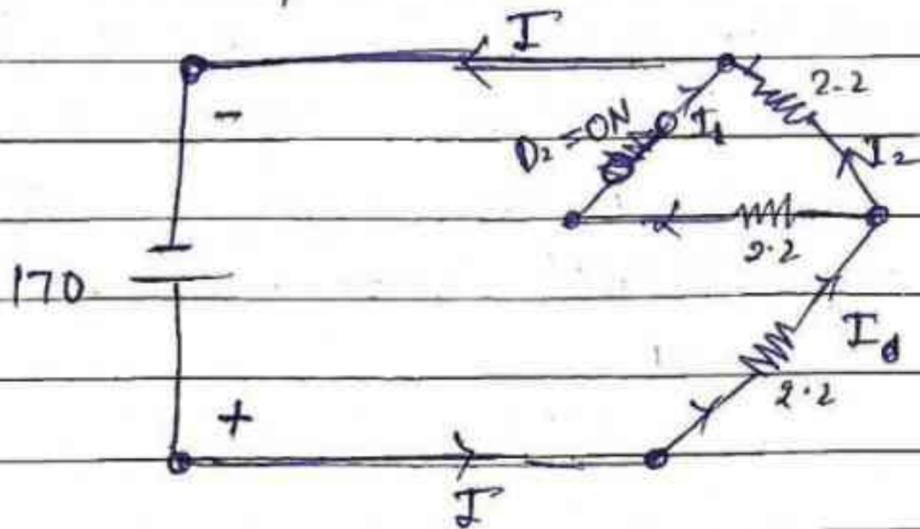

$$R_{eq} = 2.2 \parallel 2.2 + 2.2$$

$$\frac{2.2 \times 2.2}{2.2 + 2.2} + 2.2$$

$$1.1 + 2.2$$

$$R_{eq} = 3.3$$

$$I = \frac{170}{3.3} = 51.51$$

$$I_2 = \frac{51.51 \times 2.2}{(2.2 + 2.2)}$$

$$= \frac{51.51 \times 2.2}{4.4}$$

$$51.51 \times 0.5 = 25.755$$



$$I_2 = 25.755$$

$$V_0 = I_2 \times 2.2$$

$$= 25.755 \times 2.2$$

$$= 56.66 \text{ V}$$

Passing +ve half cycle -

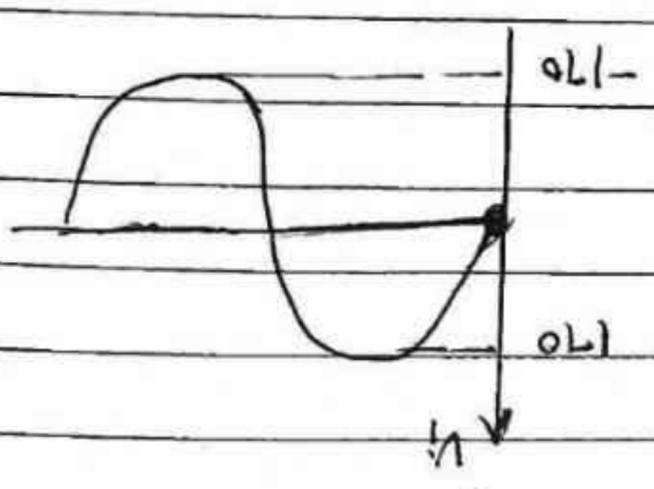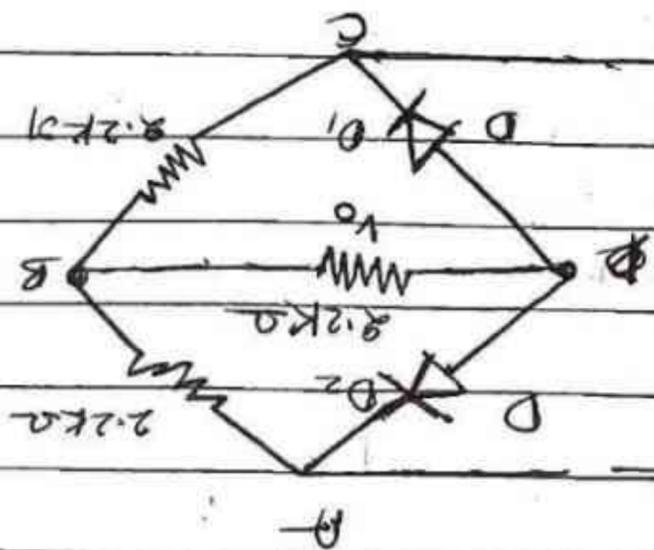

Soln


$$f_1 = \frac{51.51 \times 2.2}{(2.2 + 2.2)} = 25.755$$

$$V_0 = 2.2 \times f_1 = 56.611 \text{ V}$$

$$I_1 = \frac{116.43 \times 2.2}{3.3} = 77.42$$

$$I = \frac{170}{3.3} = 51.51$$

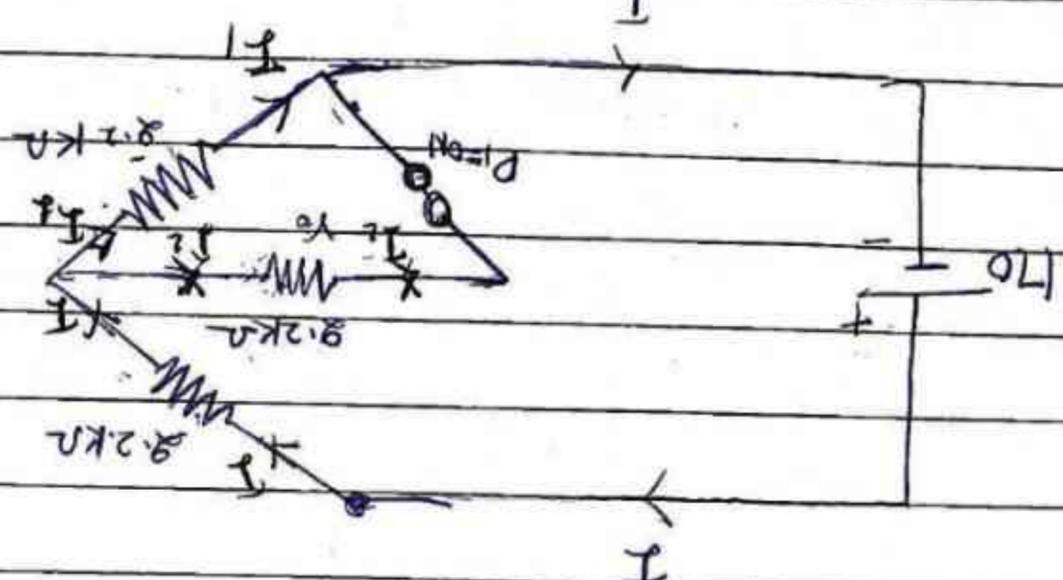$D_1 = \text{ON}$
 $D_2 = \text{OFF}$
 $V_1 = 170$



$$R_{eq} = 2.2 \parallel 2.2 = 1.1 \text{ k}\Omega$$

$$I = \frac{170}{1.1} = 154.54 \text{ A}$$

$$V_0 = 2.2 \times I = 340 \text{ V}$$

$$I = \frac{170}{3.3} = 51.51$$

$$V_0 = 2.2 \times I = 113.32 \text{ V}$$

$$= 3.3$$

$$= 6.6$$

$$2.2 \times 25.755$$

$$V_0 = 56.611 \text{ V}$$

$$= 25.755$$

$$51.51 \times 2.2$$

$$f_1 = \frac{51.51 \times 2.2}{(2.2 + 2.2)}$$

$$I_1 = \frac{116.43 \times 2.2}{3.3}$$


$D_2 = \text{OFF}$

$D_1 = \text{ON}$

$V_1 = 170$

I

Case-I During +ve Half cycle.

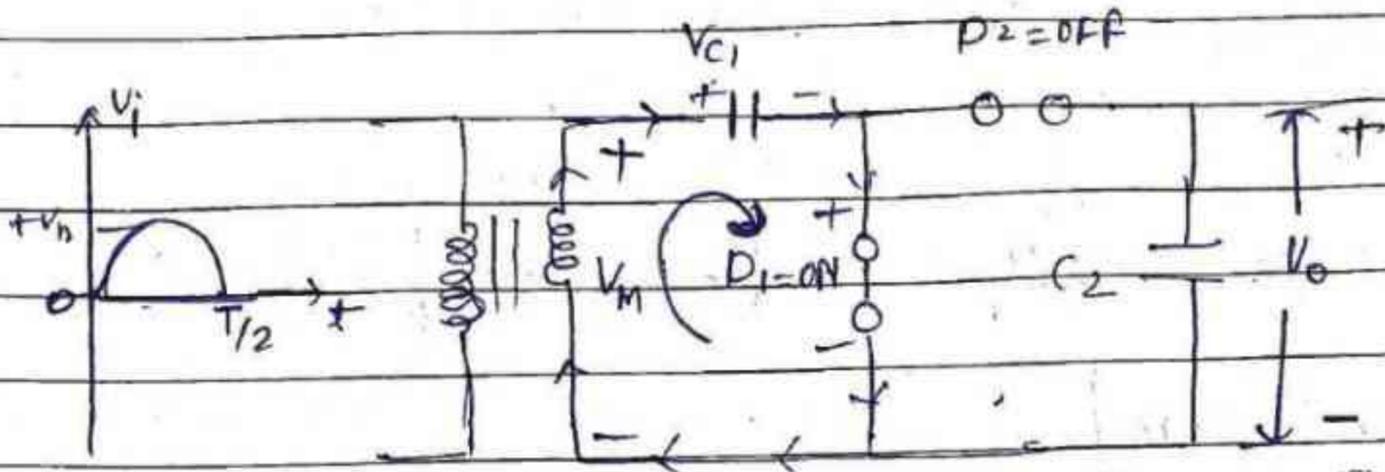

Using KVL

$$V_m - V_{c1} = 0$$


and

$$V_o = 0.V$$

$$+ V_{c1} = + V_m$$

$$\boxed{V_{c1} = V_m}$$

Case-II During -ve Half cycle.

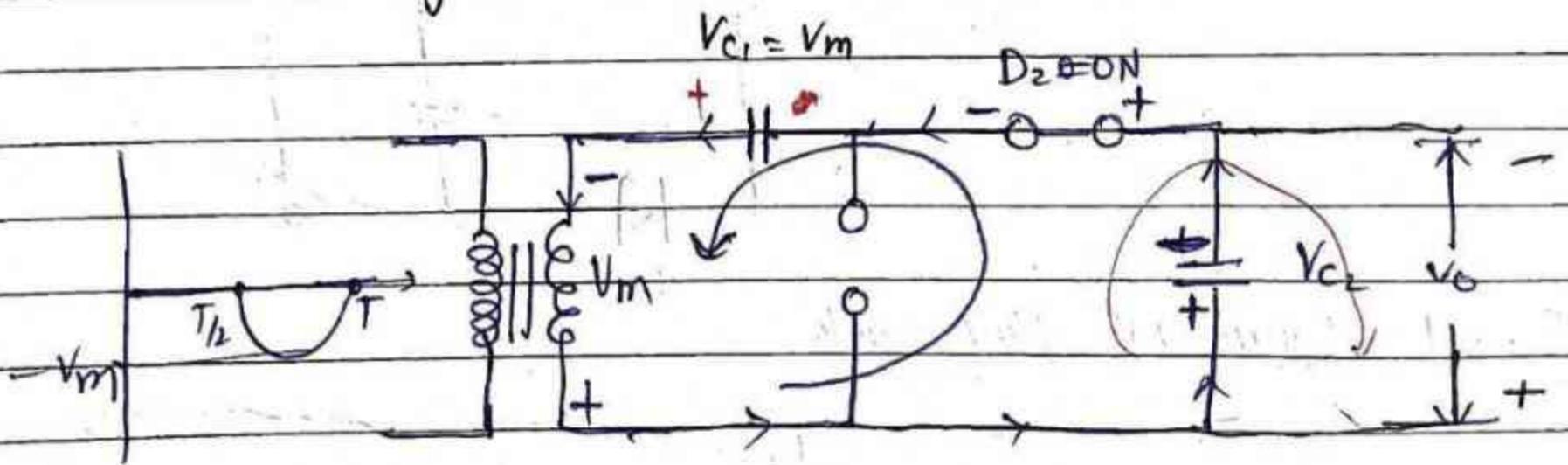

Using KVL

$$V_m - V_{c2} = 0$$

$$\boxed{V_{c2} = V_m}$$

$$V_m = V_{c2} + V_{c1}$$

$$\text{as } V_{c1} = V_m$$


$$2V_m = V_{c2}$$

$$V_o = V_{c2}$$

$$V_o = 2V_m$$

Voltage multiplier :-

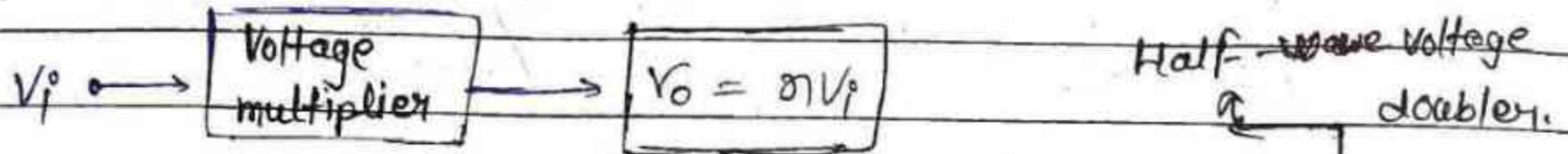A circuit is known as voltage multiplier, if its output voltage is proportional to n -times of applied input voltage.




* If $n = 2$ then $V_o = 2V_i \Rightarrow$ Voltage doubler

* If $n = 3$ then $V_o = 3V_i \Rightarrow$ Voltage tripler

* If $n = 4$ then $V_o = 4V_i \Rightarrow$ Voltage quadrupler

Voltage Doubler :-

(A) Half Wave Voltage Doubler (HWVD)

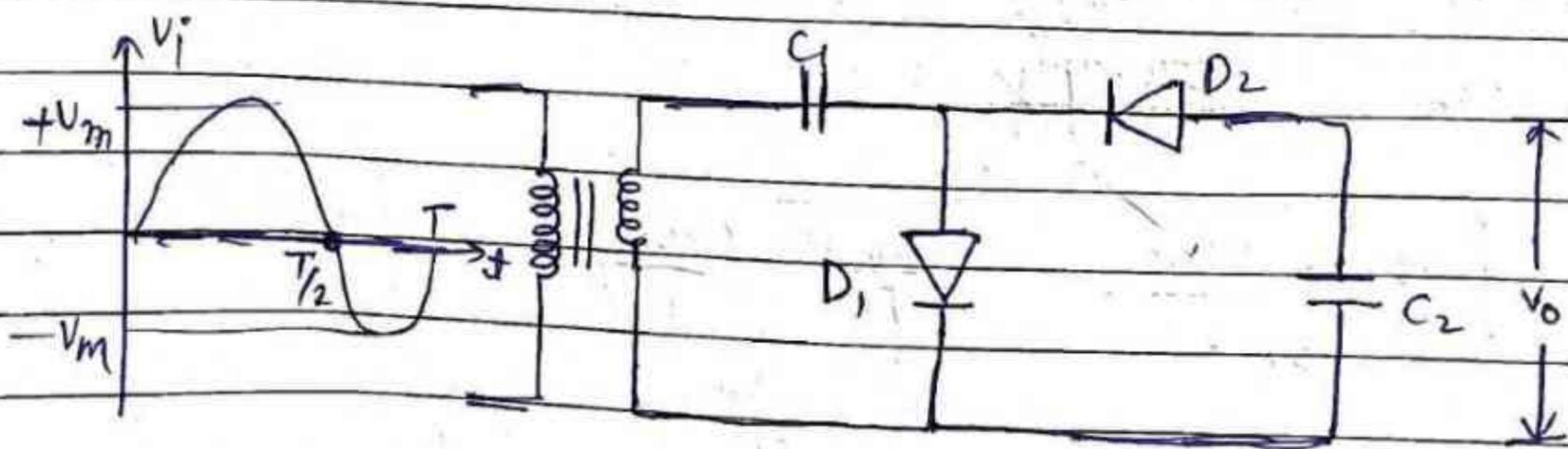

$$\frac{V_m \sqrt{\left(\frac{1}{2} - \frac{4}{\pi^2}\right)}}{\frac{2V_m}{\pi}}$$

$$\sqrt{\frac{1}{4} - \frac{4}{\pi^2}} \times \pi \Rightarrow \sqrt{\frac{1}{2} - \frac{4}{(3.14)^2}} \times 3.14$$

$$\frac{\sqrt{\frac{1}{2} - \frac{4}{\pi^2}} \times 3.14}{100} \Rightarrow \frac{\sqrt{\frac{1}{2} - \frac{4}{(3.14)^2}} \times 3.14}{100}$$

$$\frac{0.3064}{100} \times 3.14$$

$$R_F = 9.62 \Omega$$


Ans → Following

$$(iii) \frac{I_{DC}^2 \times R_L}{I_{RMS}^2 \times R_L} \Rightarrow \frac{(63.69)^2}{(70.71)^2} \Rightarrow 0.811$$

$$(iv) R.F = \frac{V_{RMS}^2 - V_{DC}^2}{V_{DC}^2} = \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2}{\frac{2V_m}{\pi}} = \frac{\left(\frac{100}{\sqrt{2}}\right)^2 - \left(\frac{200}{3.14}\right)^2}{\frac{200}{3.14}}$$

$$\frac{\frac{10000}{2} - \frac{40000}{9.85}}{\frac{200}{3.14}}$$

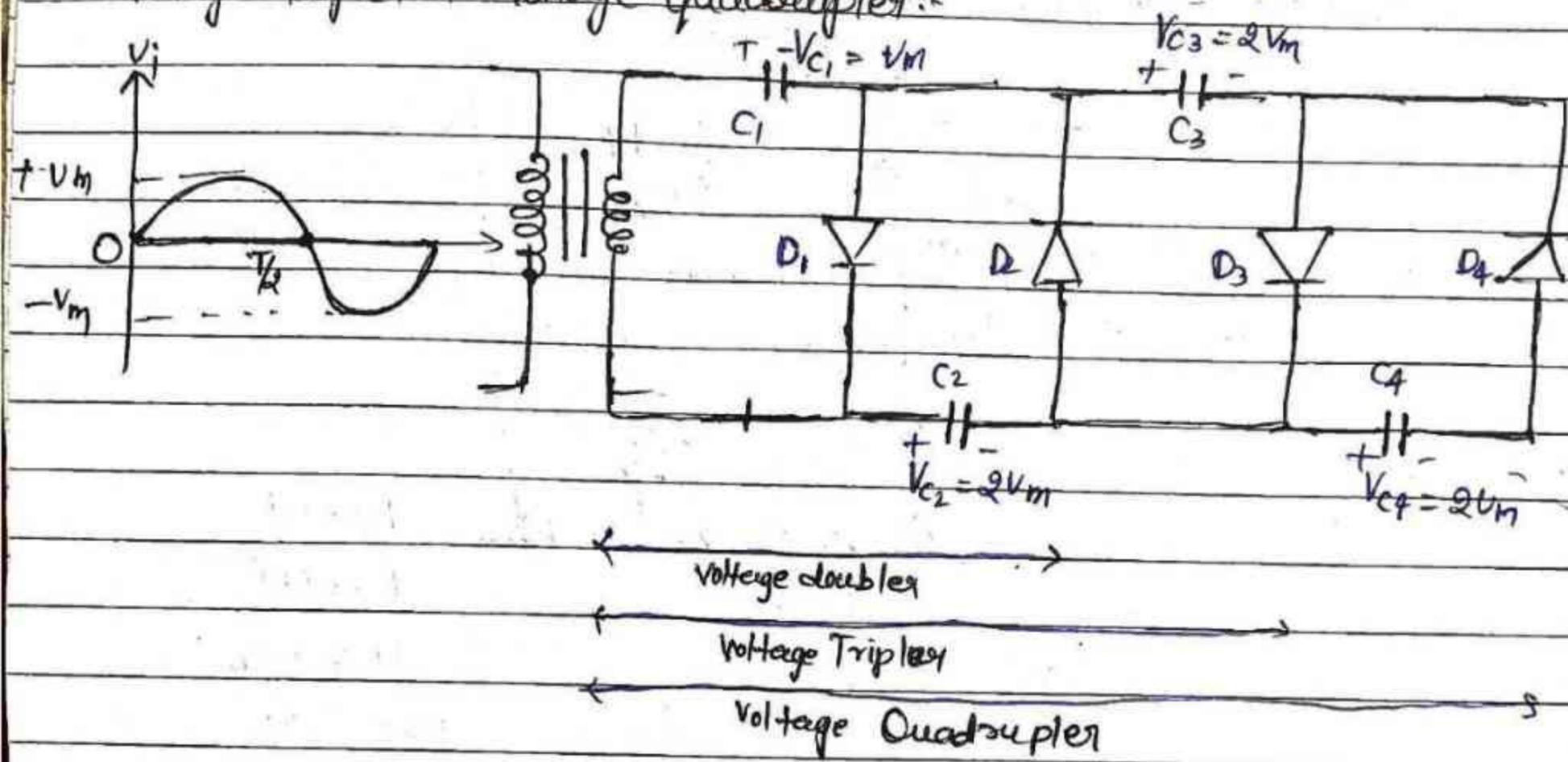* Voltage Tripler + Voltage quadrupler :-



* Working

During the $+$ ve half cycle, Diode (D_1) conducts (forwards) and the capacitor (C_1) charges up to V_m Due to the transformer secondary voltage ($+V_m$). And During the $-$ ve half cycle, Diode (D_2) conducts and the capacitor C_2 charges up to $2V_m$. Due to the transformer secondary voltage (V_m). And V_{C_1}

During the $+$ ve half cycle, Diode D_3 conducts and the capacitor C_3 charges up to $2V_m$ due to V_{C_2} . and during the negative half cycle, Diode D_4 conducts and the capacitor C_4 charges up to $2V_m$ due to the V_{C_3}

* Voltage Doubler

$$V_o = V_{C_2}$$

$$V_o = 2V_m$$

* Voltage Tripler

$$V_o = V_{C_1} + V_{C_3}$$

$$V_o = V_m + 2V_m$$

$$V_o = 3V_m$$


* Voltage Quadrupler

$$V_o = V_{C_2} + V_{C_4}$$

$$V_o = 2V_m + 2V_m$$

$$V_o = 4V_m$$

During +ve Half cycle -

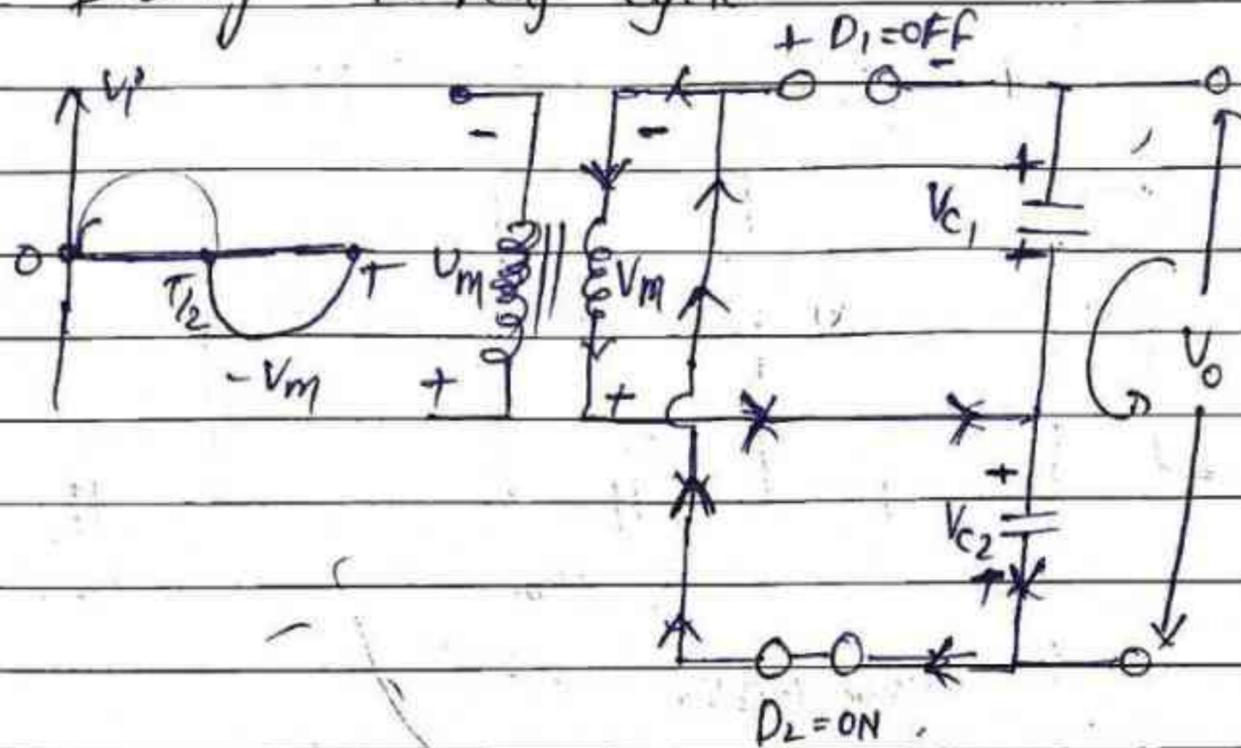

$D_2 = ON$

$D_1 = OFF$

$V_1 = -V_m$

using KVL

~~$$+V_m - V_{c2} + V_{c1} = 0$$~~

~~$$V_m + V_m = V_{c2}$$~~

~~$$2V_m = V_{c2}$$~~

~~$$-V_{c2} + V_{c1} + V_o = 0$$~~

~~$$V_o = V_{c2} - V_{c1}$$~~

~~$$V_o = 2V_m - V_m$$~~

~~$$V_o = V_m$$~~

using KVL

$$+V_m - V_{c2} = 0$$

$$V_{c2} = V_m$$

$$V_o = V_{c1} + V_{c2}$$

$$\therefore V_{c1} = V_m$$

$$V_{c2} = V_m$$

$$V_o = 2V_m$$

using KVL

and

$$V_m - V_{c2} + V_{c1} = 0$$

$$\therefore V_{c2} = V_m$$

$$V_m - V_{c2} + V_m = 0$$

$$\boxed{V_{c2} = 2V_m}$$


$$-V_{c2} + V_o = 0$$

$$V_o = V_{c2}$$


$$\therefore V_{c2} = 2V_m$$

$$\boxed{V_o = 2V_m}$$

Ⓑ Full wave voltage doubler (FWVD):

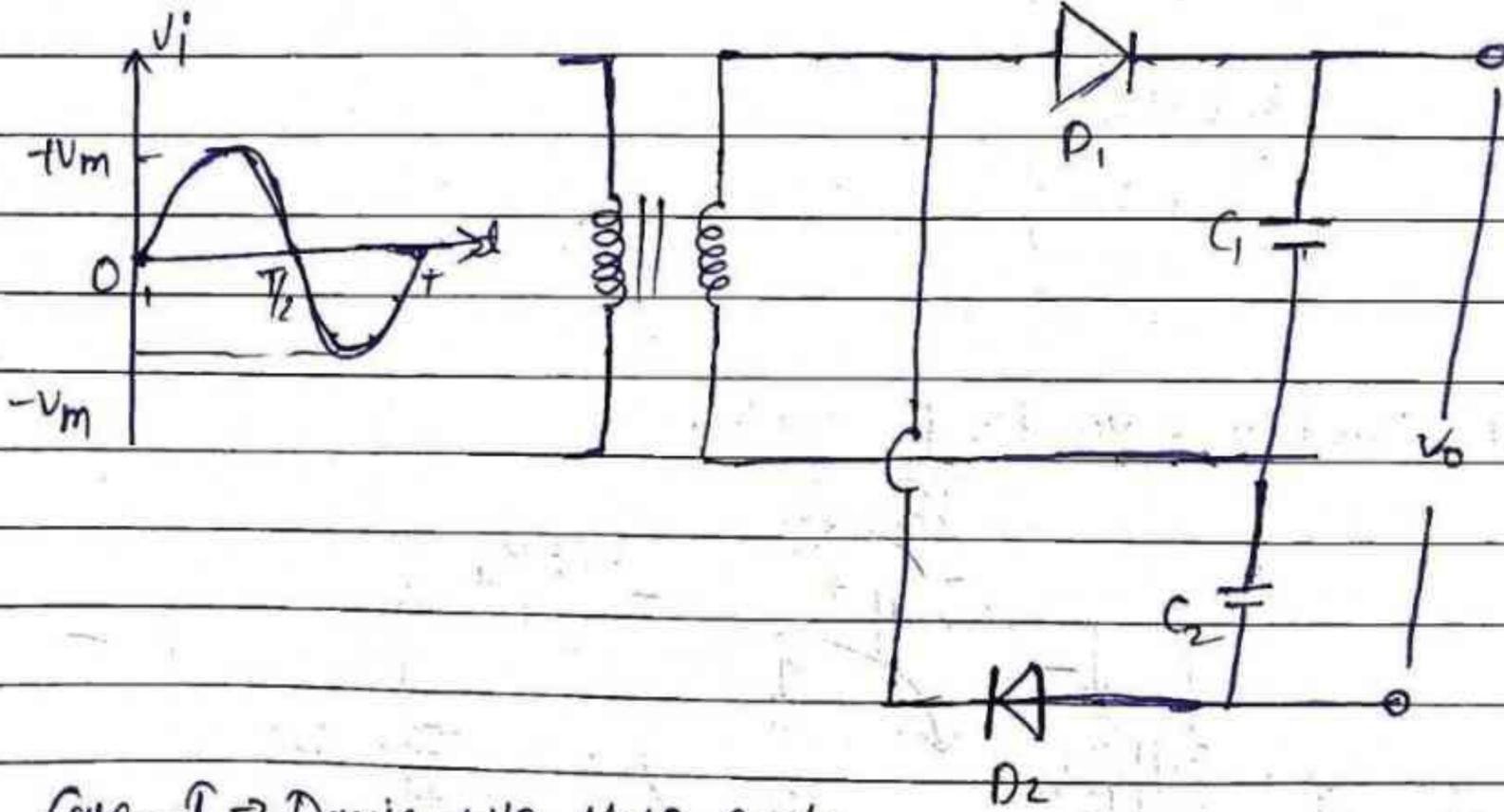

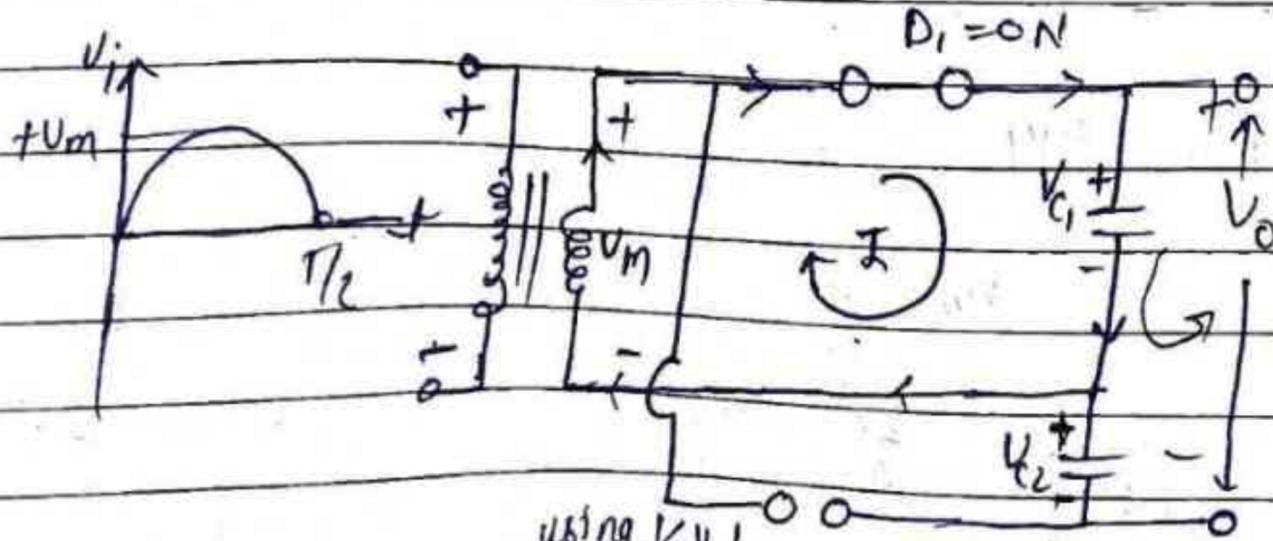Case - I \rightarrow During +ve Half Cycle



$D_1 = ON$
 $V_1 = +V_m$
 $D_2 = off$

and $V_o = V_{c1} + V_{c2}$


$\therefore V_{c1} = V_m$
 $V_{c2} = 0$

using KVL
 $V_m - V_{c1} = 0$

$$\boxed{V_{c1} = V_m}$$

~~$$\boxed{V_o = 0}$$~~

$$\therefore \boxed{V_o = V_m}$$

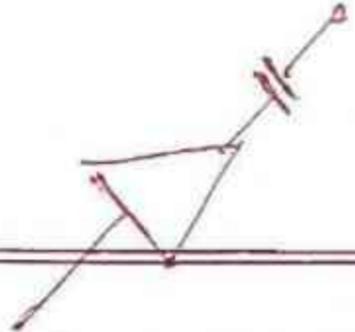

* Varactor Diode or Varicap Diode :- These diodes are semiconductor, voltage dependent and voltage variable capacitor diode.

Varactor Diode is also known as varicap Diode because its internal capacitance varies with respect to change in reverse bias voltage.



OR



OR

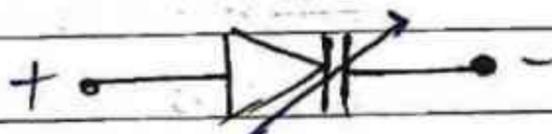


Fig. Symbol

The mode of operation depends upon the capacitance that exists when the element is reverse biased.

Under reverse bias condition, the transition capacitance is observed it is denoted by C_T and is approximately given by $C_T =$

$$C_T = \frac{K}{(V_K + V_R)^n}$$

where, $K = \text{constant}$

$V_K = \text{Knee Voltage}$

$V_R = \text{Reverse bias voltage}$

$n = \frac{1}{2}$ (for alloy junction)

$\frac{1}{3}$ (for diffused junction)

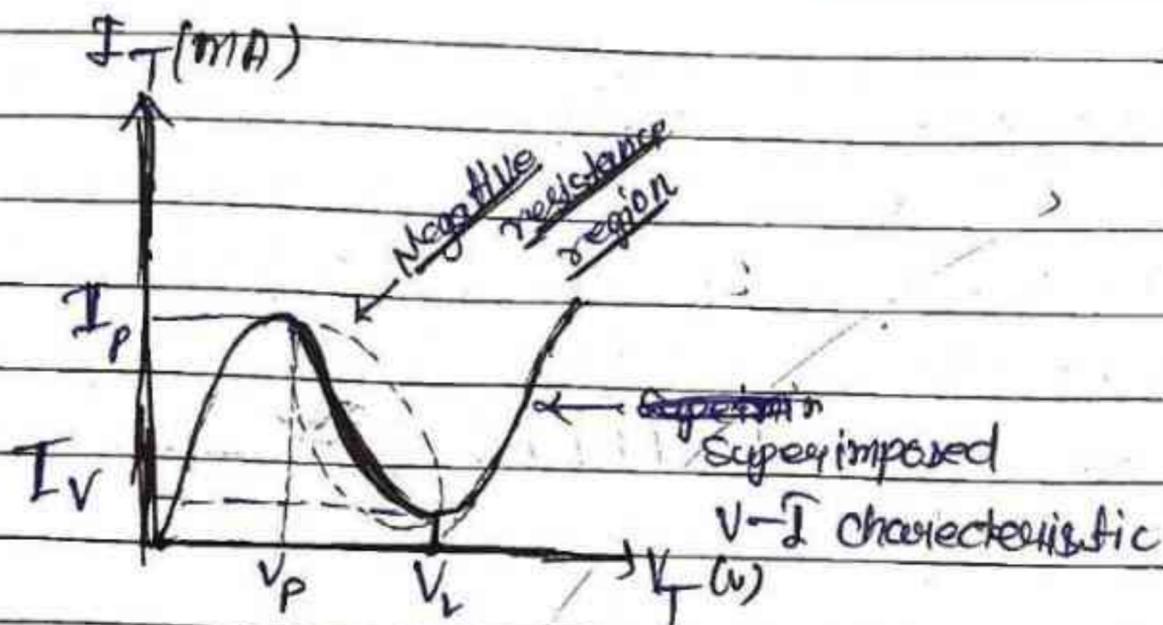


Fig:- V-I Characteristic of Tunnel Diode.

Advantages of Tunnel Diode :-

- ① - It operates at a very high switching speed.
- ② It is easy operate
- ③ It has low power ~~D.E~~ dissipation

Disadvantage of Tunnel Diodes.

- ① Limited Voltage range.
- ② Limited Current capacity
- ③ It is sensitive to temp^r changes.

Applications of Tunnel Diodes.

- ① It is use as very fast switching device in computer.
- ② In High frequency oscillators
- ③ In ~~Amplifiers~~ Amplifiers.

Special Purpose Diodes :-

- Tunnel Diode
- Varactor Diode
- Light Emitting Diode (LED)
- Photo diode.

* Tunnel Diode :- The Tunnel diode was first introduced by "Leo Esaki". It has a negative resistance region. i.e. and increase in terminal voltage ~~it~~ will cause a reduction in the diode current.

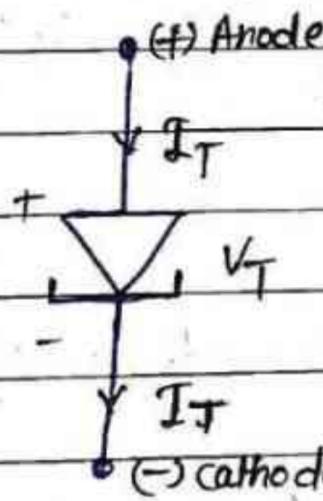


Fig - Symbol of Tunnel diode

The Tunnel Diode is fabricated by doping the semiconductor material that will form p-n junction at a level ~~too~~ hundred to thousand times more than the doping level of a typical semiconductor diode. As a result the width of a depletion region will greatly reduced of the order of $(\frac{1}{100})$ times the width of a typical semiconductor diode.

The Tunnel Diode Negative resistance region lies b/w 0.1 Volt and 0.3 Volt

The main semiconductor material used for the manufacturing use to manufactured LEDs are

- i) Aluminium, gallium, indium, phosphide, alloy. (Al, Ga, In, P) (V.O.R) - Colour
- ii) Indium, gallium, nitride, alloy. (In, Ga, N) (B.G. U.V.) - Colour
- iii) Aluminium gallium, arsenide (Al, Ga, As) (R.I.R.) - Colour

- (Al, Ga, In, P) are used to operate yellow, orange and red high brightness LEDs.
- InGaN-Alloy are used to obtain blue, green, ultra violet high brightness LEDs and
- AlGaAs are used to obtain red and infrared brightness LEDs.

The voltage drop across a conducting LED is 1.2V to 1.3V


Advantages of LED: LED = 

- i) Small size and light weight.
- ii) They are available in different spectral colours.

Disadvantage of LED:- (i) Over ~~more~~ current may damage it easily.
(ii) Blue colour LED may be harmful for eyes.

Application of LEDs-

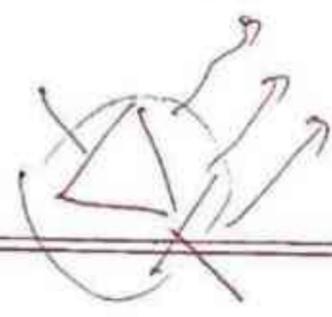- ① In seven-segment display
- ② In digital watches.
- ③ In camera flashes.
- ④ In Traffic light
- ⑤ In optocouplers.



* Lighting Emitting Diode (LED) :-

An LED is used to convert electrical signal into visible light. An LED emits lights when an electrical signal is applied to it. For proper operation of LED, it is necessary to forward bias it.

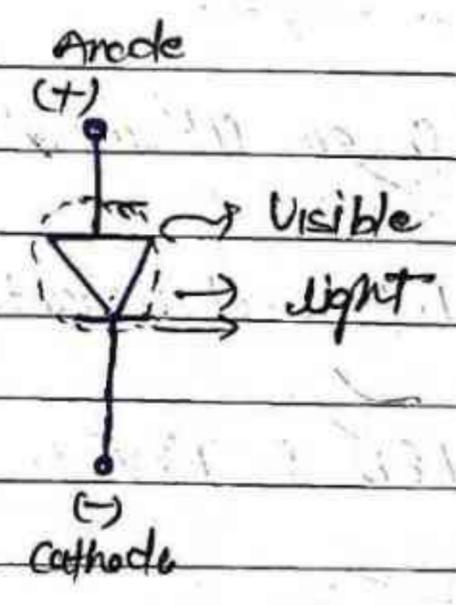


Fig:- Symbol of LED

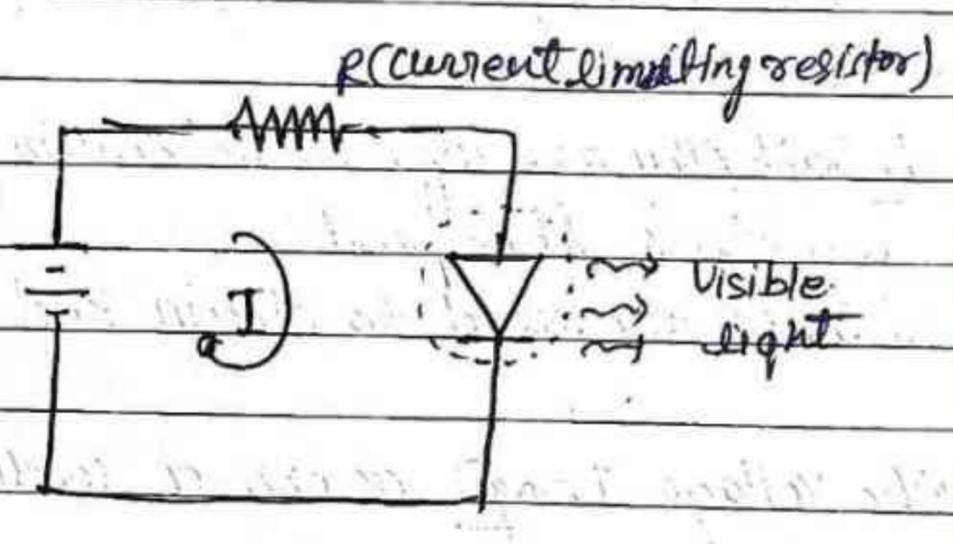


Fig:- Forward biasing of LED

LEDs works on the principle of Electroluminescence (ie. the generation of light through and electrical operation) on passing current through the diode, the majority charge carriers and the minority charge carriers recombine at the junction. On recombination, the energy is released in terms of photons.


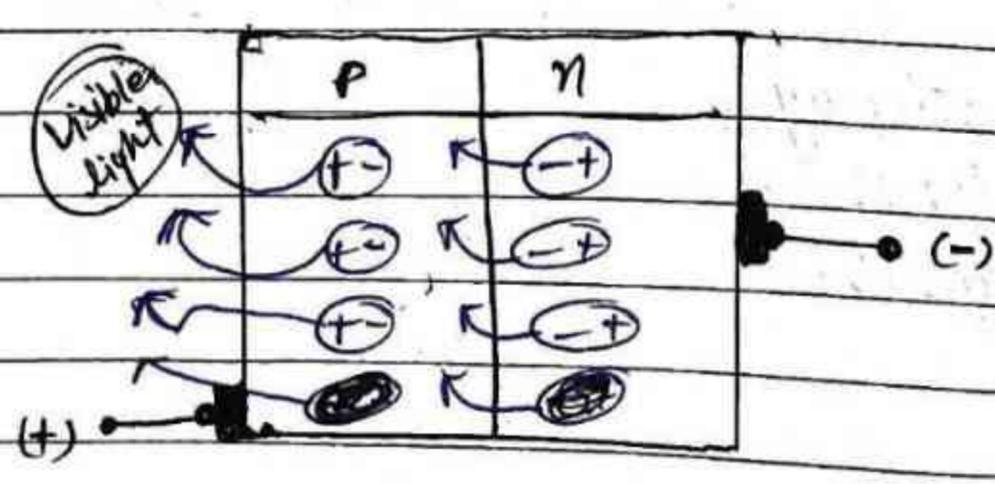


Fig:- Process of Electroluminescence in LED

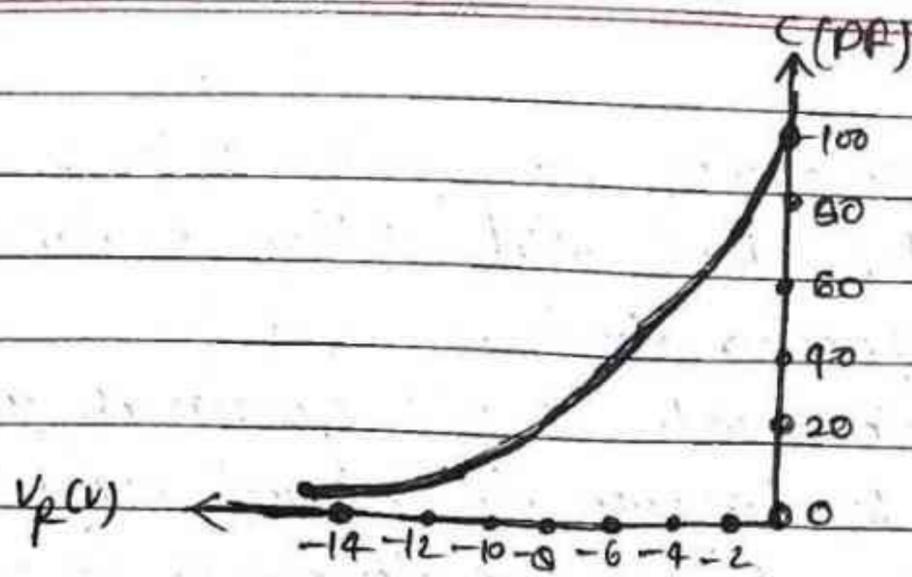

$$As, \left[C_T = \frac{\epsilon A}{W} \right]$$

Fig:- Capacitance V_s Reverse bias voltage across a varactor diode

Advantages of Varactor diodes :- ① low cost ② Portability ③ Reliability

Disadvantage of Varactor diode :- ① Varactor diode is specially designed to work in reverse biased mode.

Applications of Varactor Diodes :-

- i) In radio frequency circuit (RF)
- ii) In voltage controlled oscillator (VCO)
- iii) In FM generation.

Advantage of photo diode:-

- 1) High frequency response
It can be use as variable resistance device.
It has lower noise

Disadvantages :-

① It has rapid increases in dark current with change in temperature.

② It has small active area.

Application of photo diode :-

① In Barcode Scanners.

② In optical Fiber Communication

③ In smoke detector

④ In Solar panel.

The characteristic of the photo diodes are:-

(A) Quantum Efficiency (η):- As the Quantum efficiency is:

$$\eta = \frac{I_p \cdot h\nu}{q \cdot P_{op}}$$

Where.

I_p = photo current

$h\nu$ = photo energy

q = free electronic charge

P_{op} = optical incident power.

(B) Responsivity (R):- As the property is

$$R = \frac{I_p}{P_{op}} \quad \text{--- (1)}$$

$$\therefore \eta = \frac{I_p \cdot h\nu}{q \cdot P_{op}}$$

$$\therefore \frac{I_p}{P_{op}} = \frac{\eta \cdot q}{h\nu} \quad \text{--- (2)}$$

Using eqn (1) and (2)

$$R = \frac{\eta \cdot q}{h\nu}$$

photo diode can be operated in photo
conductive mode and photo voltaic mode.

Photo Diode

Photo Diode :- Basically Photo diodes are efficient light detector's. The working function of photo diode is just opposite to the working function of LED. In the sense that photo diode converts lights into electrical signal.

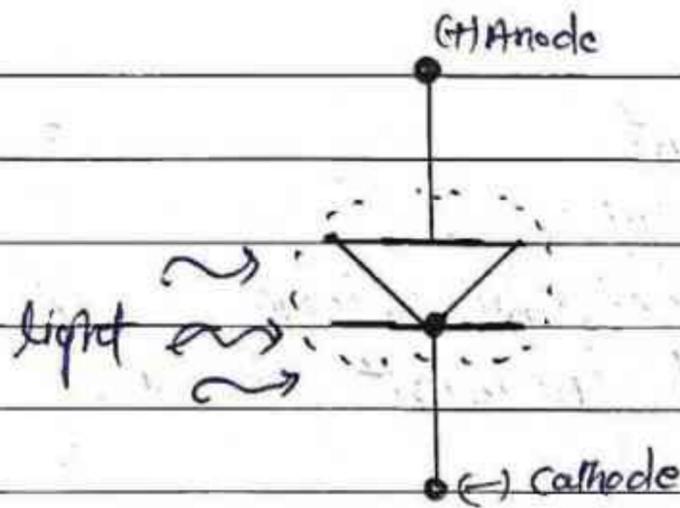




Fig:- Symbol of photo diode.

Photo diodes are manufactured by using semiconductor materials such as silicon, Germanium and Indium gallium arsenide usually, there are various types of photo diode such as.


- (i) p-n photo diode
- (ii) p-i-n photo diode
- (iii) Schottky photo diode
- (iv) Avalanche photo diode.

This types of photo diodes provides the following features and are usually used for the detection of existence of intensity, position and color of the light.


Waveform:

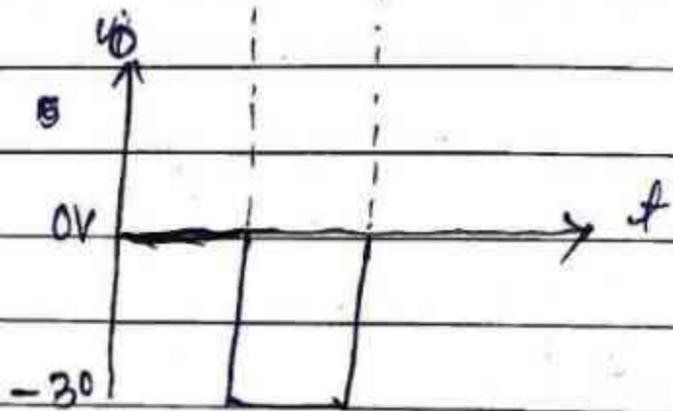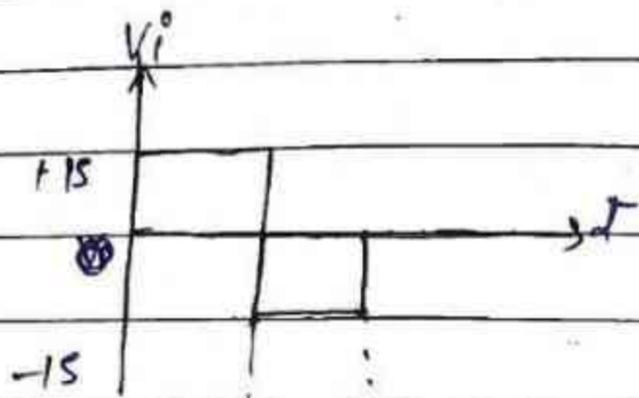

Ques:-

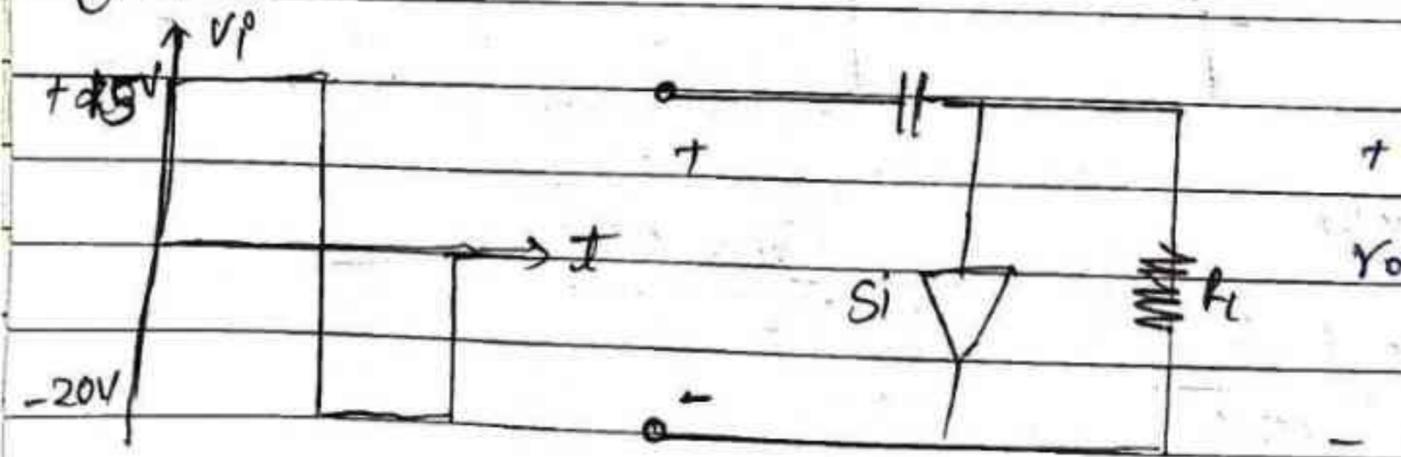

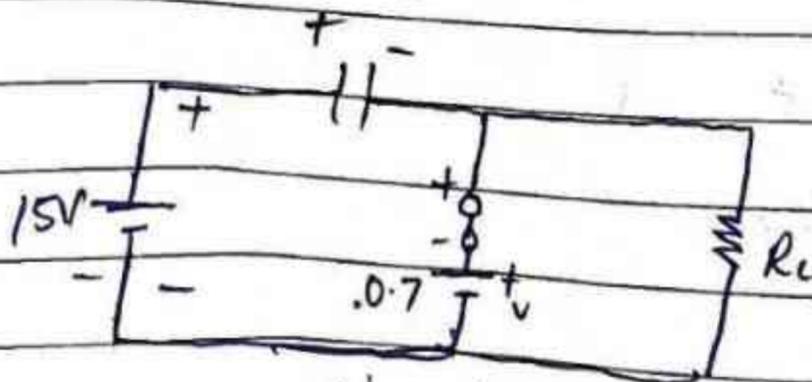Case I \rightarrow During $+15$ half cycle



using KVL


$$15 + V_o - 0.7 = 0$$

$$\boxed{V_o = 14.3}$$


$$-0.7 + V_o = 0$$

$$\boxed{V_o = 0.7}$$

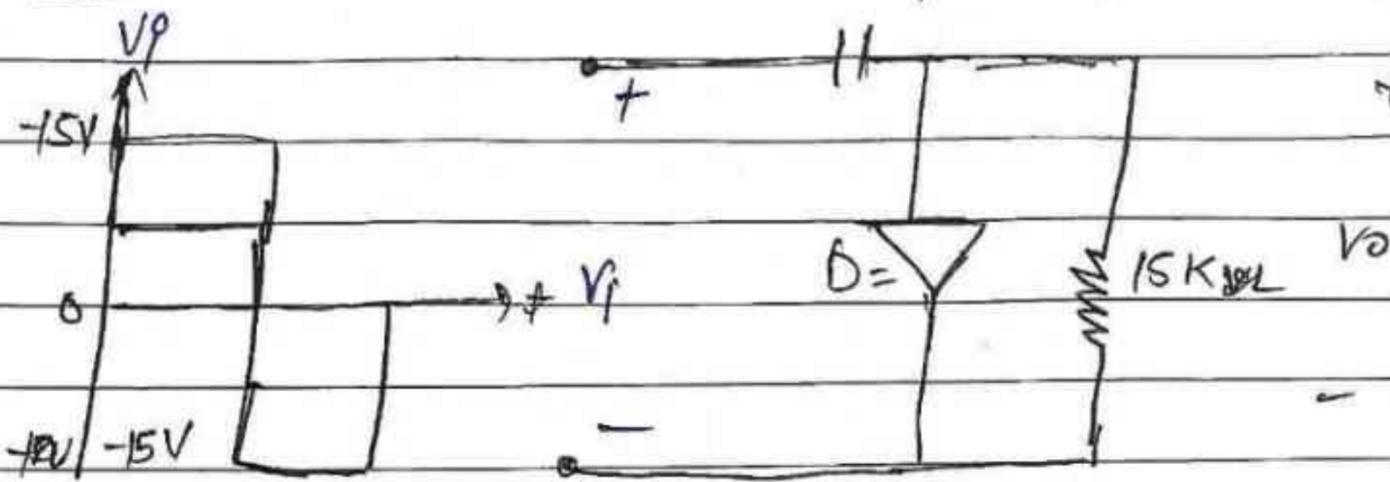Ques Sketch the V_o waveform for the given circuit



Soln Case - I - +ve half cycle

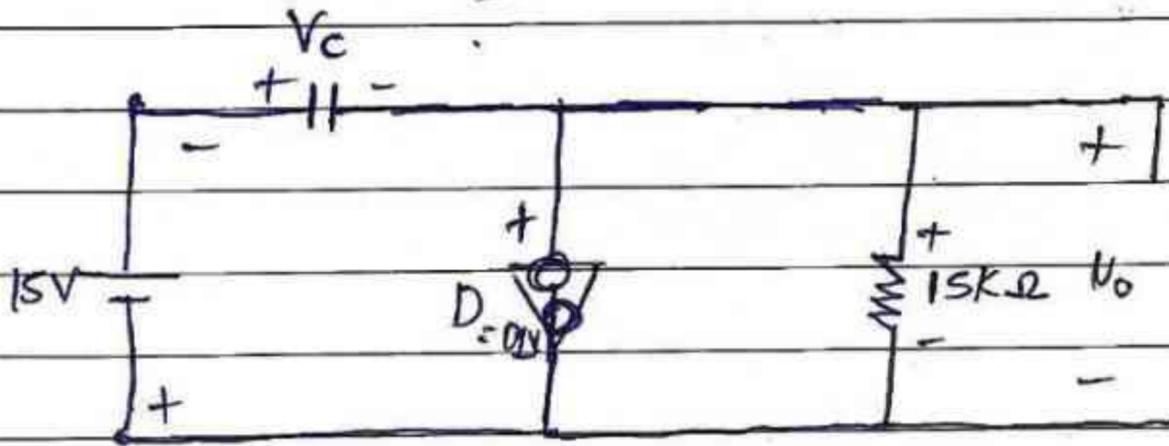


Using KVL

$$15 - V_c = 0$$

$$V_c = 15V$$

$$V_o = 0V$$

Case - II - -ve half cycle

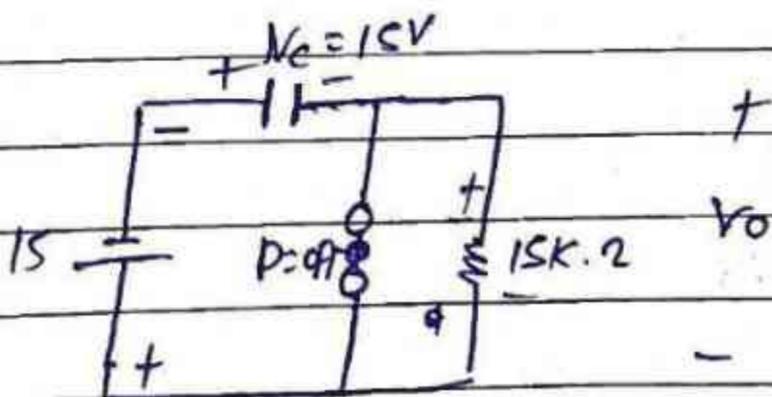

using KVL

$$+15 + V_o + 15 = V_o$$

$$V_o = -30V$$

अगर diode नीचे का है तो पहले case-1 +ve half cycle लिया जायेगा



और Diode अगर ऊपर की लगे हो तो पहले ^{Page} निगेटिव हालफ साईकल _{Date} पहले लगेगा

~~Clamper~~

clamper or level shifter -! clamper is an electronic circuit that fixes either


the positive or the negative peak excursion of a signal to a new defined voltage by adding a variable positive or negative D.C. voltage to it.

Clamper
|

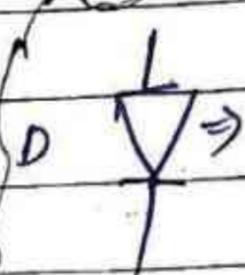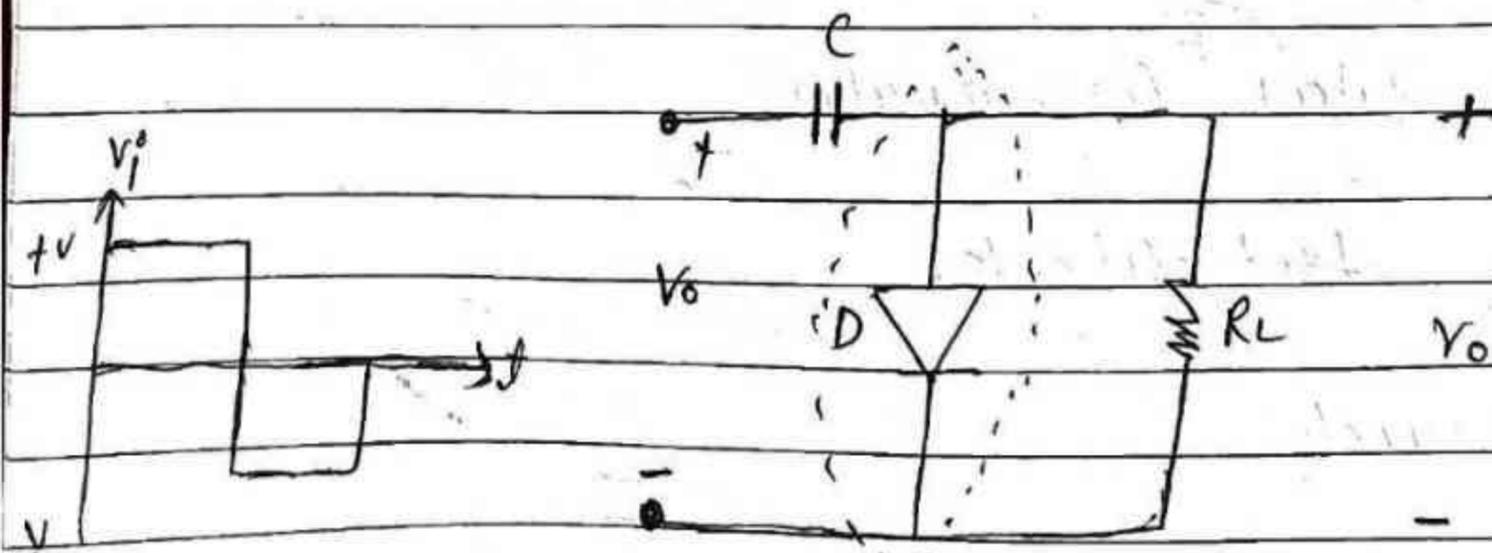

Case I = +ve half cycle : $D = ON$
 $V_c = ?$; $V_o = ?$

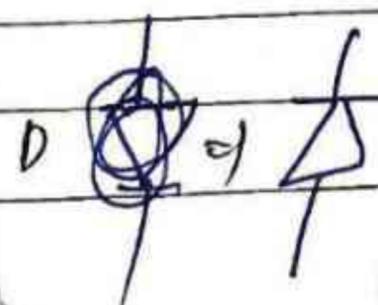
Case II = -ve half cycle : $D = OFF$
 $V_o = ?$



Case I = -ve half cycle : $D = ON$
 $V_c = ?$; $V_o = ?$


Case II = +ve half cycle : $D = OFF$
 $V_o = ?$





Case-II During ~~the~~ -ve half cycle

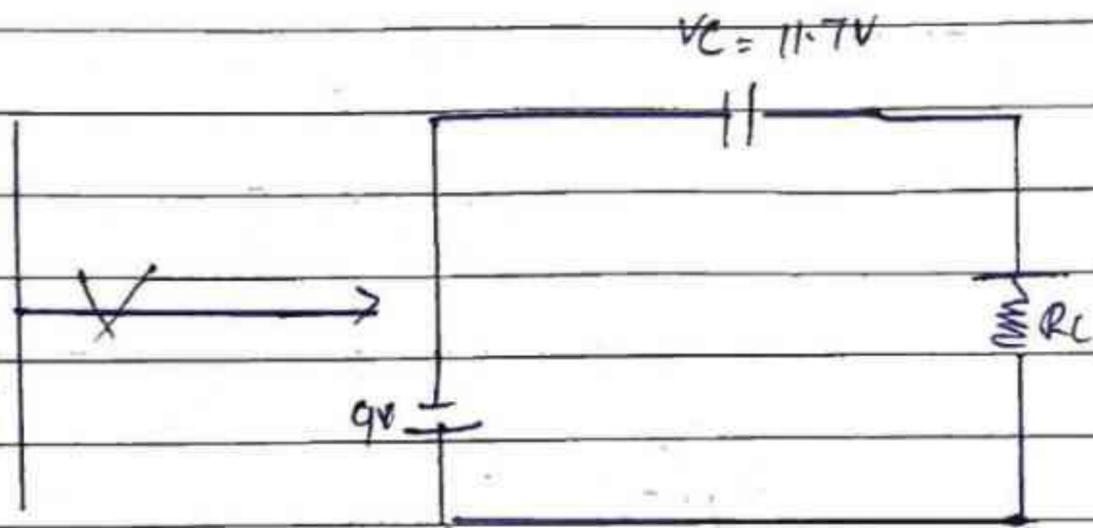

$$9 = V_o + 11.7$$

$$V_o = -20.7$$

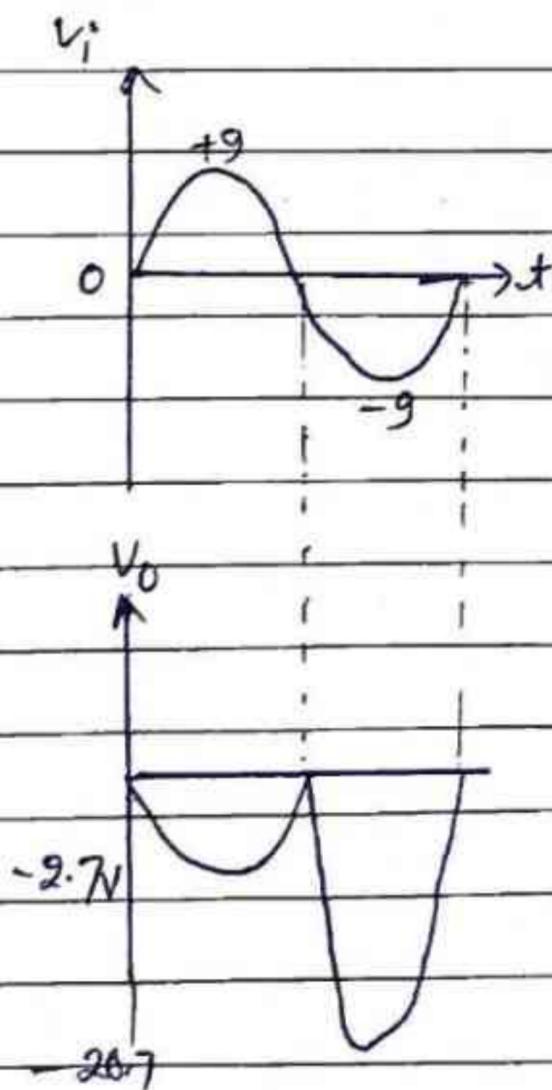

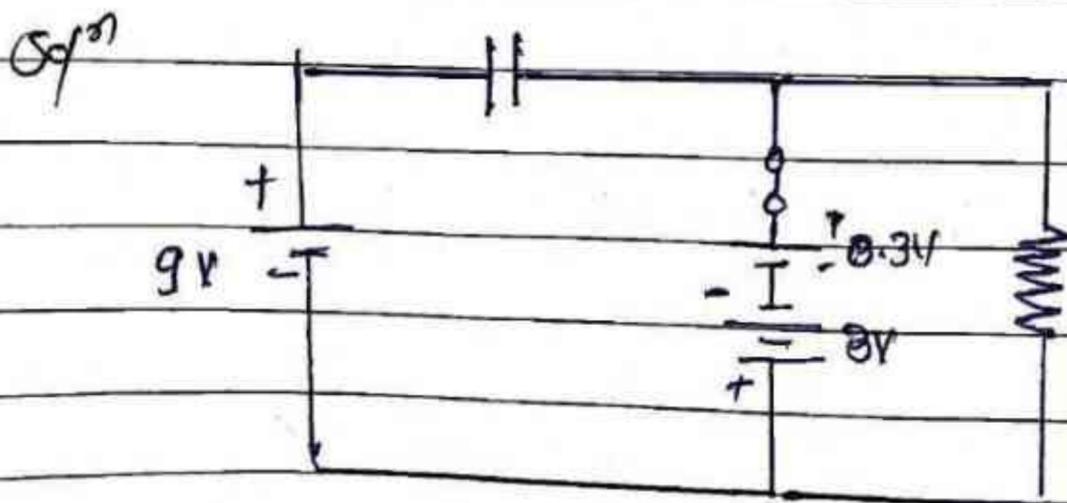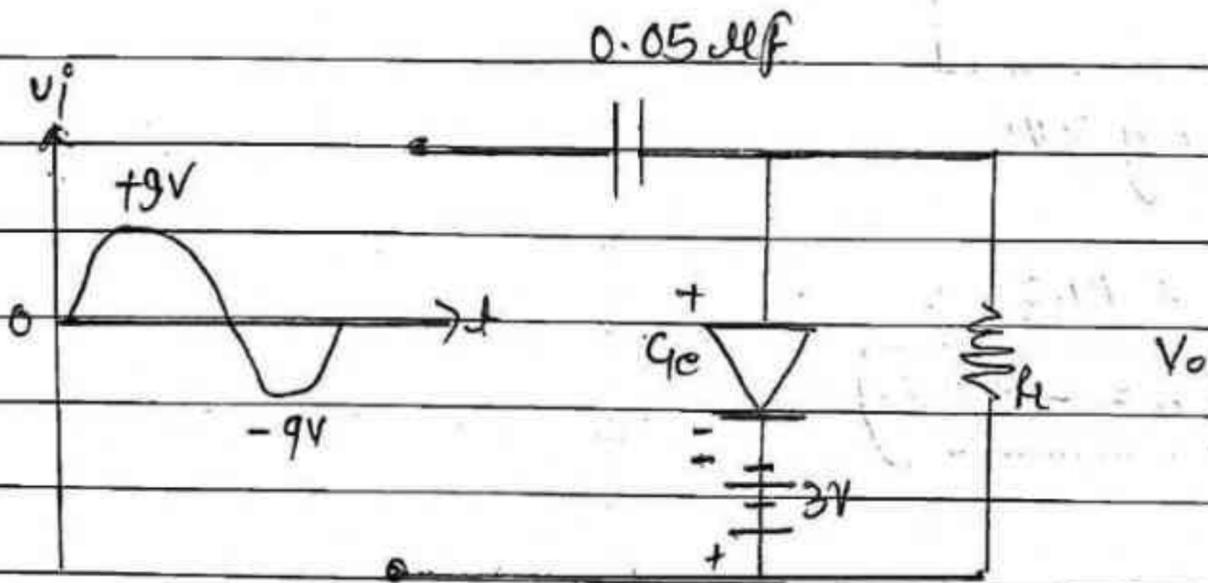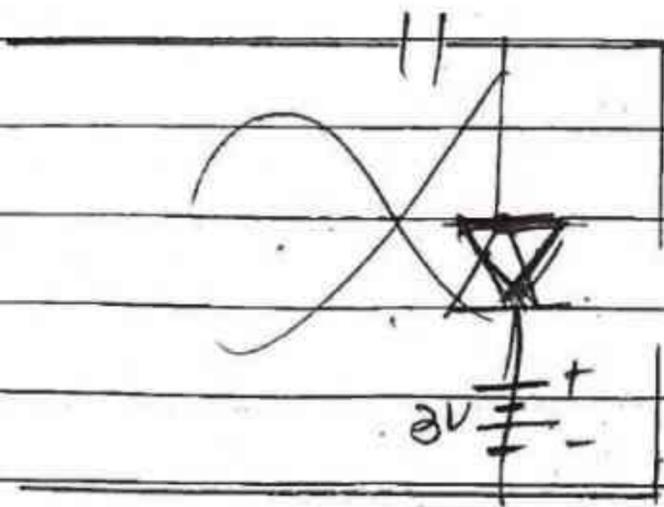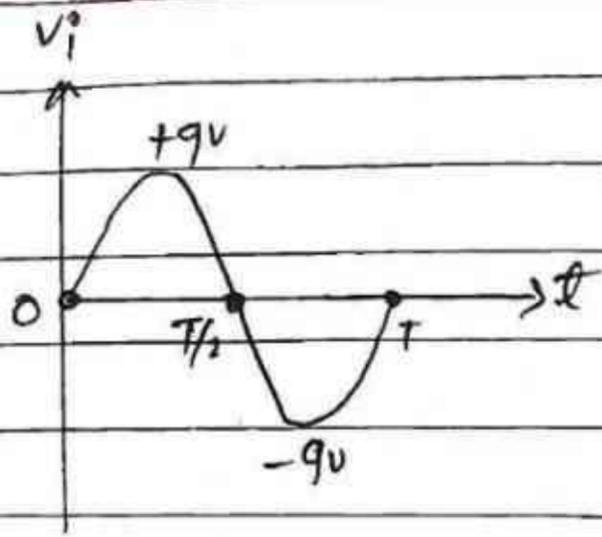

using KVL


$$9 + V_c - 0.3 + 3 = 0$$

$$V_c = 11.7 V$$

$$+3 + 0.3 = -V_o$$

$$V_o = -3.7$$


Case II During +90 deg cycle

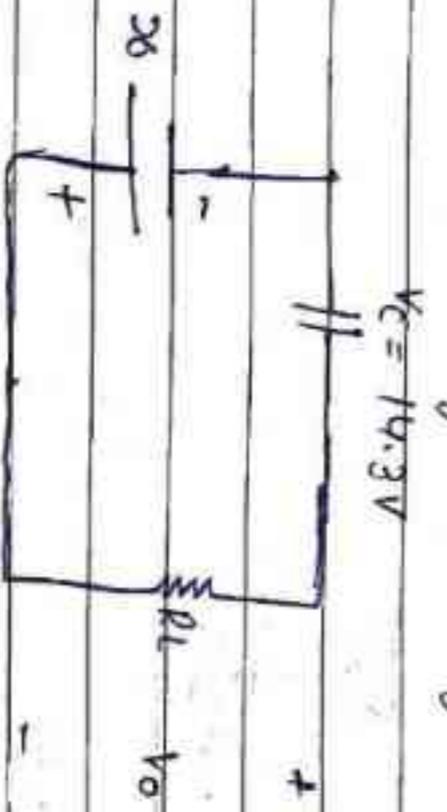

using KVL

$$20 + V_0 + 14.3 =$$

Manufacturing $V_0 = -34.3$

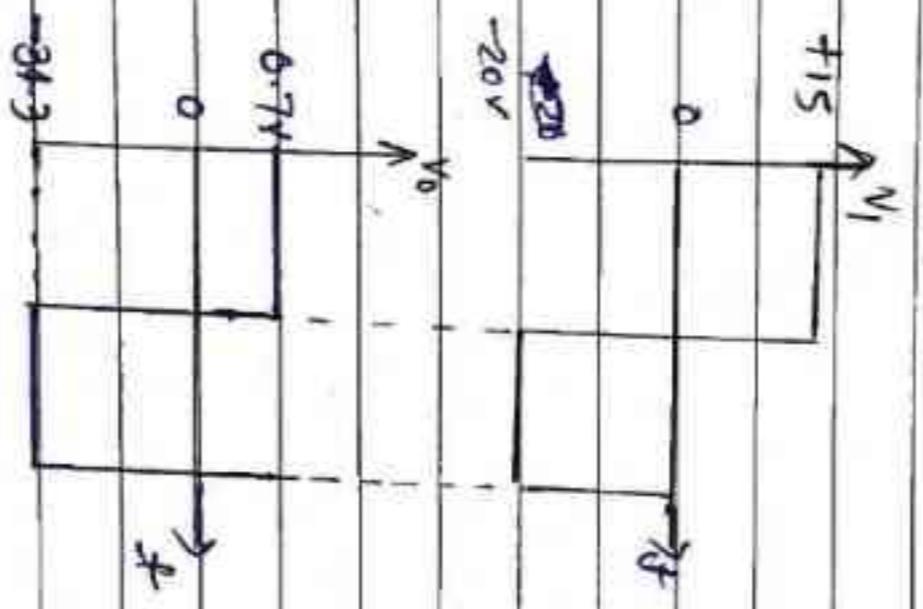

As


$\omega = 2\pi f = 2\pi \times 50 = 314 \text{ rad/s}$
 $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{15}{\sqrt{2}} = 10.6 \text{ V}$
 $I_{rms} = \frac{V_{rms}}{Z} = \frac{10.6}{14.3} = 0.74 \text{ A}$
 $P = V_{rms} I_{rms} = 10.6 \times 0.74 = 7.84 \text{ W}$

Ques :- Given Difference between p-n junction diode and zener diode.


p-n junction diode

1) it operates only in forward bias condition

2) Symbol

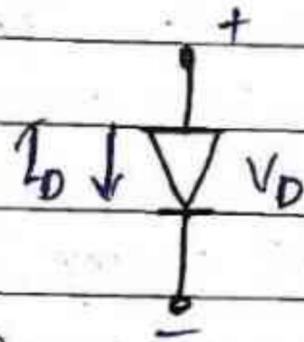


③

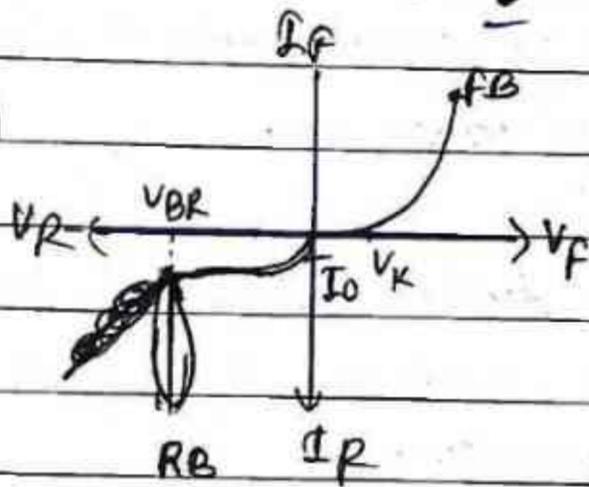


Zener diode

1) it operates in reverse bias condition.

2) Symbol

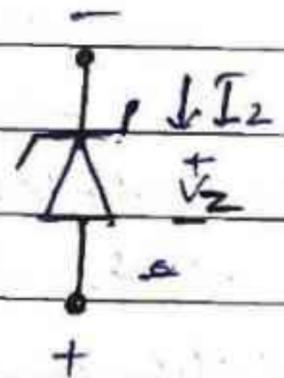

③

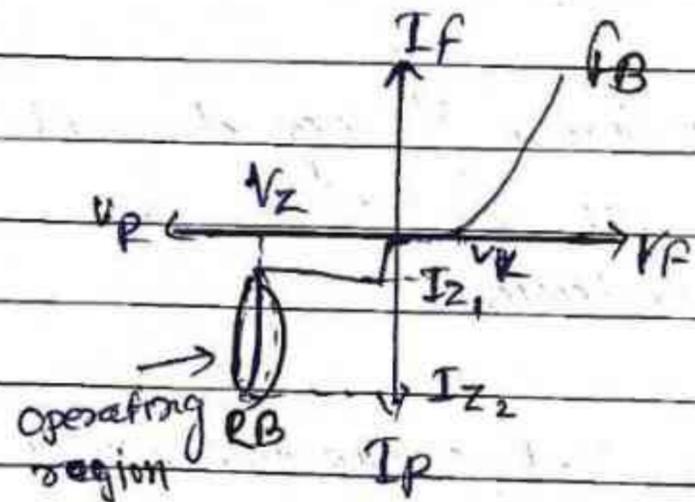


④ Application

- Rectifiers
- Voltage multipliers
- clamping circuits
- clipper

④ Application.



- Voltage regulator (shunt regulator)
- Protection circuits
- Voltage limiters.


During -ve half cycle:-

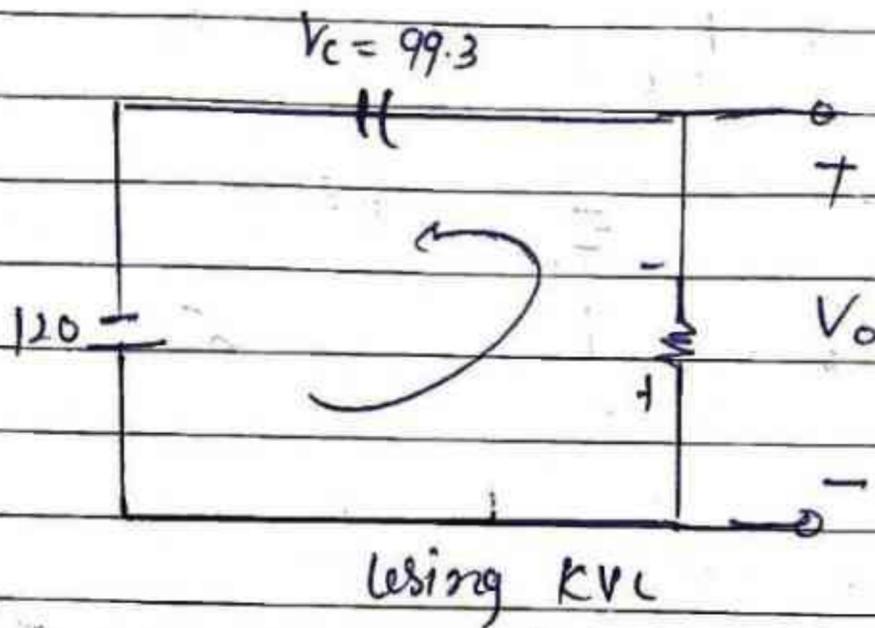


$$120 + V_o + 99.3 = 0$$

$$V_o = -219.3$$

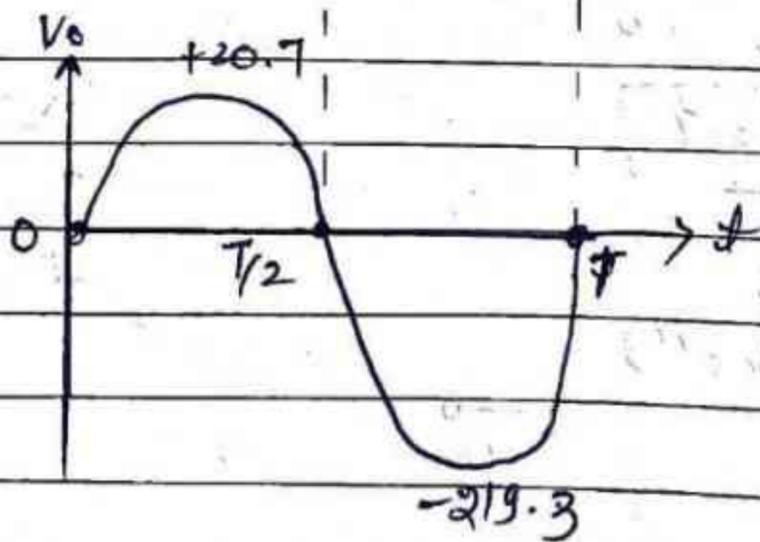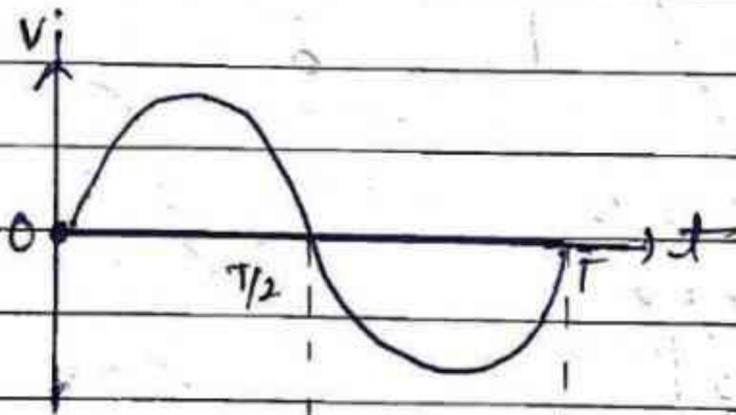

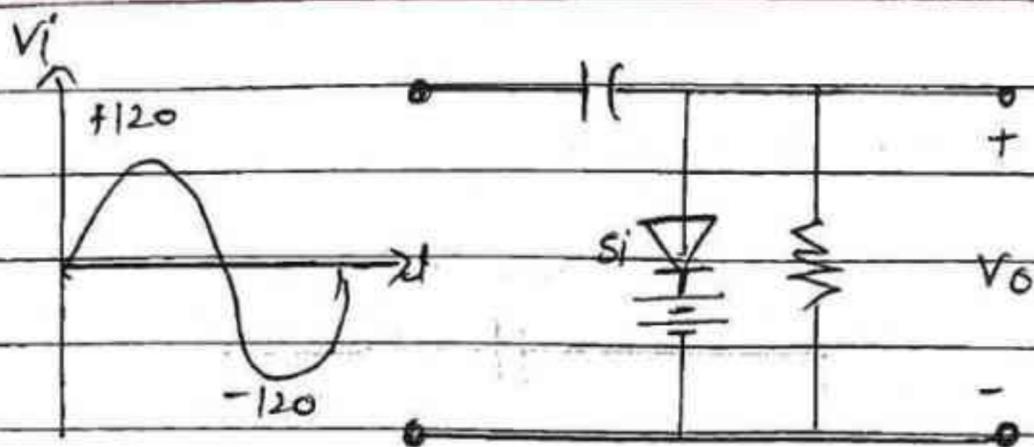Soln

During +ve half cycle-

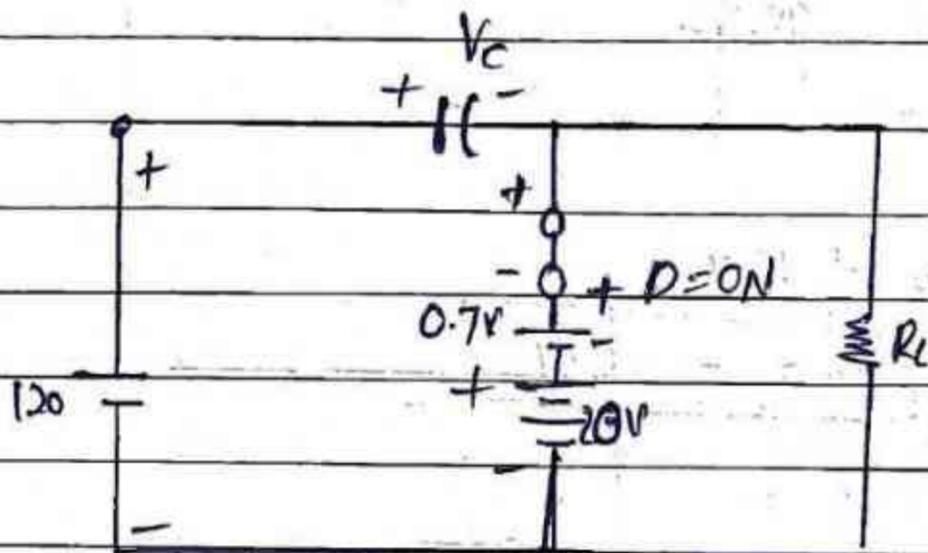

using KVL

$$120 - V_c - 0.7 - 20 = 0$$

$$+V_c = +120 + 20.7$$

$$V_c =$$

$$V_c = 120 + 20.7$$


$$V_c = 140.7$$

$$-0.7 - 20 + V_o = 0$$

$$V_o = 20.7$$

$$V_o = 20.7$$

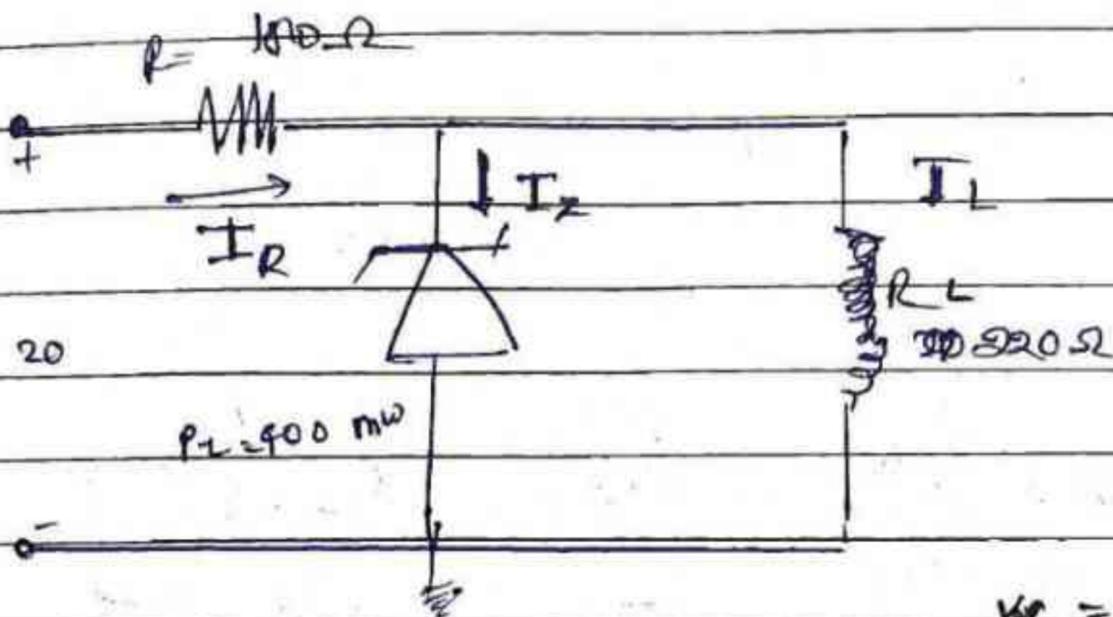
Determine V_L , I_R , I_Z and I_L of given network



$$V_x = \frac{R_L \times V_i}{R + R_L}$$

$$V_x = \frac{R_L \times V_i}{R + R_L} = \frac{220 \times 20}{180 + 220}$$

$$= \frac{4400}{400}$$

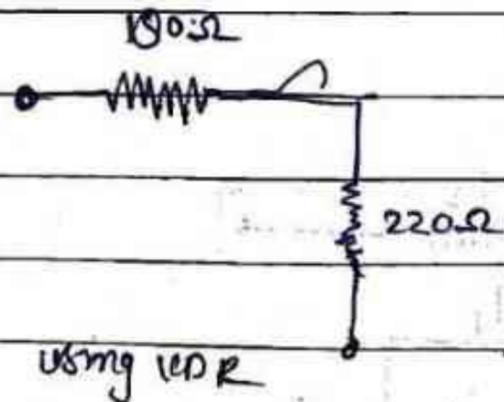

$$V_x = \frac{220}{180 + 220} \times 20 = 11V$$


Since $V_x > V_Z$, therefore Zener diode is ON

$$\therefore V_L = V_Z$$

$$V_L = V_Z$$

$$I_R = \frac{V_i - V_Z}{R} = \frac{20 - 10}{180} = 0.055A$$

using VDR

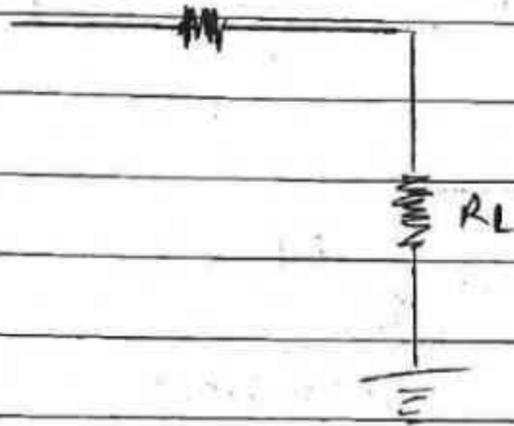


$$V_x = \frac{R_L}{R + R_L} \times V_i$$

$$V_x = \frac{R_L}{R + R_L} \times V_i$$

* If $V_x > V_z$
 If V_z then Zener diode is ~~not~~ ON

$$\therefore V_L = V_x$$

$$\therefore I_L = \frac{V_L}{R_L}$$

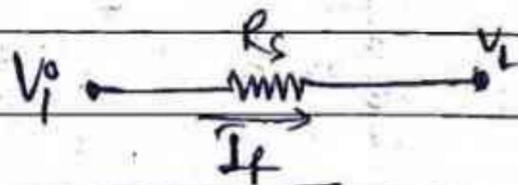

$$I_i = \frac{V_i - V_L}{R_s}$$

$$I_i = I_z + I_L$$

$$\therefore I_z = I_i - I_L$$

$$V_{RS} = I_i \times R_s \quad \text{OR} \quad V_{RS} = V_i - V_L$$

$$P_z = V_z \cdot I_z$$

Ques

Given differences b/w zener breakdown mechanism and avalanche breakdown mechanism.

Ans


Zener breakdown mechanism

Avalanche breakdown mechanism

<p>① It occurs when V_z is b/w 5V to 8V. $[5V < V_z < 8V]$</p>	<p>① It occurs when V_z is greater than 8V. $[V_z > 8V]$</p>
<p>② The valence electrons are pulled into the conduction band due to very high electric field appearing near the narrow Depletion region.</p>	<p>② The valence electrons are pulled into the conduction band due to the energy imparted by collision of accelerated minority charge carriers.</p>
<p>③ Breakdown Voltage decreases with an increase in temperature.</p>	<p>③ Break down voltage decreases increases with an increase in temperature.</p>
<p>④ It's V-I character is very sharp</p>	<p>④ It's V-I characteristic is not so sharp.</p>

Application of Zener diode:-

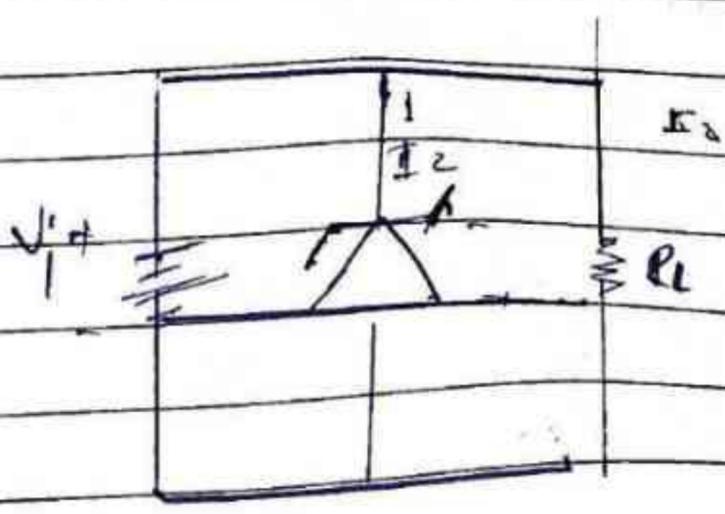⇒ Zener Diode as Voltage Regulator (Shunt regulator):-




$$I_R = \frac{V_i - V_L}{R_S} = \frac{15 - 8}{1.05} = 6.6 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{8}{1.2} = 6.6 \text{ mA}$$

$$\therefore I_R = I_Z + I_L$$

$$\therefore I_Z = I_L - I_R \Rightarrow 6.66 - 6.66 = 0 \text{ mA}$$

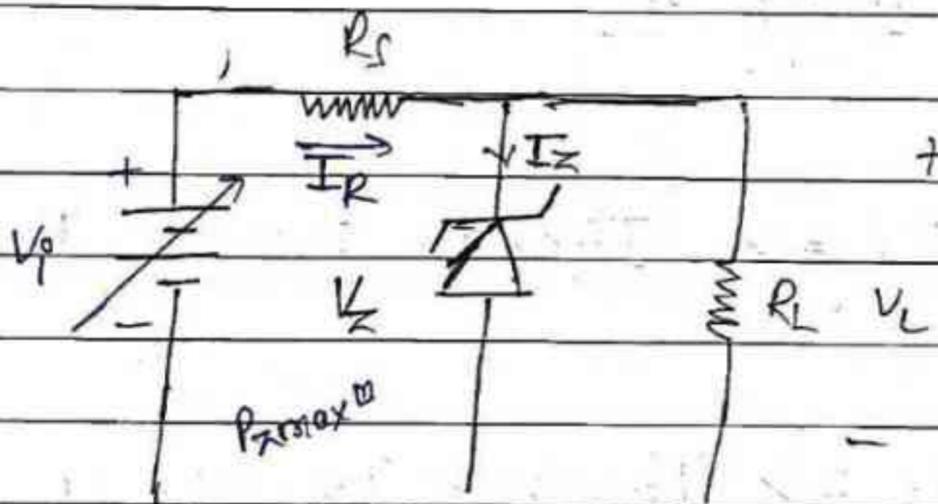Case - II When $V_i = \nearrow$ (variable) & $R_L = K$ (constant)



* $V_L = \text{Given}$

$$V_L = I_L \cdot R_L$$

$$K = K \cdot K$$

* $V_i = \uparrow$ (max^m)

$$I_R = I_Z + I_L$$

$$\uparrow = \uparrow + K$$

$$V_{i \text{ max}} \rightarrow I_{R \text{ max}} \rightarrow I_{Z \text{ max}} \rightarrow I_{L \text{ K}}$$


* $V_i = \downarrow$

$$I_R = I_Z + I_L$$

$$\downarrow = \downarrow + K$$

$$V_{i \text{ min}} \rightarrow I_{R \text{ min}} \rightarrow I_{Z \text{ min}} \rightarrow I_{L \text{ K}}$$

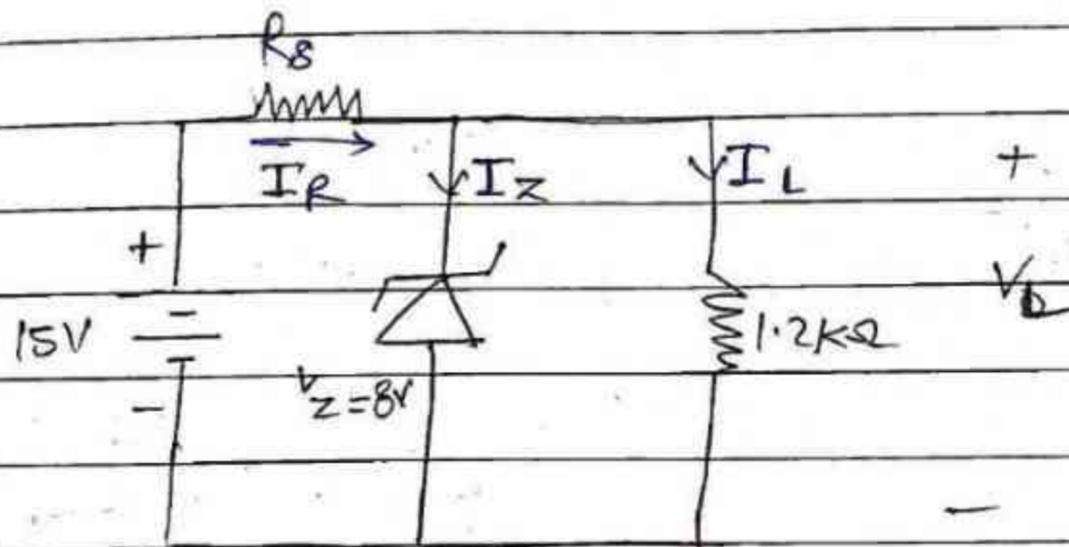Ques 2 - Calculate the value of R_s and I_z for the given network to maintain zener diode in on condition or on escape.



$$V_i = V_z$$

$$\therefore V_z = 8V$$

$$\therefore V_L = 8V$$

Now by using VDR

$$V_L = \frac{R_L}{R_s + R_L} \times V_i$$

$$8 = \frac{1.2}{R_s + 1.2} \times 15$$

$$(R_s + 1.2) \times 8 = 1.2 \times 15$$

$$8R_s + 9.6 = 1.2 \times 15$$

$$8R_s + 9.6 = 18$$

$$8R_s = 18 - 9.6$$

$$R_s = \frac{8.4}{8}$$

$$R_s = 1.05k\Omega$$

$$V_L = \frac{R_L}{R_s + R_L} \times V_i$$

$$V_L(R_s + R_L) = R_L V_i$$

$$V_L R_s + V_L R_L = R_L V_i$$

$$V_L R_s = R_L V_i - V_L R_L$$

$$V_L R_s = R_L (V_i - V_L)$$

$$V_L R_s = 1.2(15 - 8)$$

$$R_s = \frac{1.2(15 - 8)}{8}$$

$$= 1.05k\Omega$$


$$I_R = I_Z + I_L$$

$$I_Z = I_R - I_L$$

$$I_R = I_Z + I_L$$

$$0.055 - 0.045 = 0.010$$
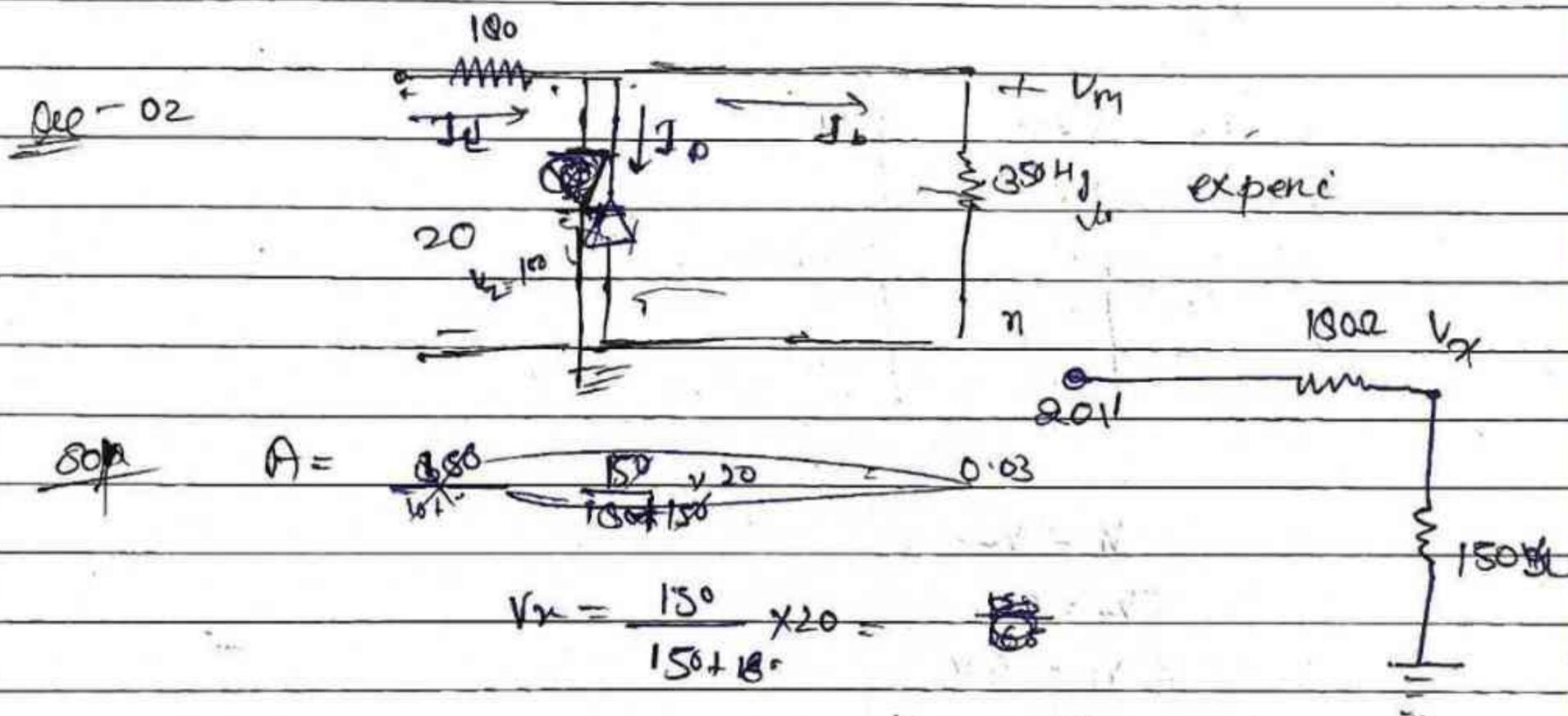
$$\therefore I_Z = I_R - I_L = 0.055 - 0.045 = 0.010 \text{ A}$$



$$V_L = \frac{150}{330} \times 20 = 9.09$$

Since $V_C < V_Z$ therefore Zener diode is OFF

$$V_L = V_Z$$

$$V_L = 9.09$$

$$I_R = \frac{V_i - V_L}{R_S} = \frac{20 - 9.09}{180}$$

$$0.060 \text{ A}$$

$$I_L = \frac{9.09}{150} = 0.060 \text{ A}$$


$$I_R = I_Z + I_L$$

$$= 0.060 - 0.060$$

$$= 0$$

Ques \Rightarrow Determine the Range of input Voltage (V_s) for the zener diode to remain in or stay given that
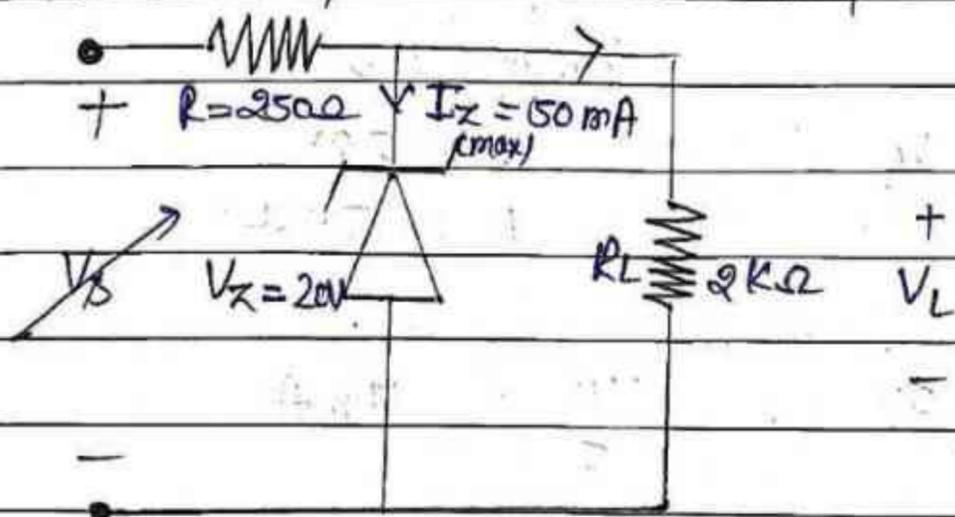
$$V_Z = 20V, I_{Z(max)} = 50mA, R_Z = 0\Omega$$



Soln \Rightarrow Since $V_L = V_Z = 20V$
using VDR

$$V_L = \frac{R_L}{R + R_L} \times V_{s_{min}}$$

$$V_{s_{min}} = \frac{V_L (R + R_L)}{R_L}$$

$$10 \times 26 (0.25 + 2) \Rightarrow 22.5V$$

$$I_{max} = \frac{V_{s_{max}} - V_L}{R}$$

$$I_{max} = \frac{V_{s_{max}} - V_L}{R}$$

$$V_{s_{max}} = I_{max} \cdot R + V_L$$

$$V_{s_{max}} = (I_{Z(max)} + I_L) R + V_L$$

$$= \left(I_{Z(max)} + \frac{V_L}{R_L} \right) R + V_L$$

(Solⁿ) → let us assume that zener diode is ON

$$\therefore V_L = V_Z = 50V$$

$$I_{max} = ?$$

$$V_{imax} = 120$$

$$I_{(max)} = \frac{V_{imax} - V_L}{R}$$

$$V_L = 50V$$

$$R = 5k\Omega$$

$$I_{(max)} = \frac{120 - 50}{5} = \frac{70}{5} = 14mA$$

$$\boxed{I_{(max)} = 14mA}$$

$$I_{(min)} = \frac{80 - 50}{5} = \frac{30}{5} = 6mA$$

$$\boxed{I_{(min)} = 6mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{50}{10} = 5$$

$$I_{(max)} = I_{z(max)} + I_L$$

$$\boxed{I_L = 5}$$

$$I_{z(max)} = 14 - 5$$

$$\boxed{I_{z(max)} = 9mA}$$

$$I_{z(min)} = I_{(min)} - I_L$$

$$6 - 5$$

$$\boxed{I_{z(min)} = 1mA}$$

$$P_{z(max)} = 50 \times 1$$

$$\boxed{P_{z(max)} = 50W}$$

* $V_L = \text{Given}$

$$I_L = \frac{V_L}{R_L}$$

$$I_P(\text{max}) = \frac{V_i(\text{max}) - V_L}{R_S}$$


$$I_P(\text{min}) = \frac{V_i(\text{min}) - V_L}{R_S}$$

* $I_P(\text{max}) = I_Z(\text{max}) + I_L \Rightarrow I_Z(\text{max}) = I_P(\text{max}) - I_L$


* $I_P(\text{min}) = I_Z(\text{min}) + I_L \Rightarrow I_Z(\text{min}) = I_P(\text{min}) - I_L$

$$P_Z(\text{max}) = V_Z \cdot I_Z(\text{max})$$

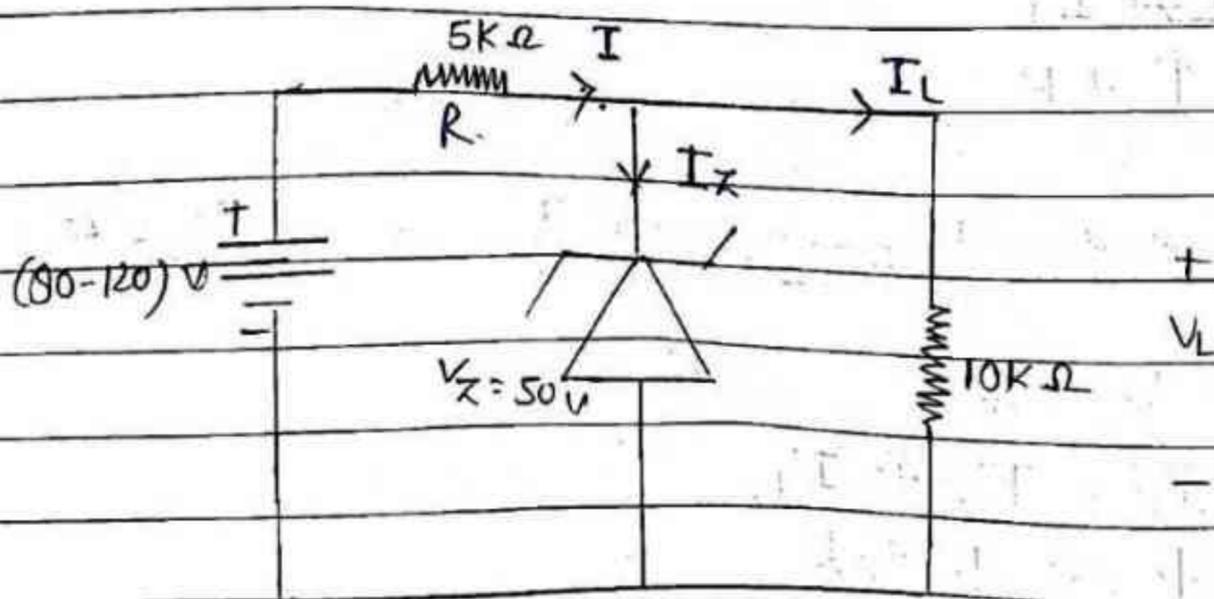Que:- Determine the value of maximum and minimum zener diode current for the circuit shown below.



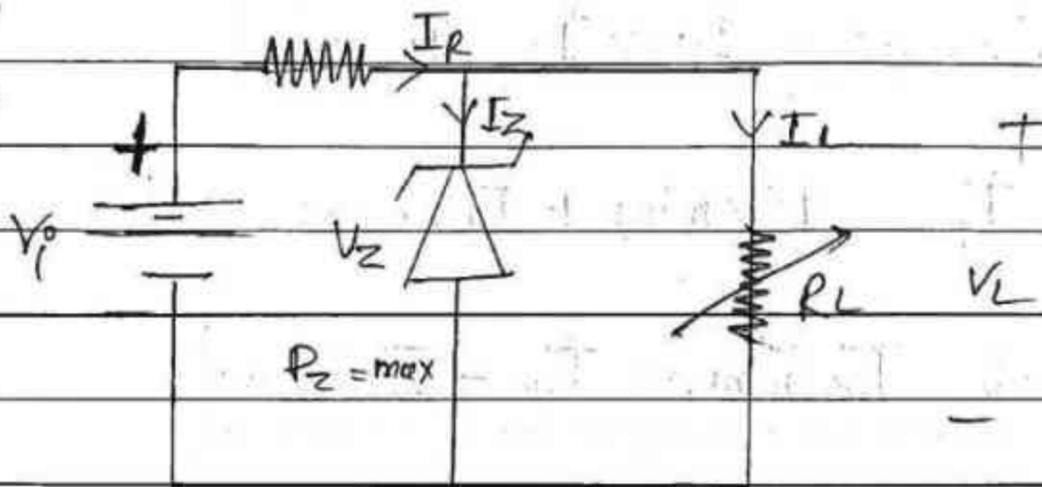Case - III \rightarrow When $V_i = K + R_L = \uparrow (K)$



* $R_L = \uparrow$

$$I_R = I_z + I_L$$

$$K = \uparrow + \downarrow$$

$$R_{L(\max)} \rightarrow I_{z(\max)} \rightarrow I_{L(\min)} \rightarrow I_R(K)$$

* $R_L = \downarrow$

$$I_R = I_z + I_L$$

$$K = \downarrow + \uparrow$$

$$R_{L(\min)} \rightarrow I_{z(\min)} \rightarrow I_{L(\max)} \rightarrow I_R(K)$$

$$I_{L(\min)} = \frac{V_L}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_L}{R_{L(\min)}}$$

$$I_R = \frac{V_i - V_L}{R_s}$$

Since Zener diode is ON, therefore $V_L = V_Z$

$$\therefore V_L = 8V$$

using VDR

$$V_L = \frac{R_L}{R_S + R_L} V_{in(min)}$$

$$V_{in(min)} = \frac{V_L (R_S + R_L)}{R_L}$$

$$= \frac{8(0.82 + 0.22)}{0.22} = 100.98V$$

$$V_{in(max)} = V_{L} + I_{Z(max)} \cdot R_S$$

$$= (I_{Z(max)} + I_L) R_S + V_L$$

$$= \left(\frac{P_{Z(max)}}{V_Z} + \frac{V_L}{R_L} \right) R_S + V_L$$

$$= \left(\frac{400}{8} + \frac{8}{0.22} \right) 0.082 + 8$$

$$= (50 + 36.36) \cdot 0.082 + 8$$

$$= (86.36) \cdot 0.082 + 8$$

$$= 7.08 + 8$$

$$= 15.08V$$


$$V_{in(max)} = 15.08V$$

$$\left(\frac{50 + 20}{2} \right) 0.25 + 20$$


$$V_{s \max} = \underline{\underline{35V}}$$

Ques: Determine the range of input voltage (V_{in}) to maintain zener diode in ON condition and exceeded the maximum power rating of the zener diode.

V_{in} (input voltage)

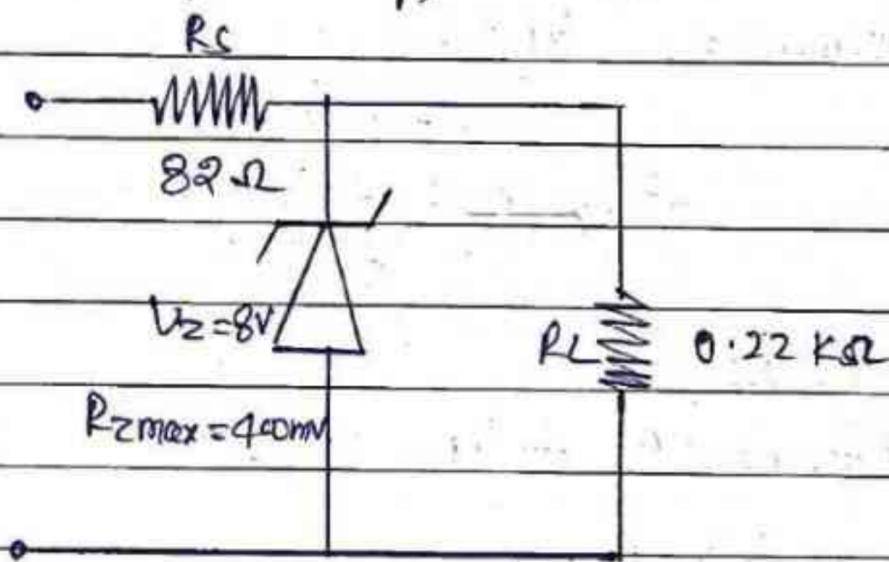

(Soln)

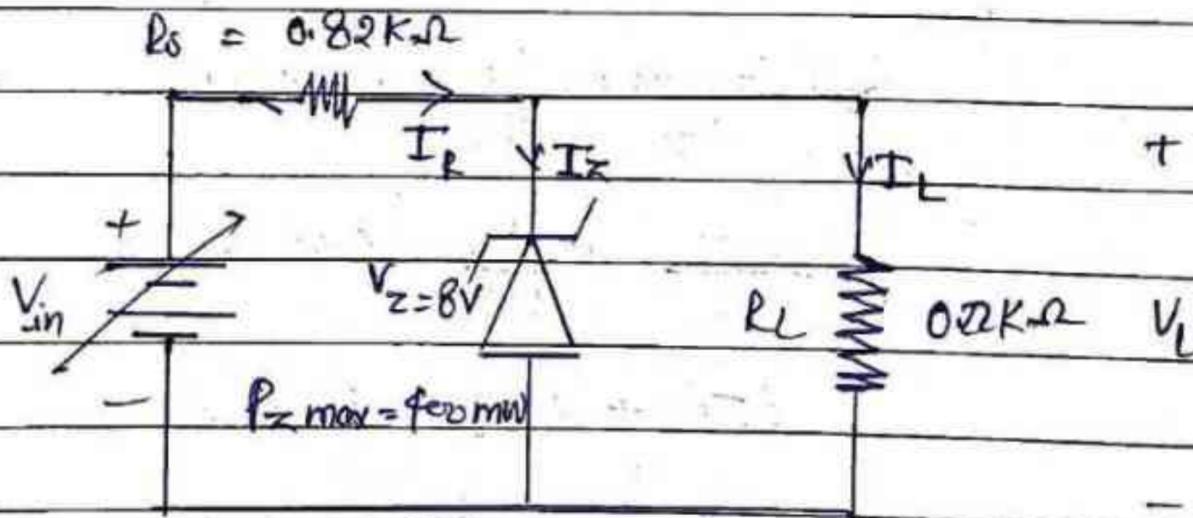

$$V_L = \frac{R_L}{R_s + R_L} \times V_{in}$$

$$= V_L (R_s + R_L) = R_L \cdot V_{in}$$

$$V_L R_s + V_L R_L = R_L \cdot V_{in}$$

$$V_L R_s = R_L \cdot V_{in} - R_L V_L$$

$$V_L R_s = R_L (V_{in} - V_L)$$

$$V_L R_s =$$

$$\therefore R_L(\text{max}) = \frac{V_L}{I_L(\text{min})} = \frac{10}{8} = 1.25 \text{ K}\Omega$$

Range of $R_L = 0.25 \text{ K}\Omega$ to $1.25 \text{ K}\Omega$

Range of $I_L = 8 \text{ mA}$ to 10 mA

$$\text{ii) } P_Z(\text{max}) = V_Z \cdot I_Z(\text{max}) = 10 \times 32 = 320 \text{ mW}$$

Solⁿ i) $V_L = 10V$

using VDR

$$V_L = \frac{R_{Lmin}}{R + R_{Lmin}} \times V_i$$

$$V_L R + V_L R_{Lmin} = R_{Lmin} \cdot V_i$$

$$V_L R = R_{Lmin} (V_i - V_L)$$

$$R_{Lmin} = \frac{V_L R}{(V_i - V_L)}$$

$$R_{Lmin} = \frac{10 \times 1}{(50 - 10)} = \frac{10}{40} = 0.25 K\Omega$$

$$V_L = R_{Lmin} \cdot I_{L(max)}$$

$$I_{L(min)} = \frac{V_L}{R_{Lmin}}$$

$$= \frac{10}{0.25} = 40 mA$$

$$\therefore R_L (max) = \frac{V_L}{I_{L(min)}}$$

$$\therefore I_R = I_{Z(max)} + I_{L(min)}$$

$$\therefore I_{L(min)} = I_R - I_{Z(max)}$$

$$= \frac{V_i - V_L - 32}{R}$$

$$= \frac{50 - 10 - 32}{1}$$

$$I_{L(min)} = 8 mA$$

$$I_R = I_{Z \max} + I_{L \min}$$

$$\therefore I_{Z \max} = I_P - I_{L \min}$$


$$I_P = I_{Z \min} + I_{L \max}$$

$$\therefore I_{Z \min} = I_P - I_{L \max}$$

and

$$P_{Z \max} = V_Z \cdot I_{Z \max}$$

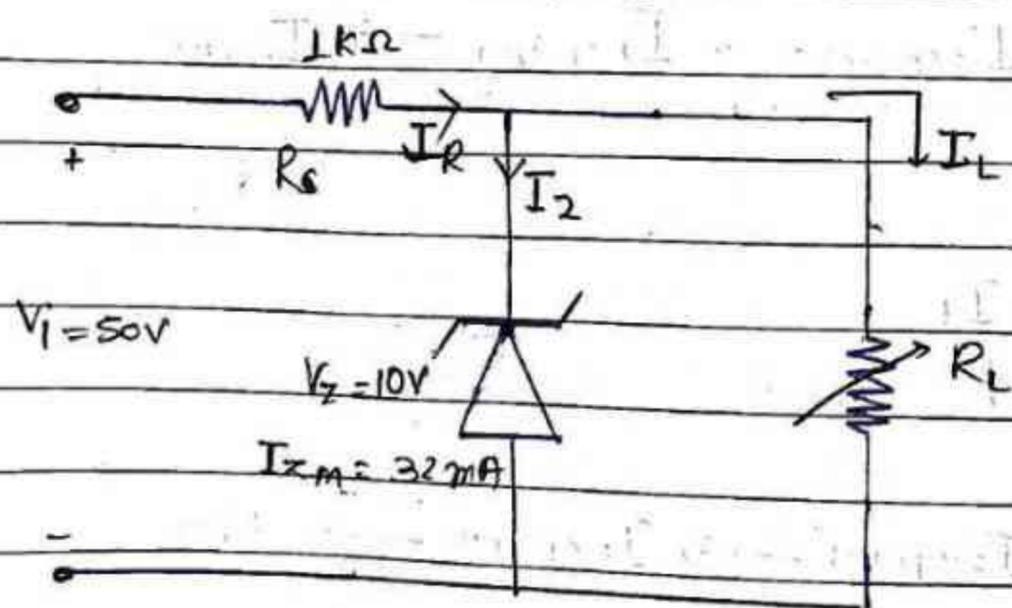Que:- Determine the range of V_i for the figure that will maintain the zener diode is "on" state?





i) Range of R_L and I_L

iii) Maximum wattage


solving Given that

$$P_{Z \max} \quad V_Z = 10V$$

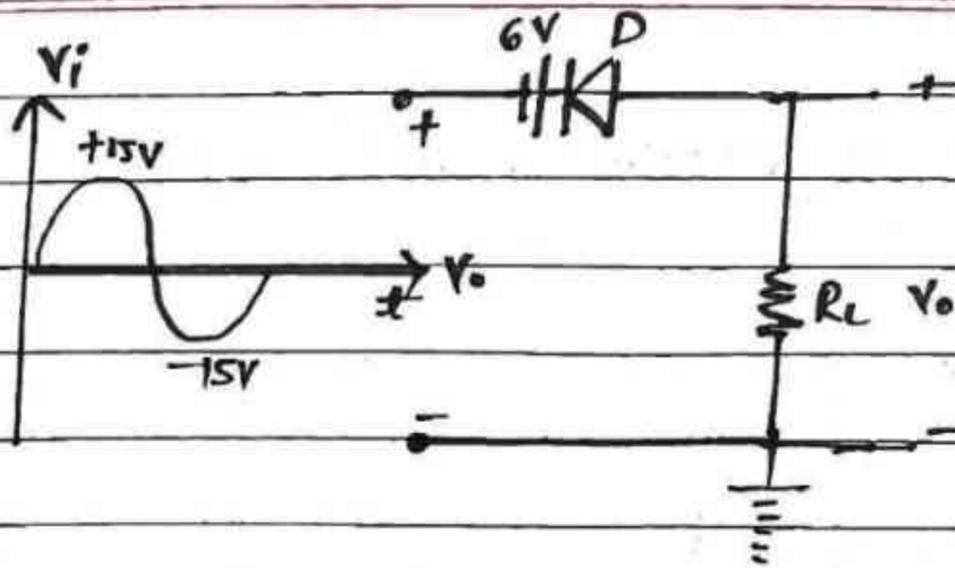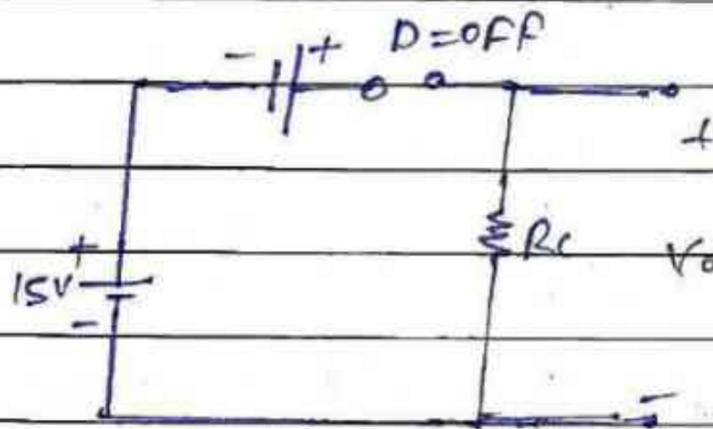Que:-SolnCase I:- During ^(+ve) Positive Half Cycle

$$V_o = 0V$$

Case II:- During -ve Half Cycle

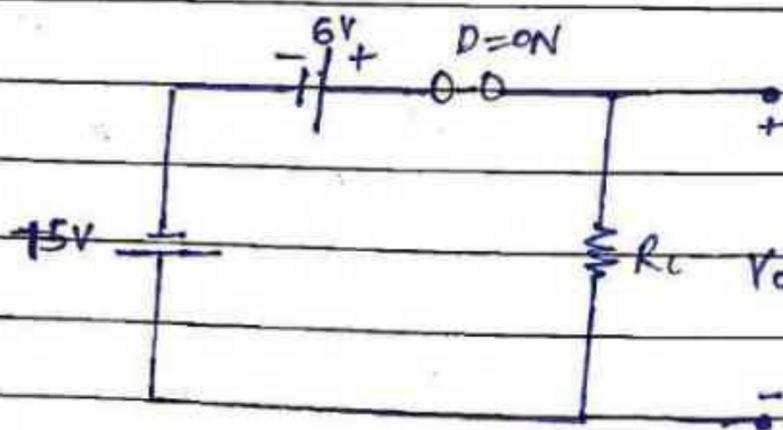

$$\begin{array}{|l} V_i < -6 & V_i > -6 \\ D = \text{OFF} & D = \text{ON} \end{array}$$

$$\begin{array}{|l} V_o = 0V & 15 + V_o - 6 = V_o \\ & V_o = -9V \end{array}$$

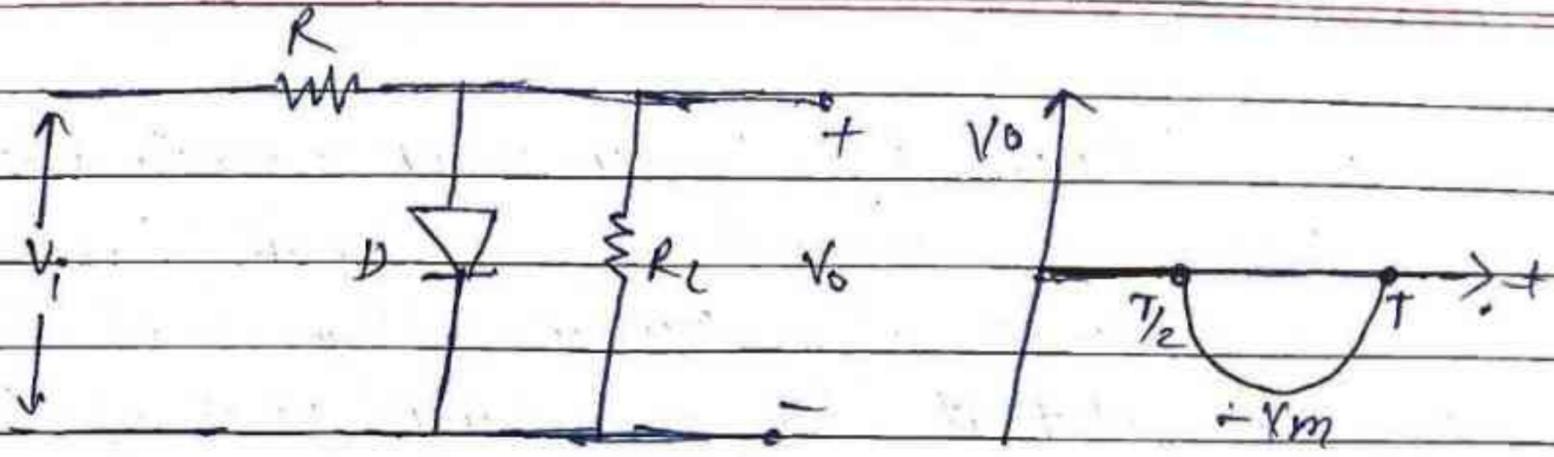


Fig:- Positive Parallel Clipper

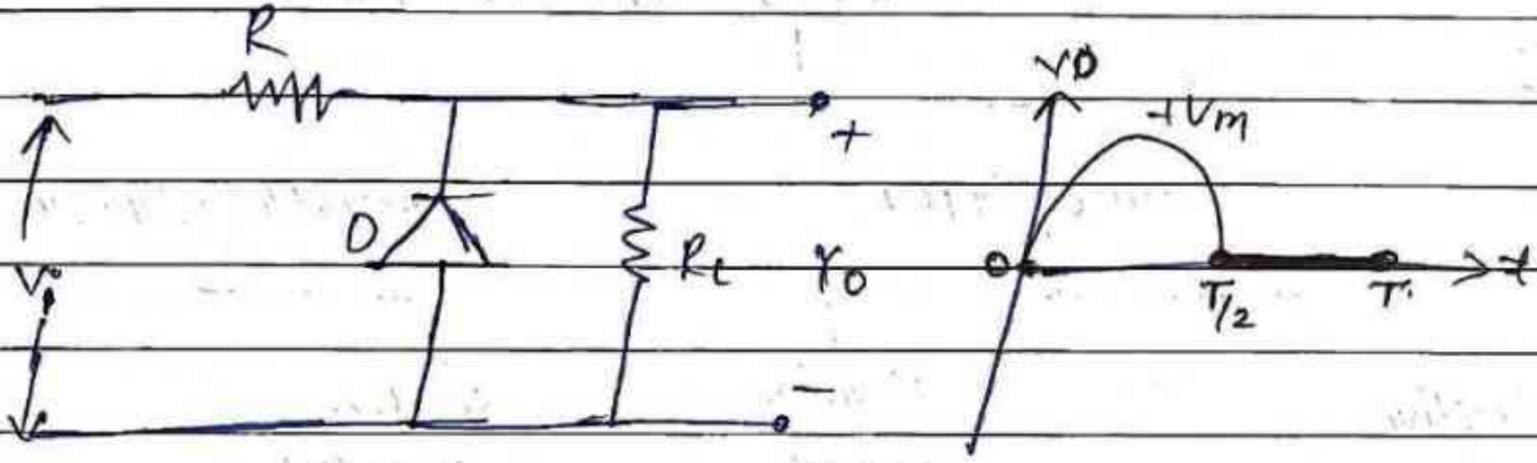


Fig:- Negative Parallel Clipper


* Note:-

\$\Rightarrow\$ F.O.B. Series Clipper \$\rightarrow\$ Case of opposition \$\rightarrow D = \text{ON} \rightarrow \boxed{V_o \propto V_i}\$



\$\Rightarrow\$ F.O.B./R.B. Parallel Clipper \$\rightarrow\$ Case of opposition \$\rightarrow D = \text{OFF} \rightarrow \boxed{V_o \propto V_i}\$

\$\Rightarrow\$ F.O.B. Series/Parallel Clipper \$\rightarrow\$ Determine Transition level (T.L.) = ?

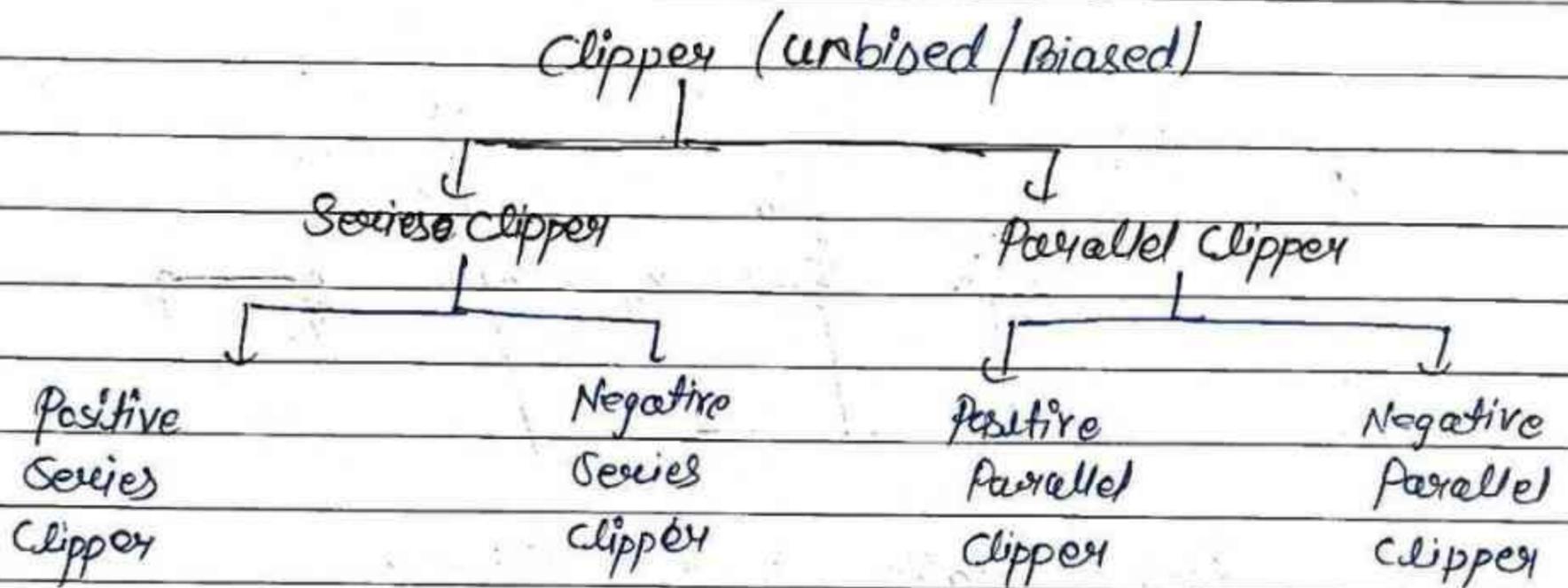Clipper OR Slicer:- A Clipper is an ~~electronic~~ electronic device designed to prevent a signal from exceeding a predetermined reference voltage level. A clipper does not distort the remaining part of the applied input waveform.




• **Unbiased Clipper:-**

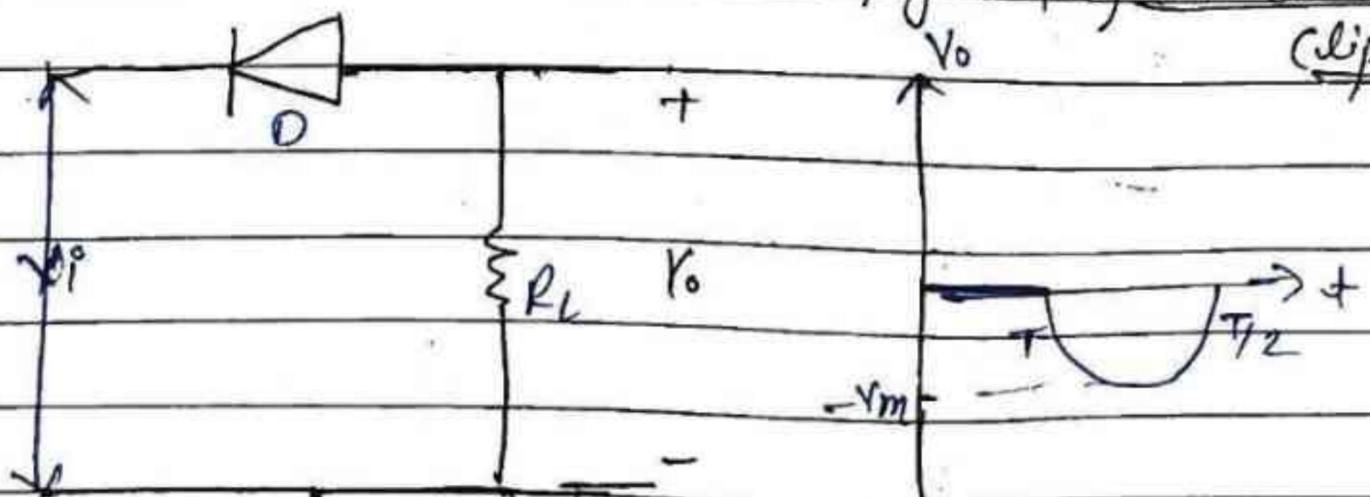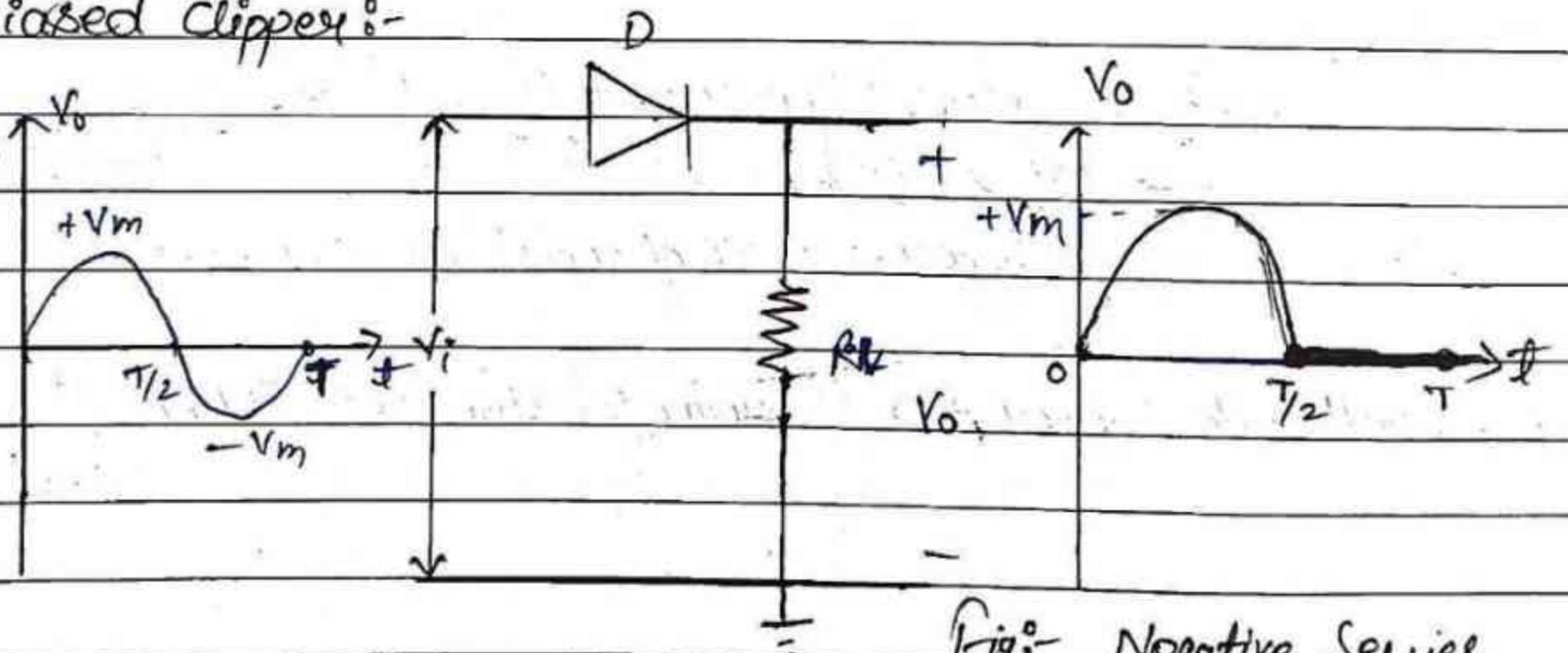


= Fig:- Positive Series Clipper

Que :- Sketch the V_o waveform for the given network.

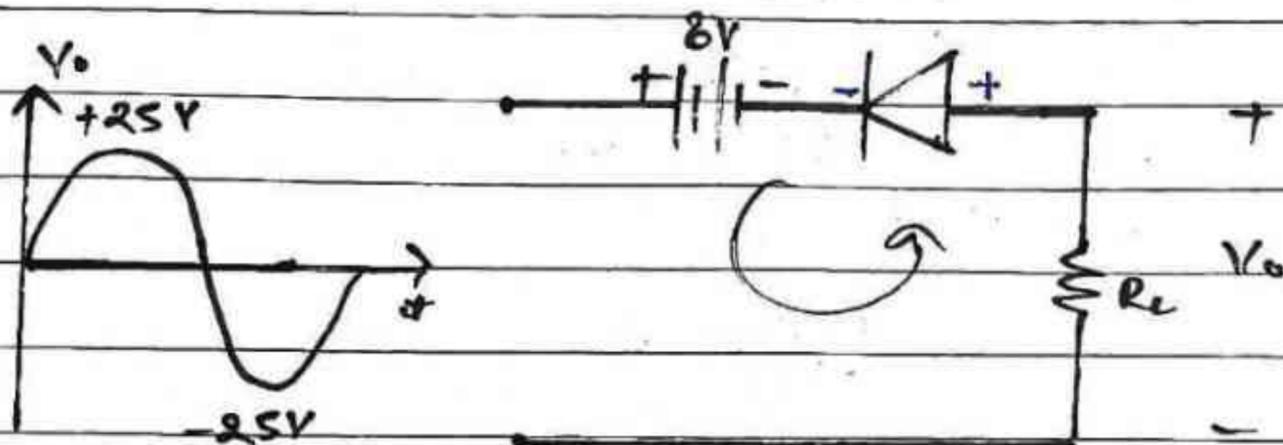

Case I :- During +ve Half Cycle.

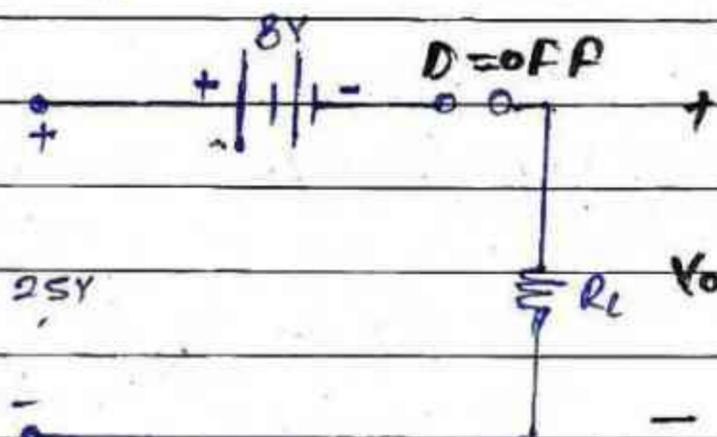


T.L =

$$V_o + 8V = 0$$

$$\boxed{V_o = -8V}$$

$V_i < 8V$	$V_i > 8V$
D = ON	D = OFF
$\boxed{V_o \propto V_i}$	$\boxed{V_o = 0}$

Case II :- During -ve half cycle.

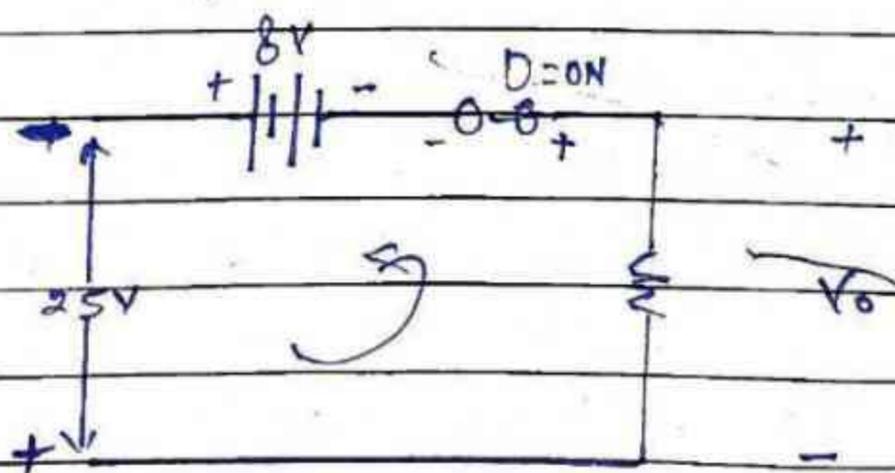

using KVL

$$25 + V_o + 8 = 0$$


$$\boxed{V_o = -33}$$

Using KVL:


$$25 + 8 - V_o = 0$$


$$V_o = 33V$$

* Case II: During -ve half cycle:-

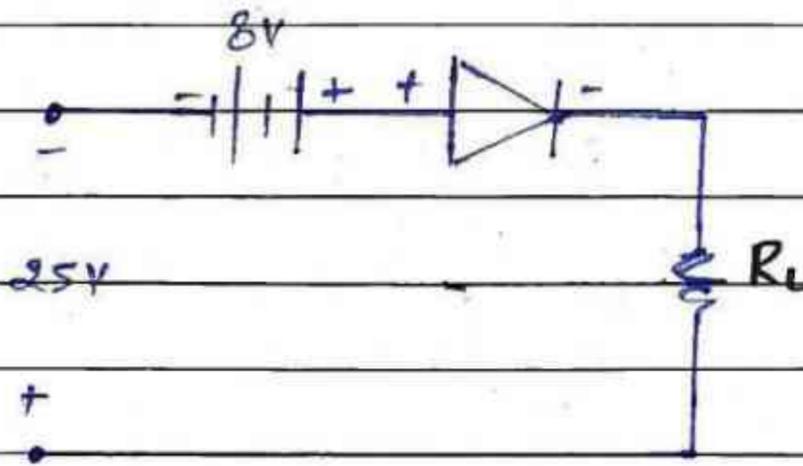


$V_i < -8V$	$V_i > -8V$
$D = ON$	$D = OFF$
$V_o \propto V_i$	$V_o = 0V$

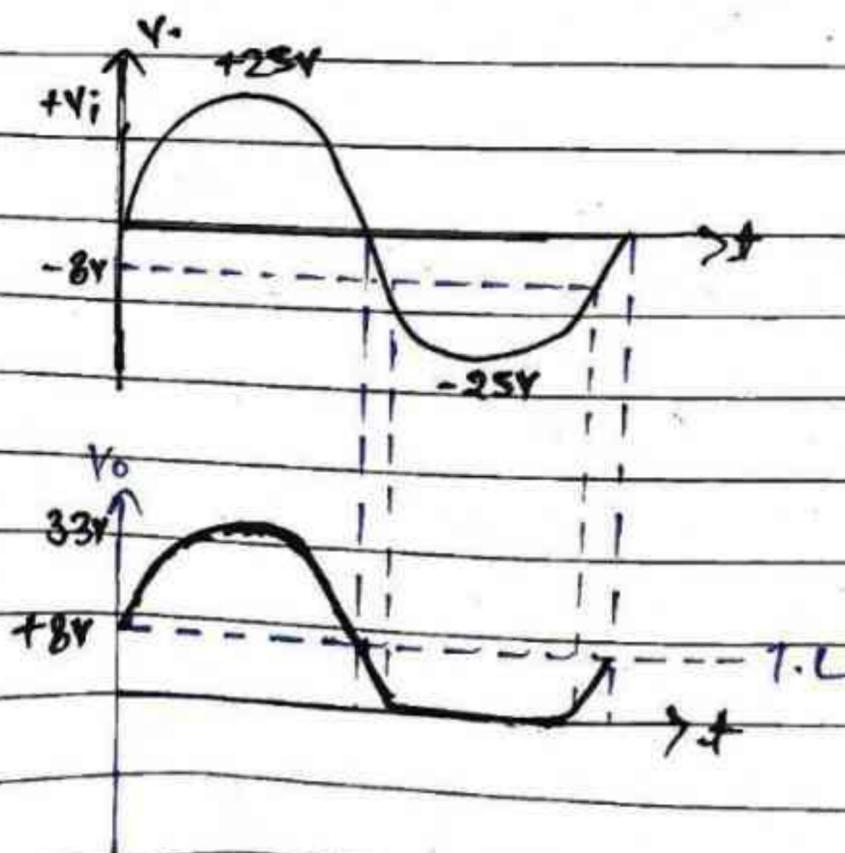

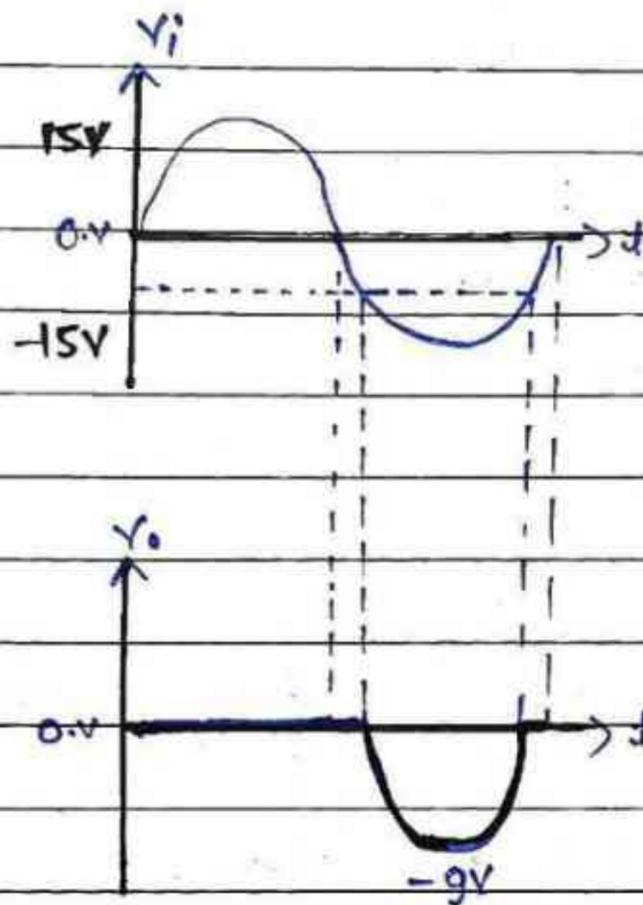

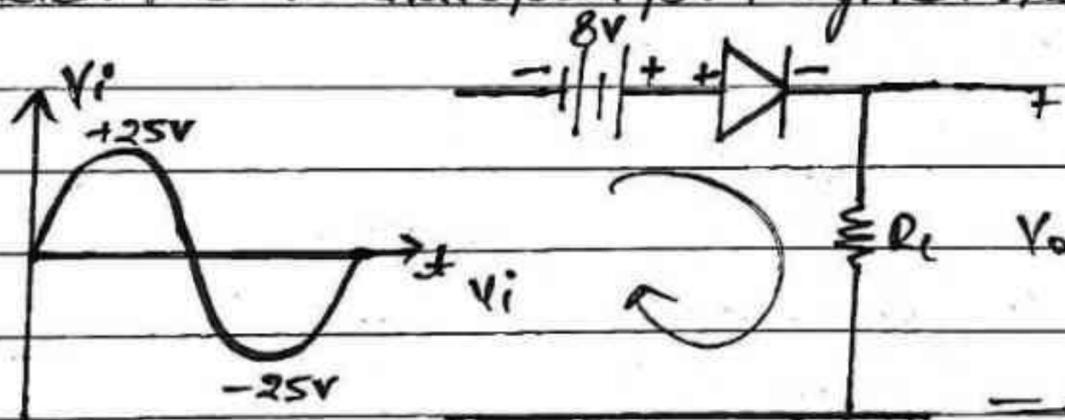Que:- Sketch the V_o waveform for the given network.



Soln

Transition level (TL):


$$8 - V_o = 0$$

$$+V_o = +8$$


$$V_o = 8$$

$$\therefore \boxed{T.L = 8V}$$

Case I: During +ve half cycle:

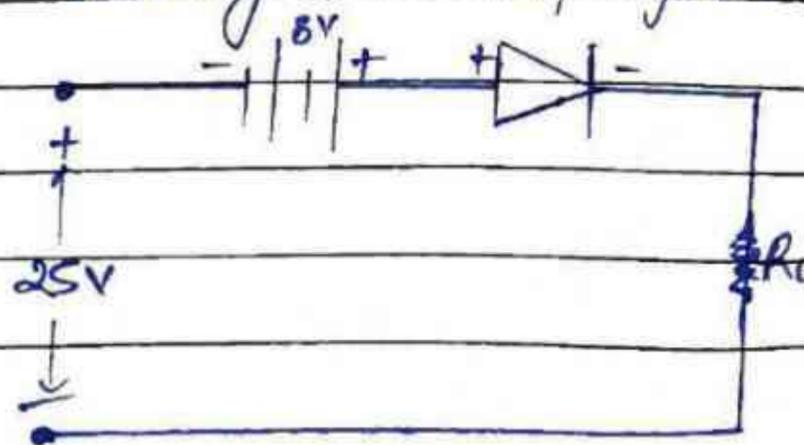


* Case I: During half cycle ^(+ve)

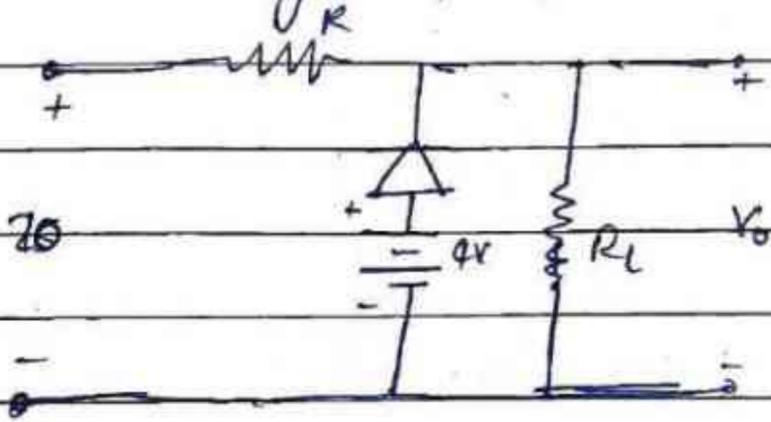


$V_i < 4V$	$V_i > 4V$
$D = ON$	$D = OFF$
$4 - V_0 = 0$	$V_0 = V_i$
$V_0 = 4$	


* Case II: During (-ve) half cycle

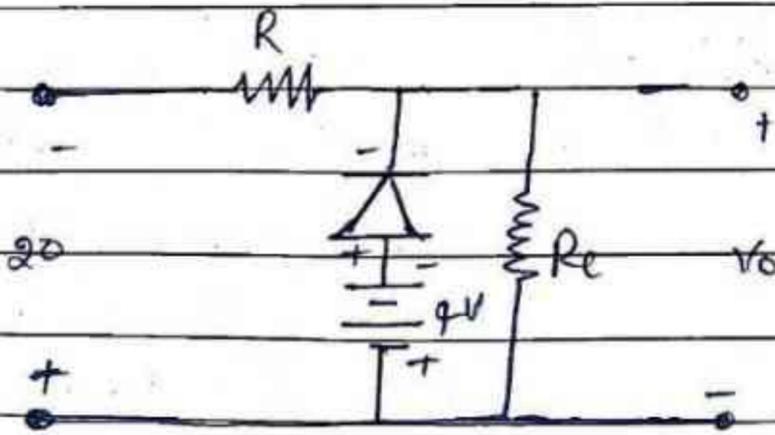

Using KVL
 $4 - V_0 = 0$
 $V_0 = 4$

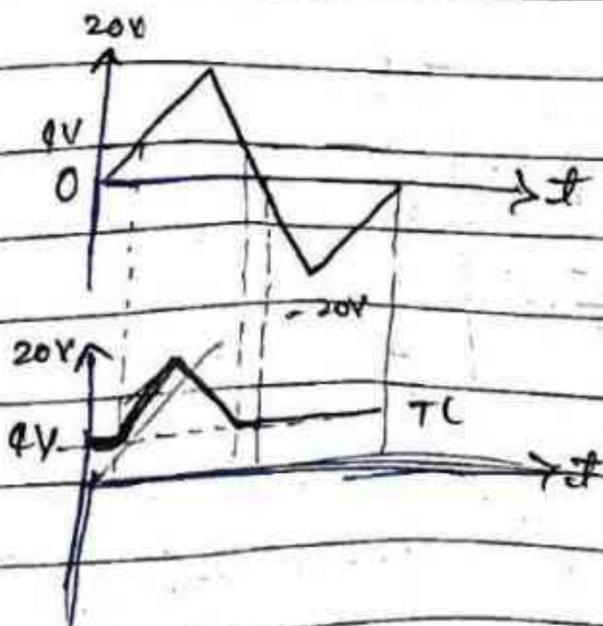



Case II: During -ve Half Cycle

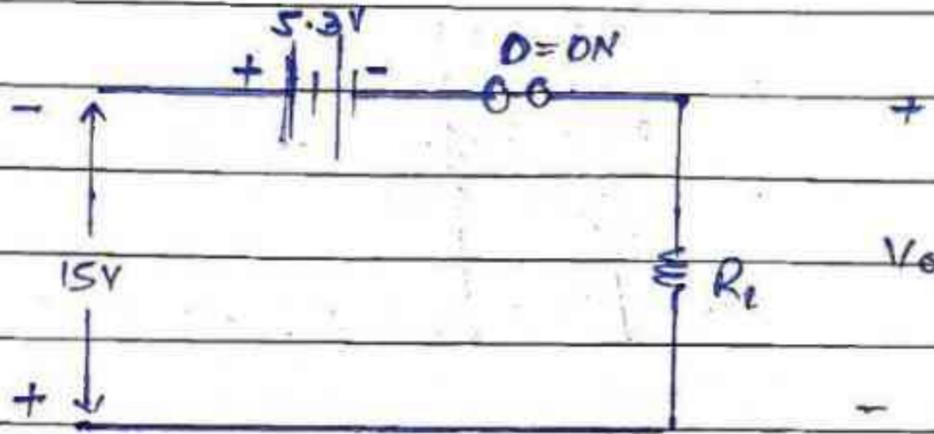

using KVL



$$15 + V_o + 5.3 = 0$$

$$V_o = -20.3$$

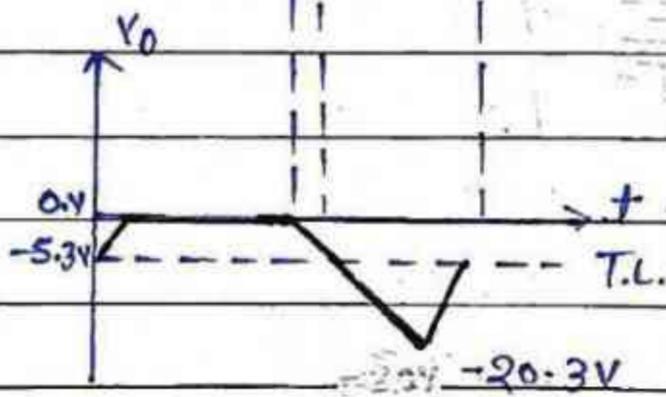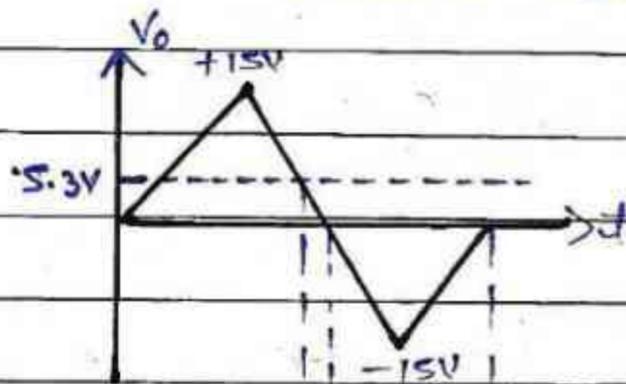

SI-sem
2020-21
Q.8-
2cd/cip

Ans

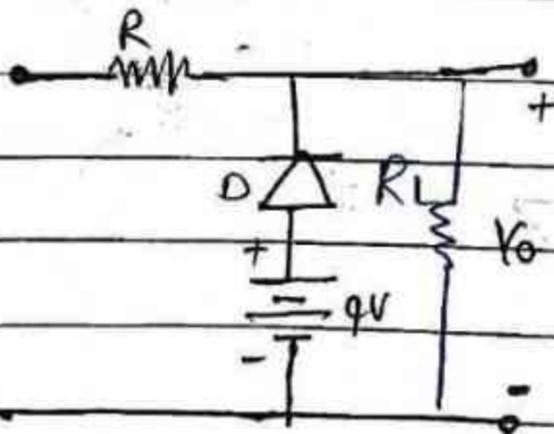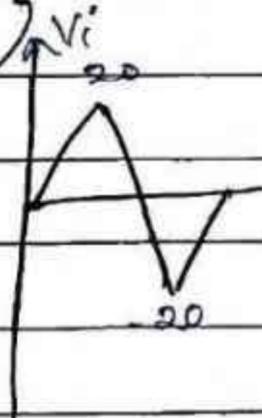


50/7

Transition level (T.L)


$$4 - V_o = 0$$

$$V_o = 4$$

$$T.L = 4V$$

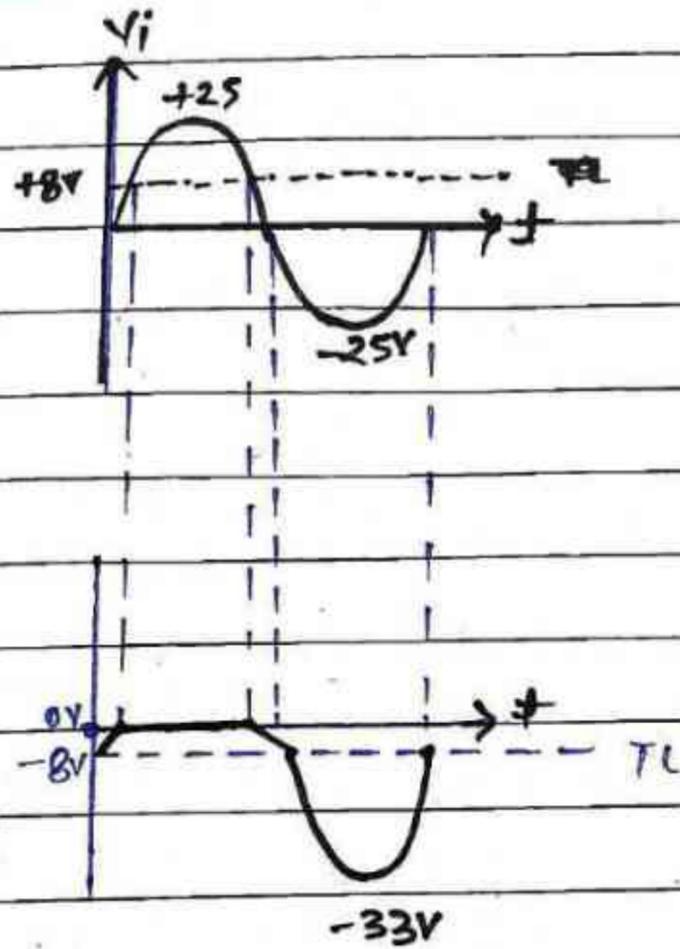

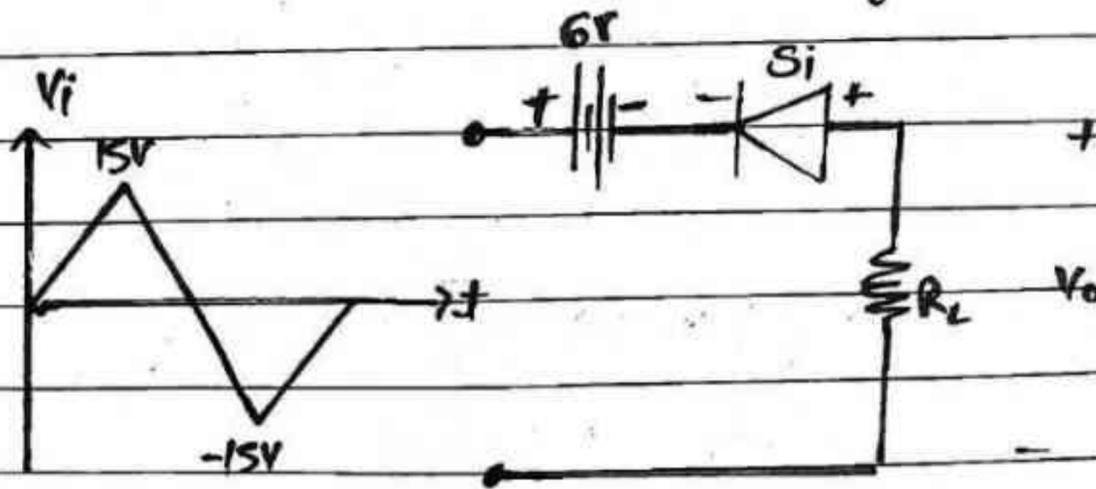
Ques :- Sketch the V_o waveform for the given network.



Soln

Transition level (T.L.) :-
 $V_o = -5.3V$
 $\therefore T.L. = -5.3V$

* Case 1: During +ve Half cycle:-

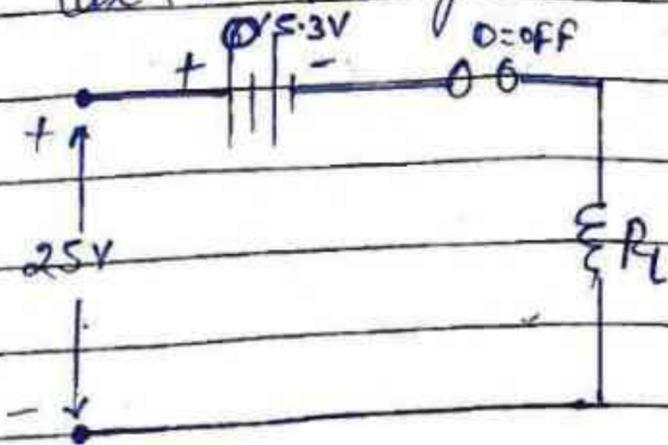

$V_i < 5.3V$	$V_i > 5.3V$
$D = ON$	$D = OFF$
$V_o = V_i$	$V_o = 0V$