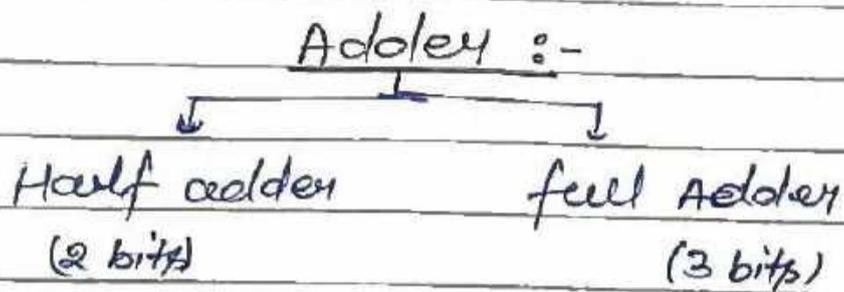


UNIT - II

(1)



Half adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$0+0=0$$

$$0+1=0$$



$$1+0=1$$

$$1+1=0 \text{ with carry } 1$$

$$S = \bar{A}B + A\bar{B}$$

$$S = A \oplus B$$

$$C = AB$$

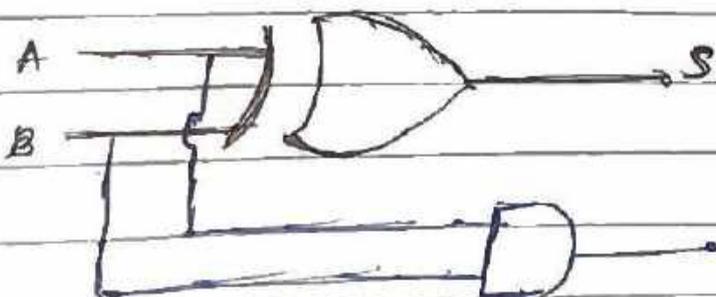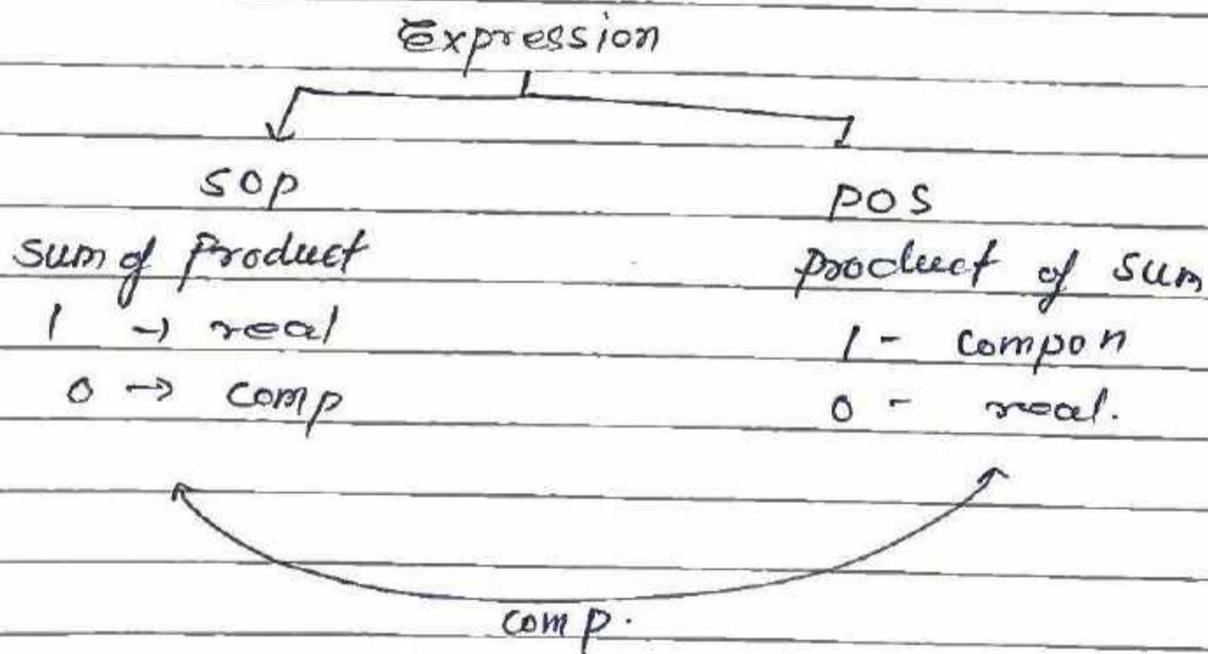

(2)

Full adder

A	B	C _{in}	S	Co _{ut}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$S = C_{in}(\bar{A}B + A\bar{B}) + \bar{C}_{in}(A\bar{B} + \bar{A}B)$$

$$S = C_{in}(A \oplus B) + \bar{C}_{in}(A \oplus B)$$

$$S = C_{in}(\bar{A} \oplus \bar{B}) + \bar{C}_{in}(A \oplus B)$$

$$\text{let } A \oplus B = X$$

$$S = C_{in} \bar{X} + \bar{C}_{in} X$$


$$S = X \oplus \bar{C}_{in}$$

$$S = A \oplus B \oplus C_{in}$$

$$Co_{out} = \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$Co_{out} = C_{in}(\bar{A}B + A\bar{B}) + AB(\bar{C}_{in} + C_{in})$$


$$Co_{out} = C_{in}(A \oplus B) + AB$$

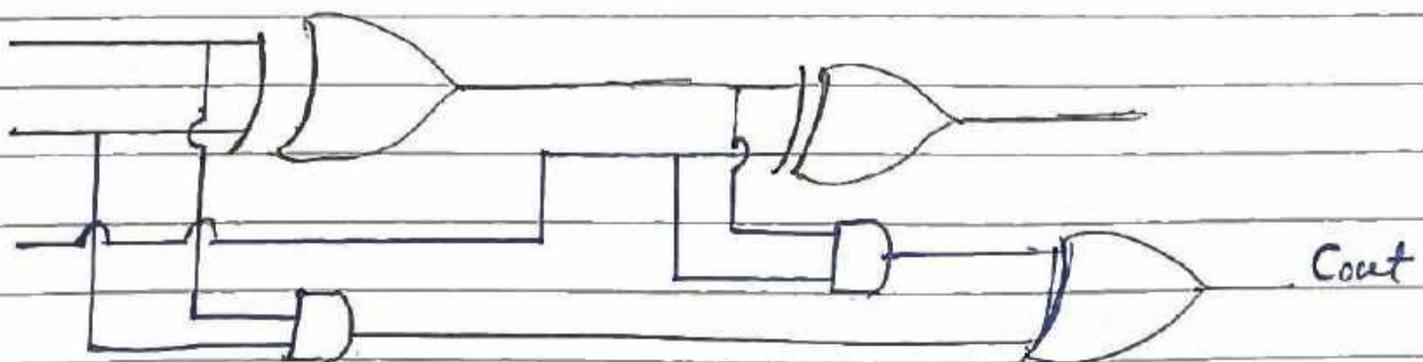

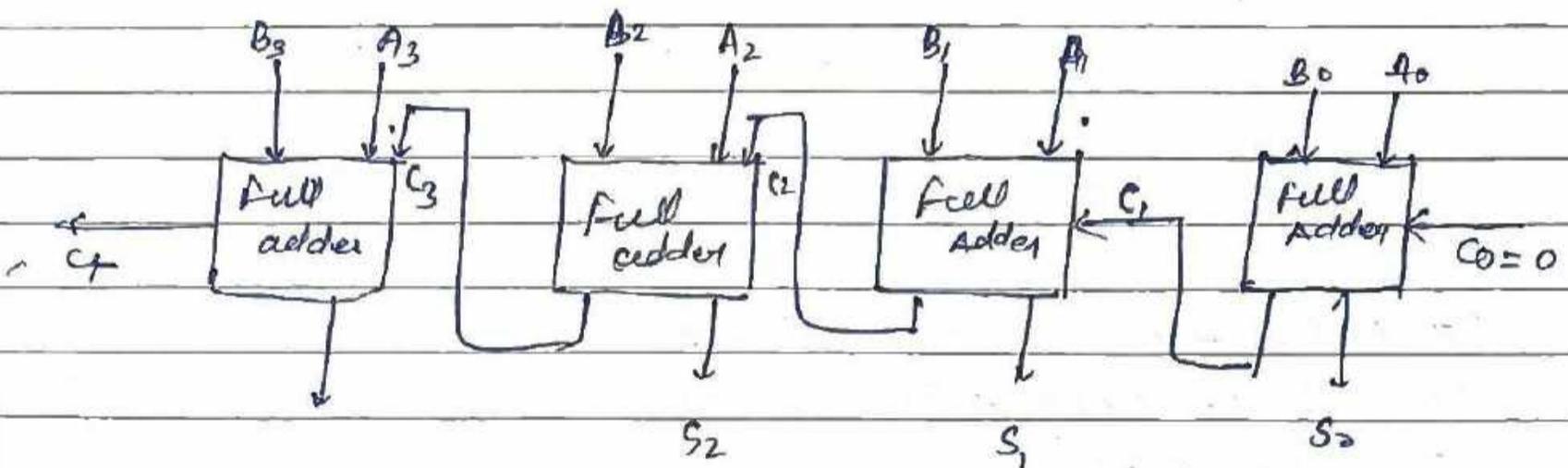(9)

Parallel Adder / Ripple Adder / Binary Adder.

$$\begin{array}{r} C_3 \quad C_2 \quad C_1 \quad C_0 \\ A_3 \quad A_2 \quad A_1 \quad A_0 \\ + \quad B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline C_4 \quad S_3 \quad S_2 \quad S_1 \quad S_0 \end{array}$$



Look Ahead Carry Adder :-


- ① To overcome the problem of excessive delay in ripple carry order adder a fast adder known as look ahead carry adder can be designed.
- ② In this adder the carry in for various stages can be generated directly by the logic expression.
- The general method for designing fast adder is to reduce the time required to form carry signal.
- It uses logic gates to look at lower order bits of the data to see if a higher order carry is to be generated. It uses two functions

① Carry Generate

② Carry Propagate.

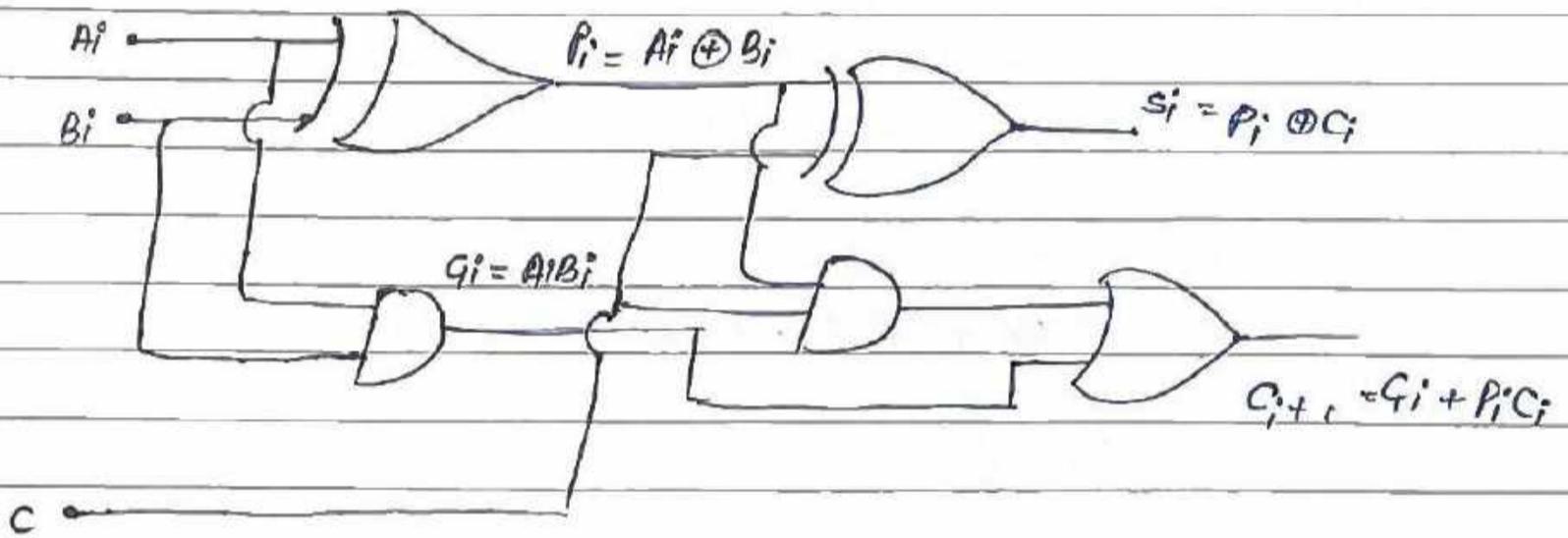(4)

- Following figure shows the full adder circuit used to add the operand bits in the highest j th column.



- From the given circuit P_i and G_i are given by $A_i \oplus B_i$ and $A_i B_i$ respectively. The output of full adder that is sum and carry can be defined as

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

- G_i is known as carry generate signal. A carry C_{i+1} is generated whenever $G_i = 1$, regardless of input carry.
- P_i is known as carry propagate signal, whenever $P_i = 1$ the input carry is propagated to the output carry.
- The Boolean expression for the carry output of various stages can be written as follows.

6

$$C_{i+1} = G_i + P_i C_i \quad \text{--- (1)}$$

$$i=0 \quad C_1 = G_0 + P_0 C_0 \quad \text{--- (1)}$$

$$i=1 \quad C_2 = G_1 + P_1 C_1$$

$$C_2 = G_2 + P_1 (G_0 + P_0 C_0)$$


$$C_2 = G_1 + G_0 P_1 + P_0 P_1 C_0 \quad \text{--- (2)}$$

$$i=2 \quad C_3 = G_2 + P_2 C_2$$

$$C_3 = G_2 + P_2 (G_1 + G_0 P_1 + P_0 P_1 C_0)$$

$$C_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + P_0 P_1 P_2 C_0 \quad \text{--- (3)}$$

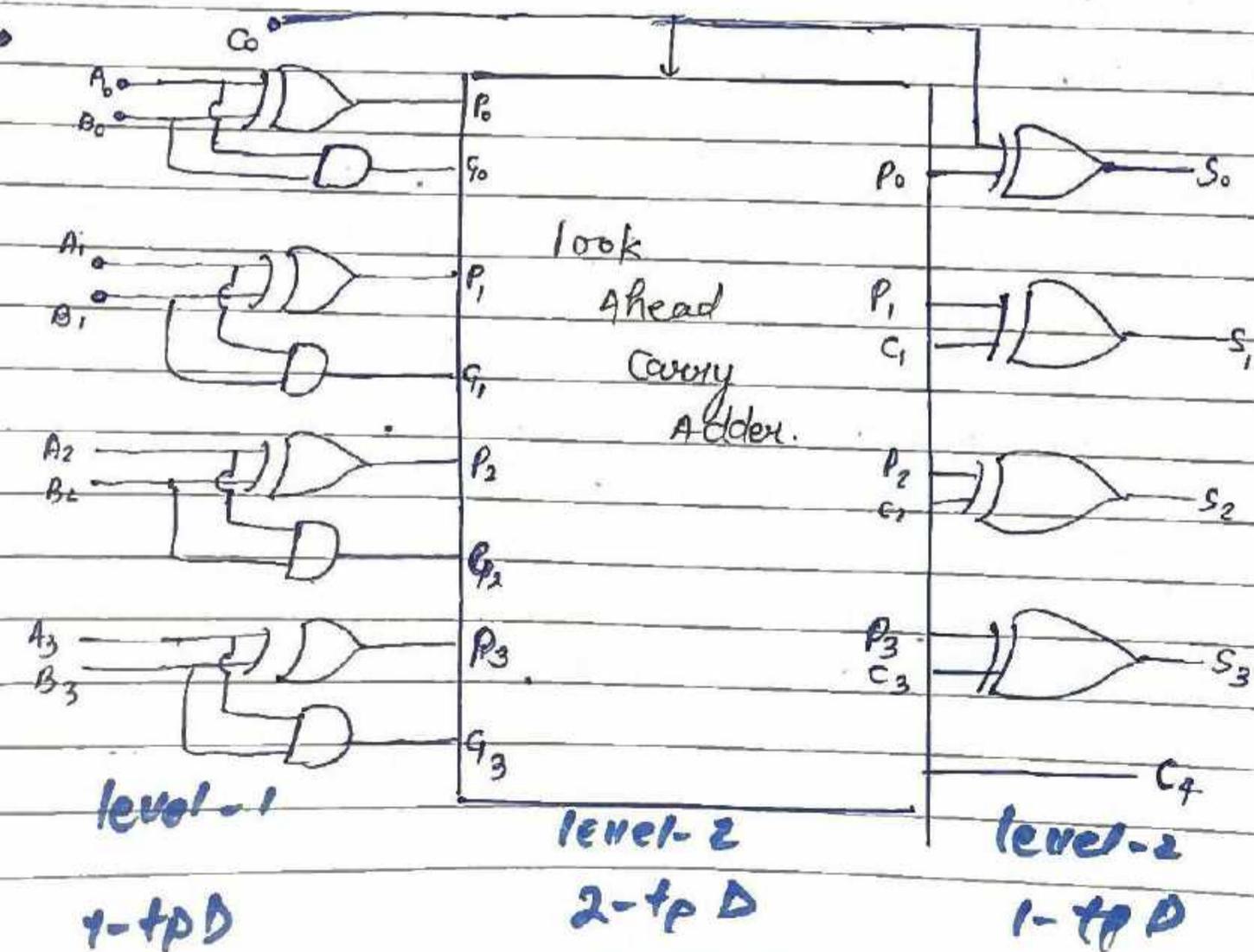- From the above expression each carry signal is expressed as a direct SOP function rather than its preceding carry signal



(6)

- The four bit carry look ahead adder consist of three level of logic.
- In the first level it generates all the P & G signal and it provides $1-t_p D$.
- In the second level it carry look ahead ~~adder~~ adder consist of four ~~to~~ (four) 2 level implementation circuit logic. It generates carry signal C_1, C_2, C_3, C_4 as defined by the upper expression and it provides a $2-t_p D$ time delay.
- In the third level four X-OR gate generates the sum ($S_i = P_i \oplus G_i$) and it provides $1-t_p D$ time delay.
- Therefore the total time delay of look ahead carry adder is $4-t_p D$.

④

Binary Multiplication (Unsigned number):-

As compare to addition and subtraction multiplication is the complex operation whether perform in hardware or software. For multiplication of unsigned binary

several important observation can be make.

They are. ① Multiplication involves the generation of partial product one for each digit in the multiplier. These partial product are then some to produce the final product.

② The partial product are easily defined when the multiplier width is zero the partial product is zero.

(iii) The total product is produced by summing the partial product. For this operation each successive partial product is shifted one position to the left related to the preceding partial product.

iv) The multiplication of n^{th} bit width binary result in a product of upto 2^n bits in length.

So the product of two (four bit) number fits into 8 bits

5) In the binary system of multiplication of the multiplicand by one bit of the multiplier is easy.

If the multiplier bit is one, the multiplicand is enter in the appropriate position added to the partial product

ex

1101 → Multiplicand (M)


1011 → Multiplier (Q)

1101

1101x

xx

9

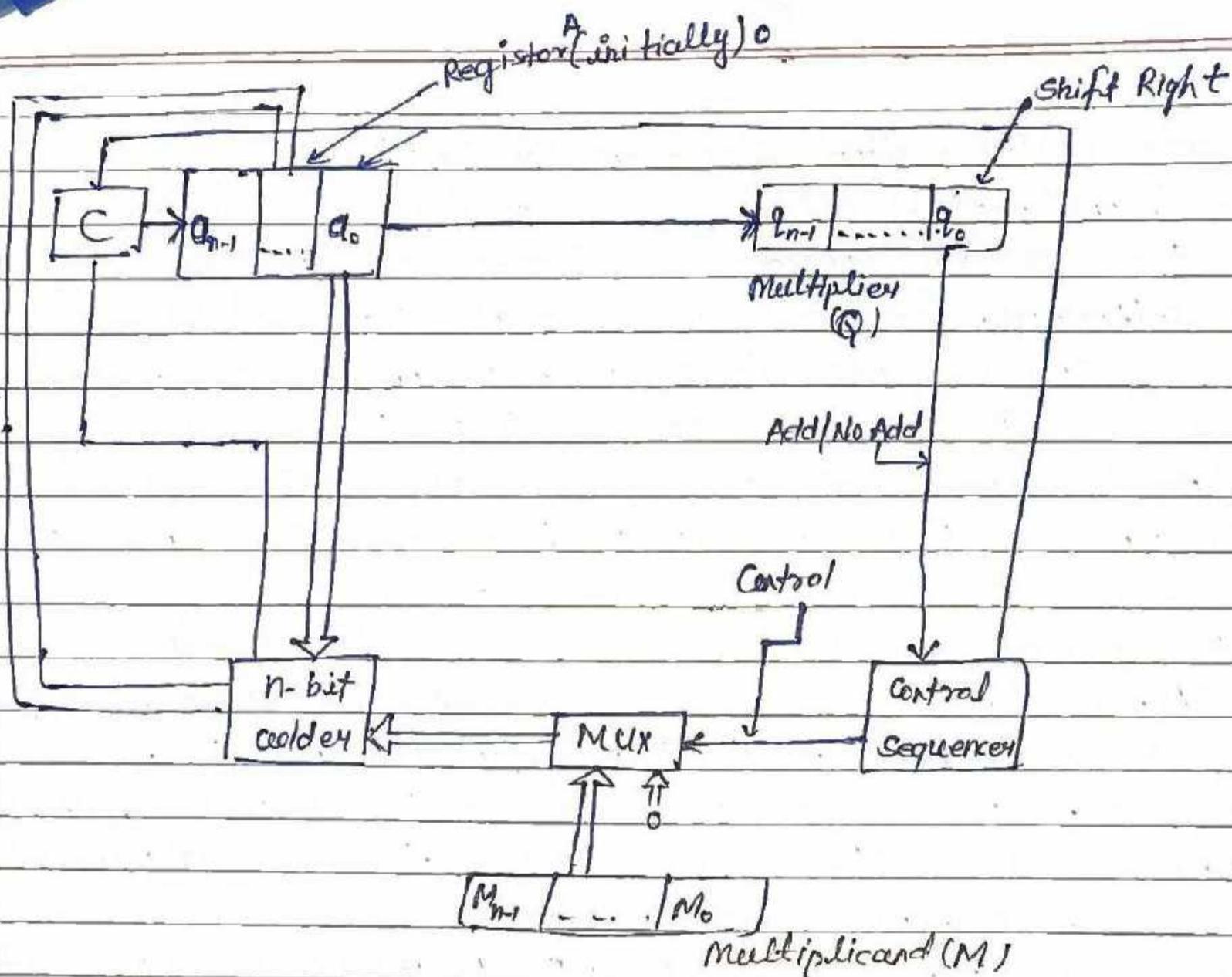

The operation of multiplier is as follow.

- ① Control sequencer reads the bit of the multiplier one at a time. If q_0 is one then the multiplicand is added to A register and the result is store in A register with the cap C bit use for overflow.
- ② Then all of the bits of the C, A, Q register are shifted to the write one bit ~~store~~^{so} that C bit goes in a_{n-1} , a_0 goes q_{n-1} , and q_0 is lost.
- ③ If q_0 is zero than no addition is perform, just right shifting is done. This process is repeated for each bit of the original multiplier.

C	A	Q	M	Initial value.
0	0000	1011	1101	Initial value.
0	1101	1011	1101	Add } First shift } cycle
0	0110	1101	1101	
1	0011	1101	1101	Add } Second shift } cycle
0	1001	1110	1101	
0	0100	1111	1101	Add } Third cycle
1	0001	1111	1101	Add } Fourth shift } cycle.
0	1000	1111	1101	

Que =

C	A	Q	M	
	0000	1100	1001	Initial Value
0	1001	1100	1001	Add } First cycle shift }
0	0100	1110	1001	
0	0010	0111	1001	Add } Second cycle
0	1011	0111	1001	
0	0101	1011	1001	Add } Third cycle
0	0010	0111	1001	
0	1011	0111	1001	
0	0101	1011	1000	

1101
 1101

 1011
 1011

 0000
 1101

 111001


①

11101 → M
10011 → Q

e	A	Q	M	
0	0000	1001	1100	Initial Value
0	1100	1001	1100	Add } Shift } First Cycle
0	0110	0100	1100	
0	0011	0010	11000	Second - Cycle
0	0001	1001	1100	Third - Cycle
0	1101	1001	1100	
0	0110	1100	1100	Add } Shift } Fourth cycle.

Q_{new} = 11101
10011


e	A	Q	M	
	00000	10011	11101	
0	11101	10011	11101	Add } Shift } → First cycle
0	01110	11001	11101	
1	11010	11001	11101	Add } Shift } → second cycle
0	10101	00111	11101	
0	01010	11110	11101	Add } - Third cycle
0	00101	01111	11101	Add } - Fourth cycle
1	00010	01111	11101	Add } Shift } → Fifth cycle
0	10001	00111	11101	

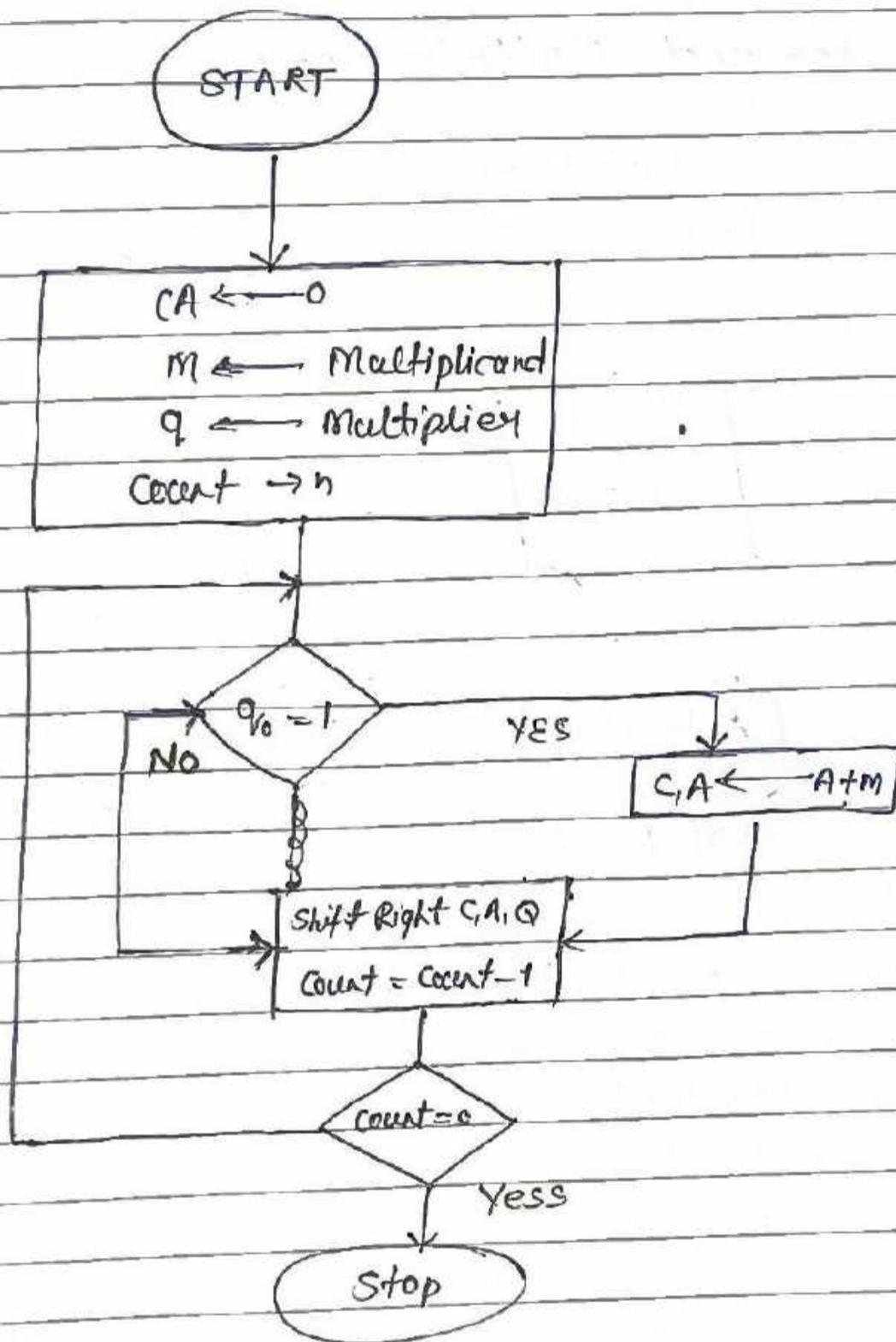

Flow chart for unsigned Binary No.


(13)

Signed operand Multiplication :-

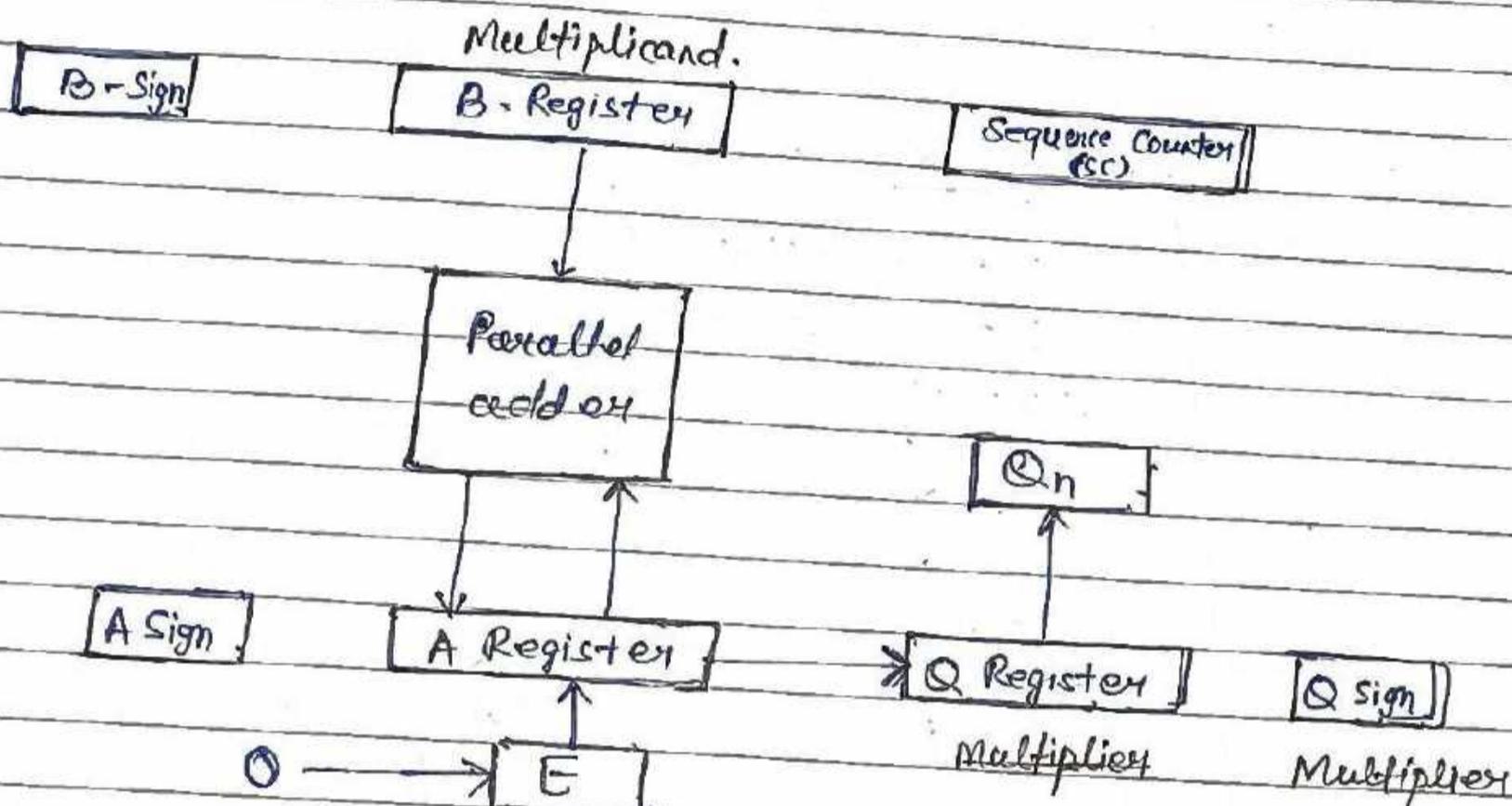

1. The sign of the product is determined from the sign of the multiplicand and multiplier. If they are alike, the sign of the product is positive; else, it is negative.
2. Two registers, B and Q, are used to store the multiplicand and multiplier, respectively.
3. Register A is used to store the partial product during multiplication.
4. Sequence counter register (SC) is used to store the number of bits in the multiplier.
5. To store the sign bits of registers B, A, and Q, 3 flip-flops are required. (A sign, B sign, Q sign).
6. Flip-flop E is used to store the carry bit generated during partial product addition.
7. Parallel adder is used in calculating the partial product. That is, it performs the addition required.

Flow chart of Multiplication :-

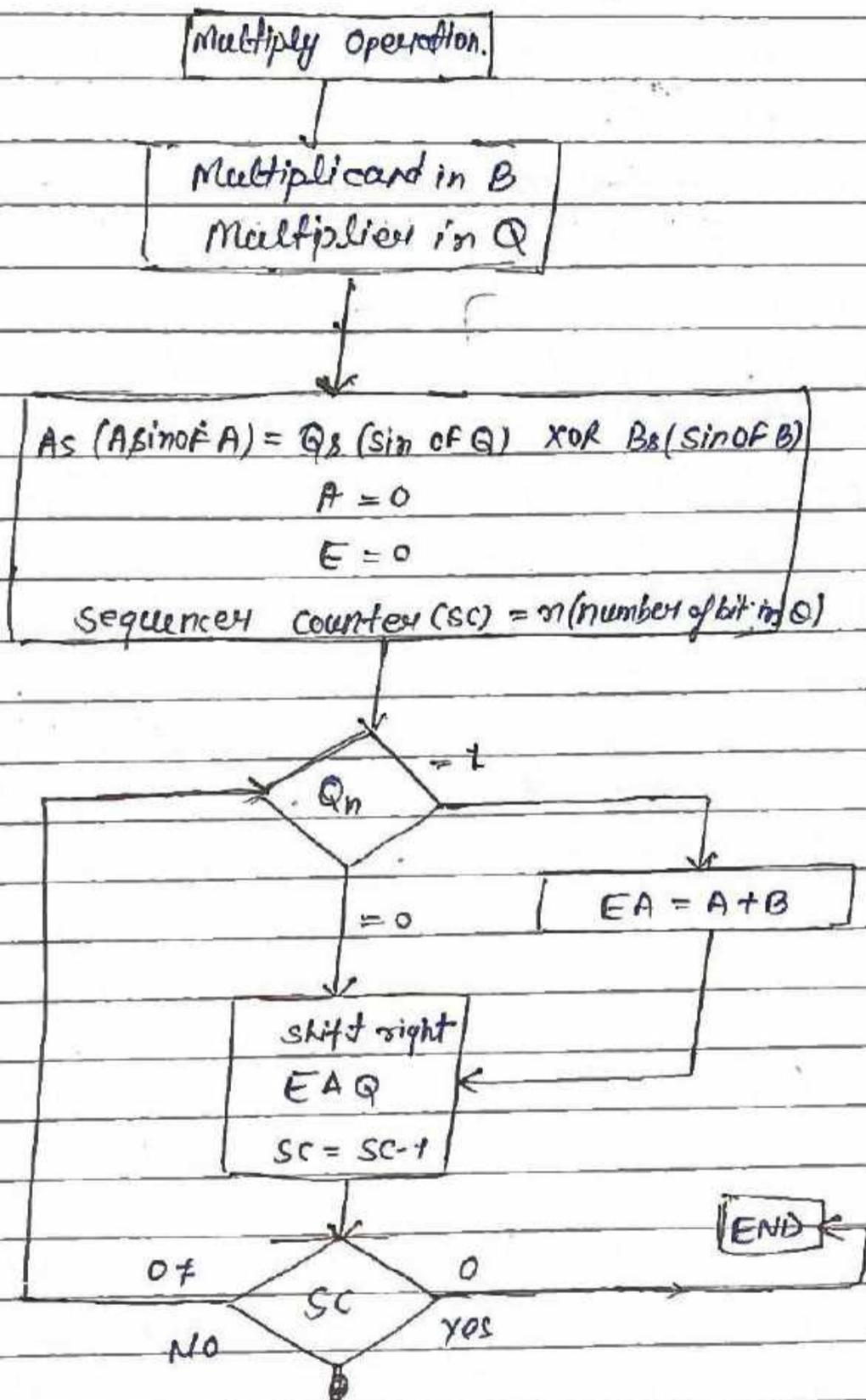

- 1.) Initially multiplicand is stored in B register and multiplier reg^s is stored in Q register.
- 2.) Sign of Register B and Q are compared using X-OR function. (that is if the both sign are alike output is zero else one) and output is store

in register A.

- 3.) Initially zero is assign to register A and E. sequence counter is initialized with value n where n is the number of bits in the multiplicand.
- 4.) Now LSB of Multiplier is checked, if it is 1 add the content of register A with multiplicand and result is assign in A register with carry bit in flip-flop E. Content of E, A, Q is shifted to right by one position.
- 5.) If Q_n equal to zero only right shift of operation on content of E, A, & Q is perform.
- 6.) Content of sequence counter is decremented by one.
- 7.) Check the content of sequence counter. If it is zero end the process and the final product is present in register A and Q. If it is not zero repeat the process.

Multiplicand = 10111

Multiplier = 10011

B = 10111	E	A	Q	SC	
	0	00000	10011	100	
10111	0	10111	10011	100	Add
01011	0	01011	11001		Shift
100010	1	00010	11001	010	Add
	0	10001	01100		Shift
10111	0	01000	10110	000	Shift
00100	0	00100	01011	001	Shift
11011	0	11011	01011	000	Add
	0	01101	10101		Shift

↳ Final Product

Multiplicand = 10011
Multiplier = 11001

$$\begin{array}{r} 10011 \\ 00010 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} 10011 \\ 01010 \\ \hline 11101 \end{array}$$

B = 10011	E	A	Q	SC	
	0	00000	11001	101	
	0	10011	11001	100	Add
	0	01001	11100		Shift
	0	00100	11110	011	Shift
	0	00010	01111	010	Shift
	0	10101	01111	001	Add
	0	01010	10111		Shift
	0	11101	10111	000	Add
	0	01110	11011		Shift

Final Product

421
110

Multiplicand = 101110
Multiplier = 100110

B = 101110

$$\begin{array}{r} 101110 \\ 010111 \\ \hline 100100 \end{array}$$

$$\begin{array}{r} 101110 \\ 001000 \\ \hline 110110 \end{array}$$

E	A	Q	SC	
0	000000	100110	110	
0	110110	100110	101	Add
0	011011	010011		Shift
0	000000	010011	101	Shift
0	101110	010011	0100	Add
0	010111	001001		Shift
1	000101	001001	011	Add
0	100010	100100		Shift
0	010001	010010	010	Add Shift
0	001000	101001	001	Shift
0	110110	101001	000	Add
0	011011	010100		Shift

011011

(17)

$$\begin{array}{r}
 15 \rightarrow 01101 \\
 10010 \\
 + \\
 \hline
 00111
 \end{array}$$

$$\begin{array}{r}
 1029 \\
 128 \\
 \hline
 896
 \end{array}$$

Booth Algorithm:- The algorithm that is used to multiply binary integer in sign 2's complement form is called booth multiplication algorithm

- It works on the principle that string of zero (0) in the multiplier require no addition but just shifting and string of one (1) in the multiplier from bit weight 2^k to 2^m can be treated as $2^k (2^{k+1} - 2^m)$

example:- binary number 001110 \rightarrow +14

It has string of one from 2^3 to 2^1 (that is $k=3$ and $m=1$) then the number can be represented as

$$2^{2+1} - 2^1$$

$$2^4 - 2^1$$

$$14$$

Therefore the multiplication $M \times 14$ where M is the multiplicand and 14 is the multiplier can be done as $M \times 2^4 - (M \times 2^1)$

Thus the product can be obtain by shifting the binary multiplicand M four time to the left and subtracting M shifted left once.

$$\begin{array}{l}
 10 \rightarrow M \\
 \times 14 \rightarrow Q
 \end{array}
 \quad
 \begin{array}{l}
 00001010 \\
 \text{4th} \rightarrow 00010100 \\
 \text{2nd} \rightarrow 00101000 \\
 \text{3rd} \rightarrow 01010000 \\
 \text{4th} = 10100000
 \end{array}$$

$$\begin{array}{r}
 \text{Multiplicand} \quad 00001010 \\
 \text{1st shift} \quad 00010100 \\
 \text{2's} \quad 11101011 \\
 \quad + \\
 \hline
 11101100
 \end{array}$$


$$\begin{array}{r} 10100000 \\ + 11101100 \\ \hline \oplus 10001100 \end{array}$$

$$\begin{array}{r} 128 \quad 64 \quad 21 \\ \hline 10001100 \end{array}$$


- Booth algorithm require examination of the multiplier bits and shifting of the partial product.
- Trial to the shifting the multiplicand may be added to the partial product or subtractive for the partial product or left unchanged according to following rule
 - The partial product does not change when the multiplier bit is identical to previous multiplier bit
 - The multiplicand is subtracted from the partial product upon encountering the least significant one (1) in the string of one in the multiplier
 - The multiplicand is added to the partial product upon encountering the first zero (provided that there was a previous one) in a strings of zeros in the multiplier.

The hardware implementation of booth algorithm requires the register configuration as shown below.

(19)

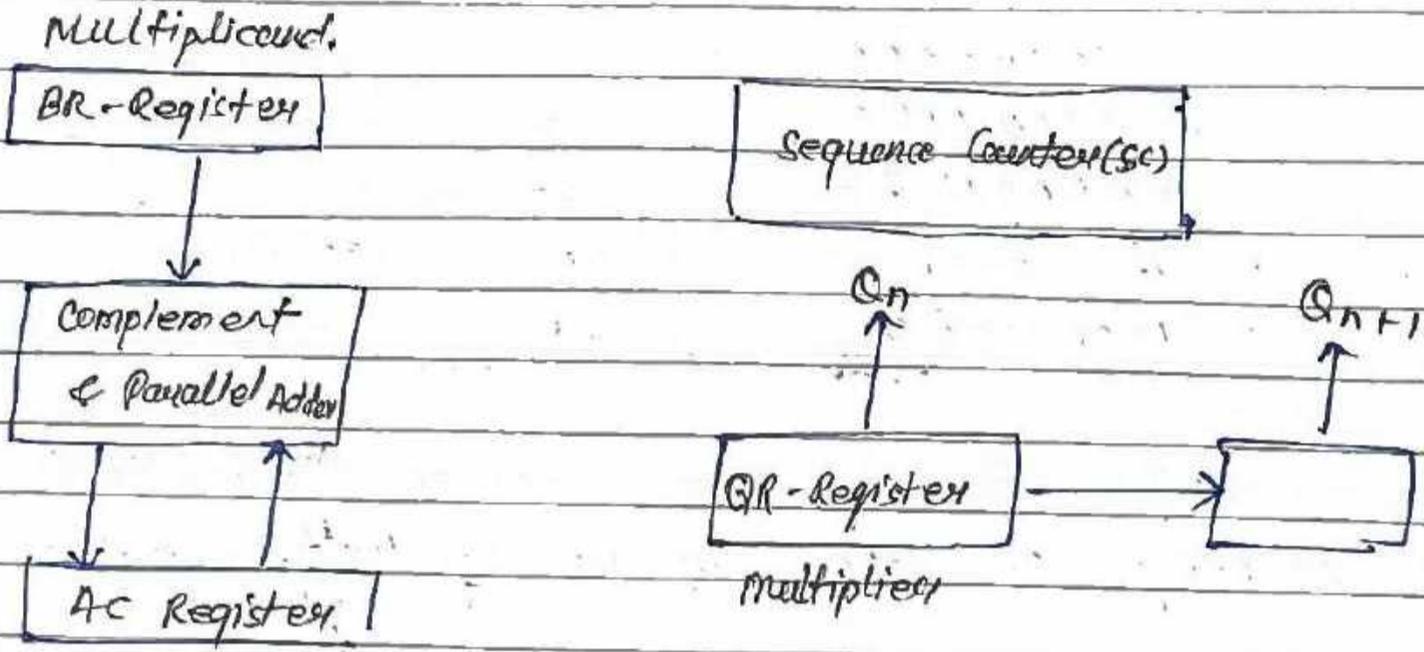

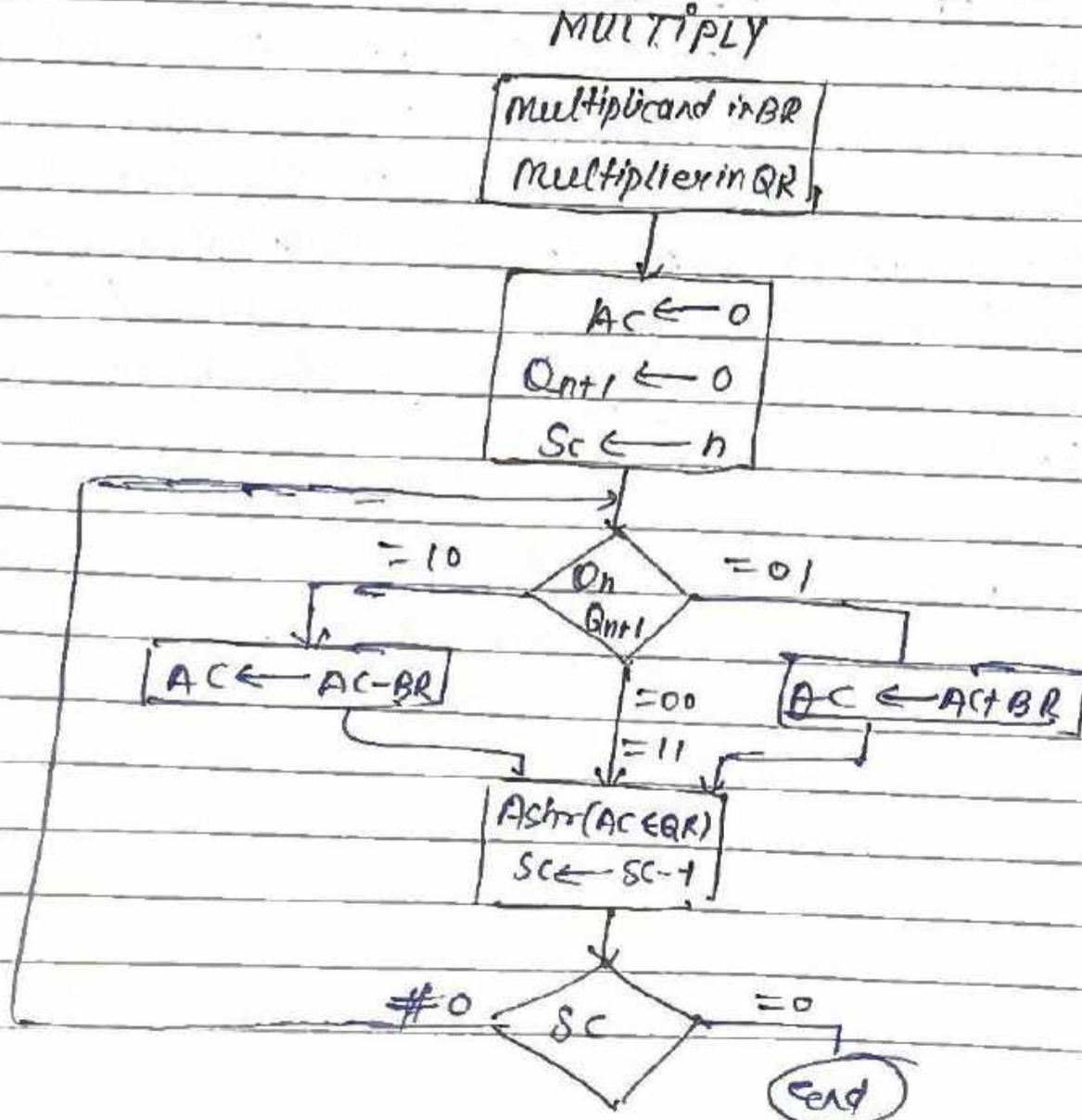An extra flip-flop Q_{n+1} is include to QR register to facilitate a double bit inspection of the multiplier. The flow chart for booth algorithm is shown below.



(20)

$$\begin{array}{r} 15 \quad 1101 \\ \rightarrow \quad 0010 \\ \rightarrow \quad -11 \\ \hline -12 \quad 10011 \end{array} \qquad \underline{00011}$$

$$\begin{array}{r} 1110 \\ 0111 \\ \hline 00101 \end{array}$$

Ques-01: Multiplier 7x3 using booth Algorithm.

Qn Qn+1	Multiplicand Br	AC	Multiplicand BR	Qn+1	SC
	BR → 0111				
	Initial	0000	0011	0	100
10	AC ← AC - BR AC ← AC + (-BR)	1001	0011	0	011
	Arsh	1100	1001	1	
11	Arsh	1110	0100	1	010
10	AC ← AC + BR	0101	0100	1	001
	Arsh	0010	1010	0	
00	Arsh	0001	0101	0	000

AC & BR = 00010101

$$\begin{array}{r} 01101 \\ 10010 \\ \hline 10011 \end{array}$$

$$\begin{array}{r} 0111 \\ 1000 \\ \hline 1 \end{array}$$

Ques - Multiply 15x-13 using booth algorithm.


-BR = 10001

Qn Qn+1	Multiplicand BR → 0111	AC	Multiplicand (BR)	Qn+1	SC
	BR → 0111				
	Initial	00000	10011	0	101
10	AC ← AC - BR AC ← AC + (-BR)	10001	10011	0	100
	Arsh	11000	11001	1	
11	Arsh	11100	01100	1	011
01	AC ← AC + BR	01001 01101	01100		010
	Arsh	00101	10110	0	
00	Arsh	00010	11011	0	001
10	AC ← AC - BR	10011	11011	0	000
	Arsh	11001	11101	1	
11	Arsh	11100	11110		

BR = 0111
 1000
 BR → 1001

01010
 10101
 + 10001

 011010

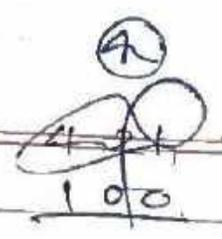

-7 x 3 -BR → 10010111

Qn	Qn+1	Multiplicand (BR)	AC	Multiplier (BR)	Qn+1	Sc
		BR → 0001	0000	0011	0	100
10		AC → AC + BR	1001 0111	0011	0	011
		Arsh	001100	1001	1	
11		Arsh	0001110	0100	1	010
01		AC → AC + BR	1010	1100	1	001
		Arsh	1100	0110	0	
00		Arsh	1110	0011	0	000

-BR → 0111
 -15 x -12

Qn	Qn+1	Multiplicand (BR)	AC	Multiplier (BR)	Qn+1	Sc
		BR → 10001	00000	10100	0	101
00		Initial	00000	01010	0	100
00		Arsh	00000	00101	0	011
010		AC ← AC - BR	01111	00101	0	010
		AC ← AC + (-BR)	00111	10010	1	
01		Arsh	11000	10010	1	001
		AC ← AC + BR	11100	01001	0	
10		Arsh	01011	01001	0	000
		AC ← AC + (-BR)	00101	10100	1	
		AC ← AC - BR				
		Arsh				

- Ques - 01) -14 x -9
- Ques - 02) -13 x 9
- Ques - 03) -18 x -19
- Ques - 04) +8 x -12.

Ques-01

- 14 x 9

- BR = 01110

	Multiplicand (BR)	AC	Multiplicator (QR)	Q _{n+1}	SC
	BR → 10010				
	Initial	00000	10111	0	101
10	AC ← AC - BR AC ← AC + (-BR)	01110	10111	0	100
	Arsh	00111	01011	1	
11	Arsh	00011	10101	1	011
11	Arsh	00001	11010	1	010
01	AC ← AC + BR	10010	11010	1	001
	Arsh	11001	01101	0	
10	AC ← AC - BR AC ← AC + (-BR)	00111	01101	0	000
	Arsh	00011	10110		

AC & QR = 00011110

Ques-02

- 13 x 9

- BR → 01101
Multiplicand (BR)
BR → 10011

	Multiplicand (BR)	AC	Multiplicator (QR)	Q _{n+1}	SC
	BR → 10011				
	Initial	00000	01001	0	101
10	AC ← AC - BR AC ← AC + (-BR)	01101	01001	0	100
	Arsh	00110	10100	1	
01	AC ← AC + BR	11001	10100	1	011
	Arsh	11100	11010	0	
00	Arsh	11110	01101	0	010
10	AC ← AC - BR AC ← AC + (-BR)	01011	01101	0	001
	Arsh	00101	10110	1	000
01	AC ← AC + BR	00010	11011	0	
	AC ← AC - BR	11000	10110	1	000
	Arsh	11100	01011	1	

AC & QR = 1110001011

- BR → 010010

On → On+1	Multiplicand (BR)	AC	Multiplier (BR)	On+1	SC
	BR → 101110	000000	101101	0	100
Initial	Initial	000000	101101	0	110
10	AC ← AC + (-BR)	010010	101101	0	101
	Arsh	001001	010110	1	
01	AC ← AC + BR	110111	0010110	1	100
	Arsh	111011	101011	0	
10	AC ← AC + (-BR)	101101	101011	0	011
	Arsh	110110	110101	1	
11	Arsh	111011	011010	1	010
01	AC ← AC + BR	101001	011010	1	001
	Arsh	110100	101101	0	
10	AC ← AC + (-BR)	000110	101101	0	000
	Arsh	000011	010110	0	

Que-5 BX-12

- BR → 11000

	Multiplicand (BR)	AC	Multiplier (BR)	On+1	SC
	BR → 01000		10100		
	Initial	000000	10100	0	101
00	Arsh	000000	01010	0	100
00	Arsh	000000	00101	0	011
10	AR → AC + (-BR)	11000	00101	0	010
	Arsh	11100	00010	1	
01	AC → AC + BR	00100	00010	1	001
	Arsh	00010	00001	0	
10	AC ← AC + (-BR)	11010	00001	0	000
	Arsh	11101	00000	1	
<p>AC & BR = <u>1110100000</u></p>					

-18 → 101110

-19 → 101101

(24)

AC → AC + BR
AC → AC + (-BR)

-BR → 010010

Op. Out	Multiplicand (BR)	AC	Multiplicand (BR)	Out	SC
	BR → 101110				
	Initial	000000	101101	0	110
10	AC ← AC + (-BR)	010010	101101	0	101
	Arsh	001001	010110	1	
01	AC ← AC + BR	110111	010110	1	100
	Arsh	111011	001011	0	
10	AC ← AC + (-BR)	001101	001011	0	011
	Arsh	000110	101011	1	
11	Arsh	000011	010101	1	010
01	AC ← AC + BR	110000	010101	1	001
	Arsh	111000	001001	0	
10	AC ← AC + (-BR)	001010	001001	0	000
	Arsh	000101	000100		

-BR = 010010

BR → 101110

Initial

		000000	101101	0	110
10	AC ← AC + (-BR)	010010	101101	0	101
	- Arsh	001001	010110	1	
01	AC ← AC + BR	110111	010110	1	100
	Arsh	111011	101011	0	
10	AC ← AC + (-BR)	001101	101011	0	011
	Arsh	000110	110101	1	
11	Arsh	000011	011010	1	010
01	AC → AC + BR	110001	011010	1	001
	Arsh	111000	101101	0	
10	AC → AC + (-BR)	001010	101101	0	000
	Arsh	000101	010110	1	

Integer Division:- An algorithm which deal with two integer $A \div B$, compute their remainder and quotient is called division algorithm.


Division algorithm are of two types

- ① Slow Algorithm
- ② ~~Best~~ or Restoring Algorithm
 - Ⓐ Non-Restoring algorithm

③ Fast Algorithm.

- Ⓐ Newton Raphson algorithm
- Ⓑ SRT Division Algorithm.
 - "Sweeney, Robertson and Touchey"

Restoring division algorithm:-

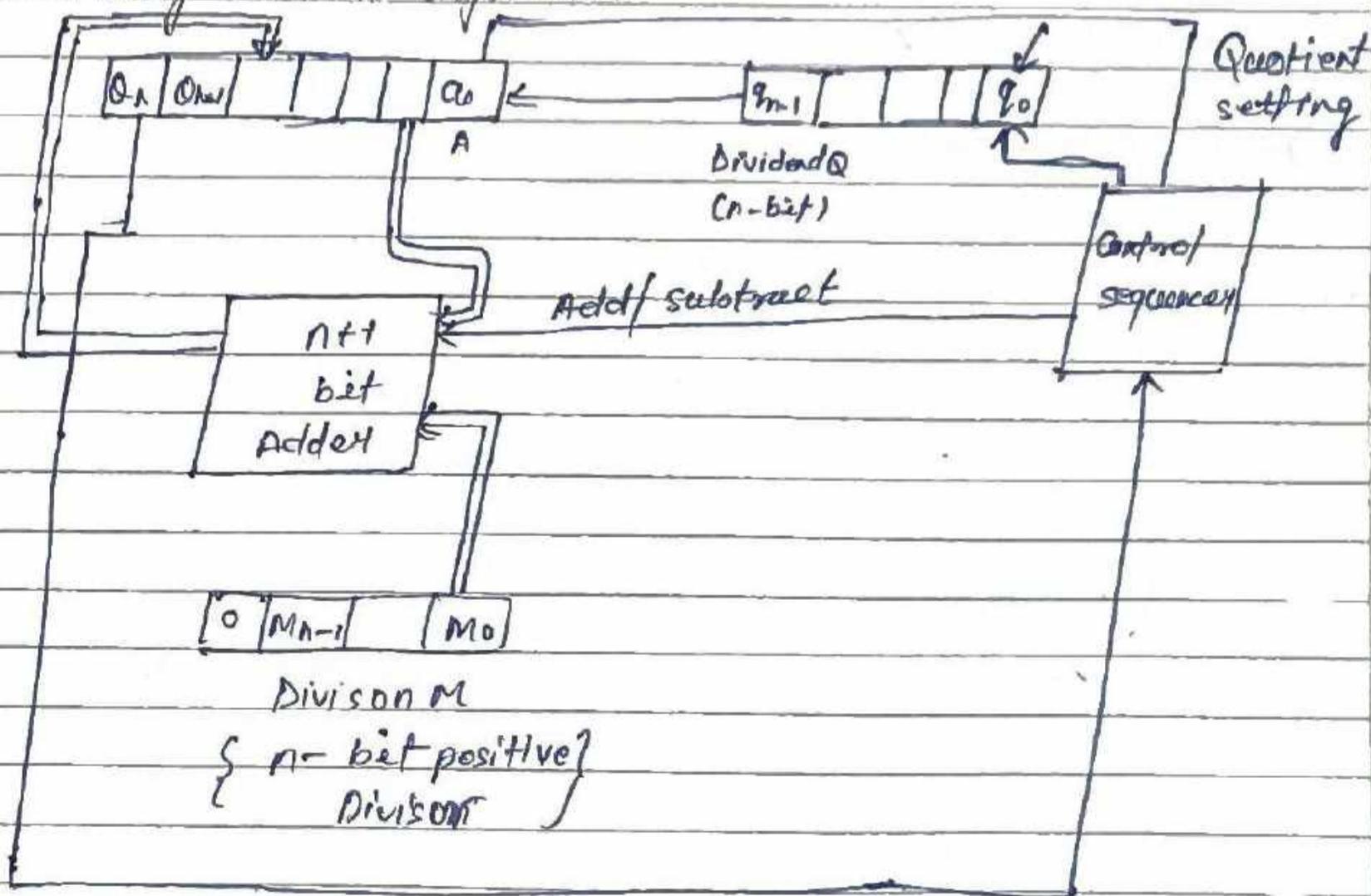


- Restoring algorithm is a traditional algorithm for performing binary division.
- In restoring division we restore the partial remainder after each subtraction if the result is negative (MSB is 1).
- above logic circuit shows the arrangement that implements the restoring division algorithm
- An n bit positive dividend is loaded into register N and an n bit positive divisor is loaded into register q at the start of operation.
- Register A is set said set to zero.
- After a division is completed the n bit quotient is in register q and the remainder is in Register A .

Flow Chart :-

(27)

Flow Chart :-

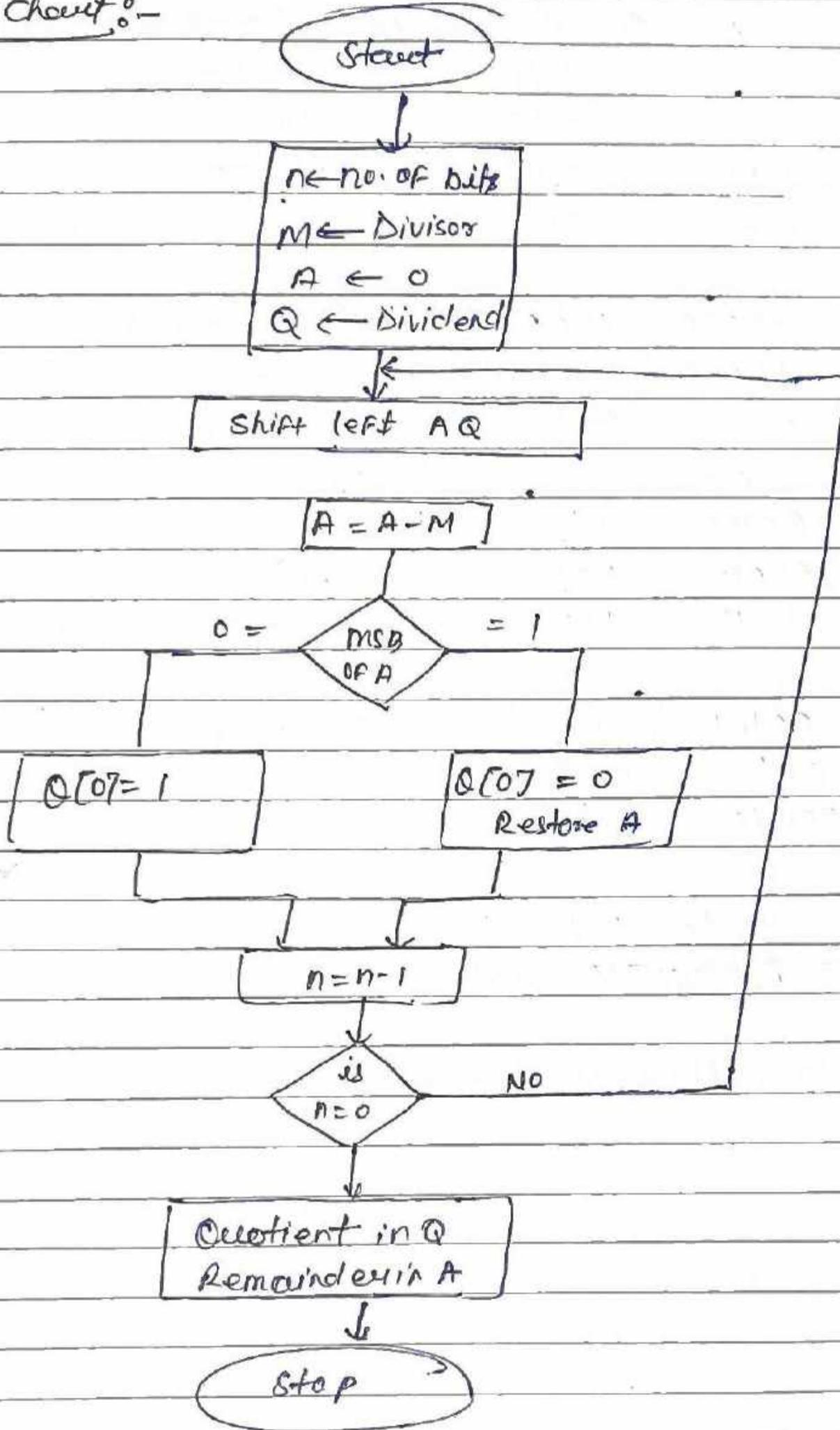

n	M	A	Q	Q	Action / comments
4	0001	00000	1011		Initialization
		00001	011?		Shift left A, Q
		11110	011?		$A = A \oplus (-M)$
		00001	0110		MSB of A = 1, Restore A, $Q[0] = 0$
3					$n = n - 1$
		00010	110?		Shift left A, Q
		11111	110?		$A = A \oplus (-M)$
		00010	1100		MSB of A = 0, Restore A, $Q[0] = 0$
2					$n = n - 1$
		00101	100?		Shift left A, Q
		00010	100?		$A = A \oplus (-M)$
		00010	1001		MSB of A = 0, $Q[0] = 1$
1					$n = n - 1$
		00101	001?		Shift left A, Q
		00010	001?		$A = A \oplus (-M)$
0		00010	0011		MSB of A = 0, $Q[0] = 1$

Quotient in Q = 0011
 Remainder A = 00010

Ques Divide 7 by 3 using Restoring Method.

$$\begin{array}{r} 0001 \\ 1101 \\ \hline 1111 \end{array}$$

$-M \Rightarrow 1101$

$$\begin{array}{r} 0011 \\ 1101 \\ \hline 000 \end{array}$$

~~7x3~~

$$\begin{array}{r} 0011 \\ 1111 \\ + 1101 \\ \hline 10000 \end{array}$$

(29)

$$\begin{array}{r} 1101 \\ 0001 \\ \hline 1110 \end{array}$$

$$\begin{array}{r} 0001 \\ 1101 \\ \hline 1110 \end{array}$$

$$\begin{array}{r} 0010 \\ 1101 \\ \hline 1111 \end{array}$$

n	m	A	Q	Action / Comment
3	0011	0000	111	Initialize
2		0001	11?	Shift left A, Q
		1110	11?	AC + (-M)
		0001	110	MSB of A = 1 Restore A, Q[0] = 0 n = n - 1
1		0011	10?	Shift left A, Q
		0000	10?	AC + (-M)
		0000	101	MSB of A = 0 Q[0] = 1 n = n - 1
0		0001	01?	Shift left A, Q
		1110	01?	AC + (-M)
		0001	010	MSB of A = 1 Restore A, Q[0] = 0 n = n - 1
		0010	10?	Shift left A, Q
		1111	10?	AC = A + (-M)
		0010	100	MSB of A = 1 Restore A, Q[0] = 0 n = n - 1


X

$$A = 0001$$

$$Q = 010$$

$$\begin{array}{r} 0011 \\ 1100 \\ + 1 \\ \hline 1101 \end{array}$$

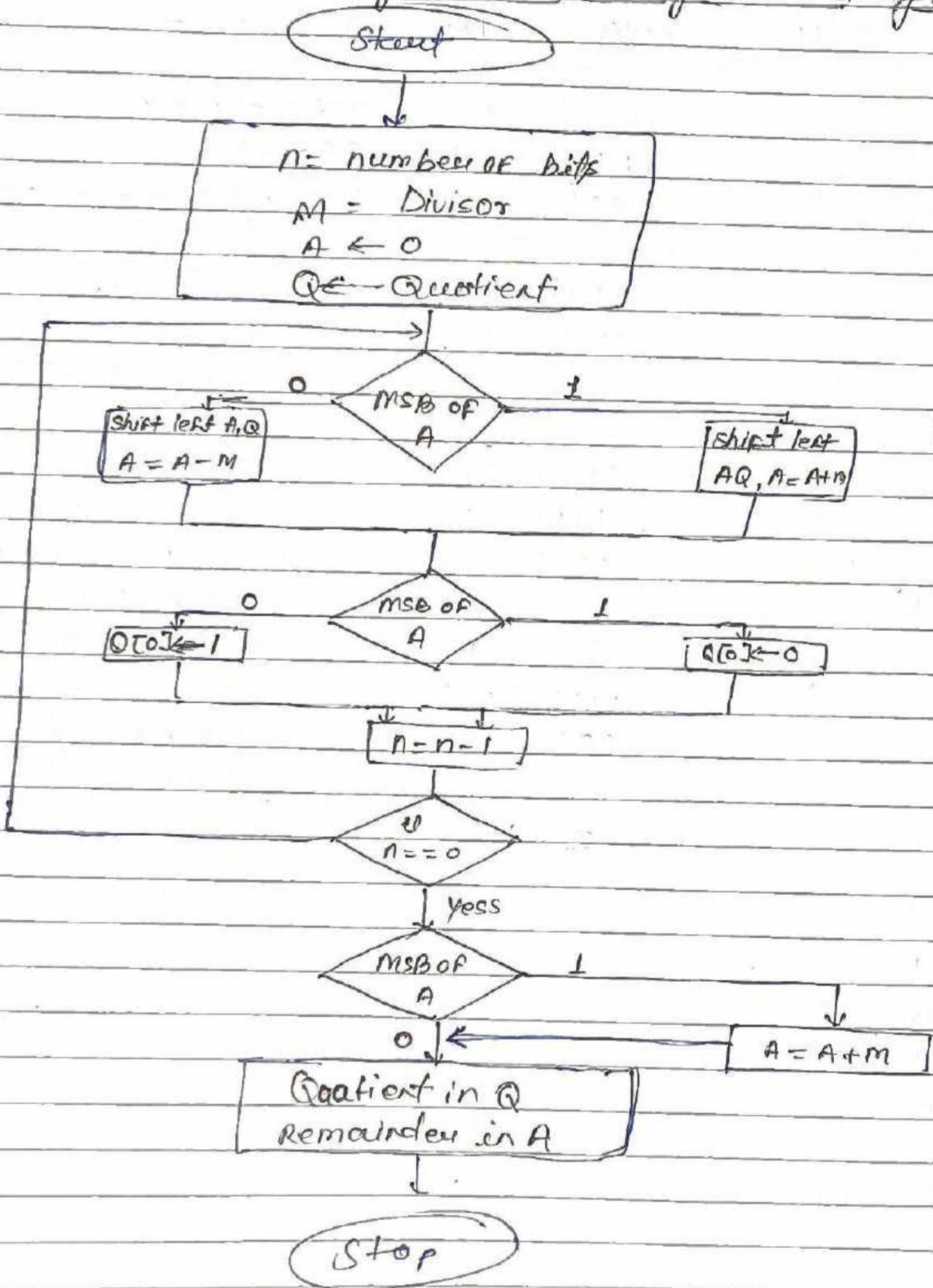Flow chart for integer division using Non-restoring Method.



(31)

$$\begin{array}{r} 00011 \\ 11111 \\ \hline 00010 \end{array}$$

$$\begin{array}{r} 00001 \\ 11101 \\ \hline 11110 \end{array}$$

$$\begin{array}{r} 00101 \\ 11101 \\ \hline 00010 \end{array}$$

$$\begin{array}{r} 11110 \\ + 00011 \\ \hline 00001 \end{array}$$

$$\begin{array}{r} 11100 \\ 00011 \end{array}$$

Ques - 11 by 3 :-

-m -> 11101

n	M	A	Q	Action/Comment.
4	00011	00000	1011	Initialization.
		00001	011?	Shift left A, Q
		11110	011?	A = A - M
		11110	0110	MSB of A = 1, Q[0] = 0
3				n = n - 1
		11100	110?	Shift left A, Q
		11111	110	A = A + M
		11111	1100	MSB of A = 1, Q[0] = 0
2				n = n - 1
		11111	100?	Shift left A, Q
		00010	100?	A = A + M
		00010	1001	MSB of A = 0, Q[0] = 1
1				n = n - 1
		00101	001?	Shift left A, Q
		00010	001?	MSB A = A - M
		00010	0011	MSB of A = 0, Q[0] = 1
0				n = n - 1

Quotient = 0011

Remainder = 00010.

$$\begin{array}{r} 1101 \\ + 0011 \\ \hline 10000 \end{array}$$

$$\begin{array}{r} 0001 \\ 1101 \\ \hline 1110 \end{array}$$

$$\begin{array}{r} 1101 \\ \hline 0001 \\ 1101 \\ \hline 1110 \end{array}$$

(32)

$$\begin{array}{r} 1110 \\ 0011 \\ \hline 0001 \end{array}$$

Divide 7 by 3

- m = 1101

n	m	A	Q	Action / Comments
3	0011	0000	111	Initialization
		0001	011?	Shift left A, Q
		1110	011?	A = A - M
		1110	0110	MSB of A = 1 Q[0] = 0
2				n = n - 1
		1101	10?	Shift left A, Q
		0000	010?	A = A + M
		0000	101	MSB of A = 0 Q[0] = 1
1				n = n - 1
		0001	01?	Shift left A, Q
		1111	01?	A = A - M
		1110	010	MSB of A = 1 Q[0] = 0
0				n = n - 1
		0001	010.	A = A + M

Quotient \Rightarrow 010
 Remainder \Rightarrow 0001

- Ques-1 Divide 9 by 9
- Ques-2 Divide 11 by 5
- Ques-3 Divide 14 by 6
- Ques-4 Divide 16 by 7
- Ques-5 Divide 19 by 6

} Restoring and Non Restoring method.

33

①

Q = 9 ⇒ 1001

m = 7 ⇒ 00100

-m ⇒ 11100

Div 9 by 7

n	m	A	Q	Action / Comments
4	00100	00000	1001	Initialization
		00001	001?	Shift left A, Q
		11101	001?	A = A - m
3		11101	0010	MSB of A = 1 Q[0] = 0 n = n - 1
		11010	010?	Shift left A, Q
		11110	010?	A = A + m
		11110	0100	MSB of A = 1 Q[0] = 0 n = n - 1
2		11100	100?	Shift left A, Q
		00000	100?	A = A + m
		00000	1001	MSB of A = 0, Q[0] = 1 n = n - 1
1		00001	001?	Shift left A, Q
		11101	001?	A = A - m
		11001	0010	MSB of A = 1 Q[0] = 0 n = n - 1
0		00001	0010	A = A + m

Quotient in Q → 0010

Remainder in A → 00001

2

-m → 11011
Q = 11 → 1011
M = 5 → 00101

34

Divide 11 by 5 Non-Restoring method :-

-m → 11011

n	M	A	Q	Action / comment
4	00101	00000	1011	Initialization
		00601	011?	Shift left A, Q
		11100	011?	A = A + M
		11100	0110	MSB of A = 1, Q[0] = 0
3				n = n - 1
		11000	110?	Shift left A, Q
		11101	110?	A = A + M
		11101	1100	MSB of A = 1, Q[0] = 0
2				n = n - 1
		11011	100?	Shift left A, Q
		00000	100?	A = A + M
		00000	1001	MSB of A = 0, Q[0] = 1
1				n = n - 1
		00001	001?	Shift left A, Q
		11100	001?	A = A - M
		11100	0010	MSB of A = 1, Q[0] = 0
				n = n - 1
		00001	0010	A = A + M

Quotient Q = 0010

Remainder R = 00001

(3)

(35)

Ques-3 14 divide by 6
Non-Restoring

$$\begin{array}{r}
 Q = 14 \rightarrow 1110 \\
 M = 6 \rightarrow 00110 \\
 -M \quad 11010
 \end{array}$$

n	m	A	Q	Action / Comment
4	00110	00000	1110	Initialization
		00001	110?	Shift left A, Q
		11011	110?	A = A - M
		11011	1100	MSB OF A = 1 Q[0] = 0
3				n = n - 1
		10111	100?	Shift left A, Q
		11101	100?	A = A + M
		11101	1000	MSB OF A = 1 Q[0] = 0
				n = n - 1
		11011	000?	Shift left A, Q
		00001	000?	A = A + M
		00001	0001	MSB OF A = 0, Q[0] = 1
				n = n - 1
1		00010	0010?	Shift left A, Q
		11100	001?	A = A - M
		11100	0010	MSB OF A = 1, Q[0] = 0
				n = n - 1
		00010	0010	MSB OF A = 1 A = A + M

Quotient Q = 0010
 Remainder in A = 00010

Ques-4 Divide 16 by 7 Non storing Method.

Q = 16 → ~~101~~ 1110

M = 7 → 111 → 00111

-M → 00111 → 1's of M

Q's
11000
+1

11001

-M = 11001

n	M	A	Q	Action/Comments
4	00111	00000 00000	1110	Initialization
		00001	110?	Shift left A, Q
		11010	110?	A → A - M
		11010	1100	MSB of A = 1, Q[0] = 0 n = n - 1
3		11010	100?	Shift left A, Q
		11000	100?	A → A + M
2		11000	1000	MSB of A = 1, Q[0] = 0 n = n - 1
		11001 00000	000?	Shift left A, Q
		00000	000?	A → A + M
		00000	0001	MSB of A = 0, Q[0] = 1 n = n - 1
1		00000	001?	Shift left A, Q
		11001	001?	A → A + M
		11001	0010	MSB of A = 1, Q[0] = 0 n = n - 1
0				MSB of A = 1, A → A + M

6

37

19 by 6

Q = 19 -> 10111

M = 000110 -> -M -> 1's of M -> 111001 + 1

-M = 111010

-M -> 111010

n	M	A	Q	Action/Comments
5	000110	000000	10111	Initialization.
		000001	0111?	Shift left A, Q
		111011	0111?	A -> A - M
4		111011	01110	MSB of A = 1 Q[0] = 0 n = n - 1
		110110	1110?	Shift left A, Q
		111100	1110?	A -> A + M
		111100	11100	MSB of A = 1 Q[0] = 0 n = n - 1
3		111001	1100?	Shift left A, Q
		111111	1100?	A -> A + M
		111111	11000	MSB of A = 1 Q[0] = 0 n = n - 1
2		111111	1000?	Shift left A, Q
		000101	1000?	A -> A + M
		000101	10001	MSB of A = 0 Q[0] = 1 n = n - 1
1		001011	0001?	Shift left A, Q
		000101	0001?	A -> A - M
		000101	00011	MSB of A = 0 Q[0] = 1

$$\begin{array}{r} 11011 \\ + 1 \\ \hline 11000 \end{array}$$

$$\begin{array}{r} 11011 \\ + 1 \\ \hline 11000 \end{array}$$

X (30)

Restoring Method

9 by 9
 $Q = 9 \rightarrow 1001$
 $M = 4 \rightarrow 00100$
 $-M \rightarrow 11010$

n	m	A	Q	Action/Comment
4	00100	00000	1001	Initialization
		00001	001?	Shift left A, Q
		11011	001?	$A \rightarrow A - M$
		00001	0010	MSB of A = 1, restore A, $Q[0] = 0$
3				$n = n - 1$
		00010	010?	Shift left A, Q
		11100	010?	$A \rightarrow A - M$
		00010	0100	MSB of A = 1, restore A, $Q[0] = 0$
2				$n = n - 1$
		00100	100?	Shift left A, Q
		11110	100?	$A \rightarrow A - M$
		00100	1000	MSB of A = 1, restore A, $Q[0] = 0$
1				$n = n - 1$
		00100	000?	Shift left A, Q
		00011	000?	$A \rightarrow A - M$
		00011	0000	MSB of A = 0, $Q[0] = 1$
				$n =$

7

11 by 5 - M = 11011

(39)



n	M	A	Q	action / comments
4	00101	00000	1011	Initialization
	0	00001	011?	A - shift left A, Q
		11100	011?	A = A - M
		00001	0110	MSB OF A = 1 restore A, Q[0] = 0
3				n = n - 1
		00010	110?	Shift left A, Q
		11101	110?	A = A - M
		00010	01100	MSB OF A = 1 restore A, Q[0] = 0
2				n = n - 1
		000101	100?	Shift left A, Q
		00000	100?	A = A - M
		00000	1001	MSB OF A = 0, Q[0] = 1
1				n = n - 1
		00001001?		Shift left
		11100	001?	A = A - M
		00001	0010	MSB OF A = 1 restore A, Q[0] = 1

8 19 by 6

-M = 11010

n	M	A	Q	Action / comments
4	00110	00000	1110	Initialization
		00001	110?	Shift left A, Q
		11011	110?	A = A - M
		00001	1100	MSB OF A = 1, Q[0] = 0 restore A
3				n = n - 1
		00011	100?	Shift left A, Q
		11101	100?	A = A - M
		00011	1000	MSB OF A = 1, Q[0] = 0 restore A
2				n = n - 1

(9)

(41)

000010	0001?	Shift left A, Q
111011	0001?	A = A - M
000010	00010	MSB of A = 0 Q[0] = 0 restore A
		n = n - 1

(10)

19 by 6 -m = 111010

n	M	A	Q	Action / Comments
5	000110	000000	10011	Initialization
		000001	0011?	Shift left
		111011	0011?	A = A - M
		000001	00110	MSB of A = 1 Q[0] = 1 restore -A
4				n = n - 1
		000010	0110?	Shift left A, Q
		111100	0110?	A = A - M
		000010	01100?	MSB of A = 1 Q[0] = 0 restore = A
3				n = n - 1
		000100	1100?	Shift left A, Q
		111110	1100?	A = A - M
		000100	11000	
2				n = n - 1
		001001	1000?	Shift left A, Q
		000011	1000?	A = A - M
		000011	10001	MSB of A = 0 Q[0] = 1
1				n = n - 1
		000111	0001?	Shift left A, Q
		000001	0001?	A = A - M
		000001	00011	MSB of A = 0 Q[0] = 1
0				n = n - 1

IEEE (Floating Point Representation)

- ① Single Precision (32 bits)
- ② Double Precision (64 bits)

() Any base \longrightarrow ()₂ \longrightarrow Normalised Form.

Single Precision.

① (54)₁₀


2	54	0
2	27	1
2	13	0
2	6	0
2	3	1
	1	

$$\begin{aligned} \text{Exponent} &= E' + 127 \\ &= 5 + 127 \\ \text{Exponent} &= 132 \end{aligned}$$

2	132	0
2	66	0
2	33	1
2	16	0
2	8	0
2	4	0
2	2	0
	1	

(54)₁₀ \longrightarrow (110110)₂
 Normalised form = 1.0110×2^5

Exponent = 10000100
 mantisa = 10110

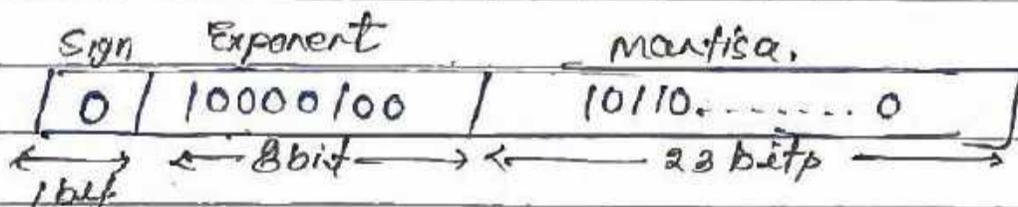


$(35)_{10}$

2	35	1
2	17	8
2	8	0
2	4	0
2	2	0
1		

$(35)_{10} \rightarrow 100011$
 Normalised form = 1.00011×2^5

Exponent = 10000100
 mantissa = 000110

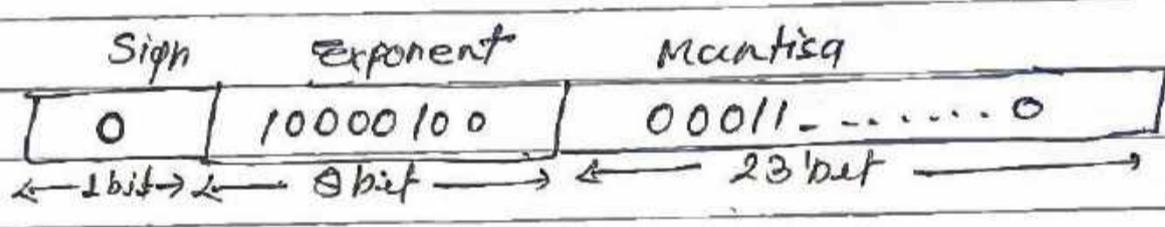

Exponent = $E' + 127$
 $= 5 + 127$
 $= 132$


2	132	0
2	66	0
2	33	1
2	16	0
2	8	0
2	4	0
2	2	0
1		

$(-54)_{10}$

2	54	0
2	27	1
2	13	1
2	6	0
2	3	1
1		

$(54) \rightarrow 110110$
 Normalised form 1.10110×2^5

Exponent = 10000100
 mantissa = 10110

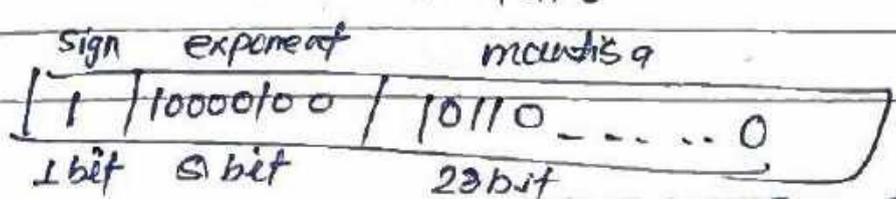

Exponent = $E' + 127$
 $= 5 + 127$
 $= 132$

2	132	0
2	66	0
2	33	1
2	16	0
2	8	0
2	4	0
2	2	0
1		

(94)

2)

$(-234.725)_{10}$

2	234	0
2	117	1
2	58	0
2	29	1
2	14	0
2	7	1
2	3	1
1		

$0.725 \times 2 = 1.450 \Rightarrow 1$

$0.450 \times 2 = 0.90 \Rightarrow 0$

$0.90 \times 2 = 1.8 \Rightarrow 1$

$0.8 \times 2 = 1.6 \Rightarrow 1$

$(-234.725)_{10} \rightarrow (11101010.1101)_2$

Normalised form $\Rightarrow 1.11010101101 \times 2^7$


Exponent = $E' + 127$
= $7 + 127$

Exponent = 134

2	134	0
2	67	1
2	33	1
2	16	0
2	8	0
2	4	0
2	2	0
1		

Exponent = 10000110

Mantissa = 11010101101

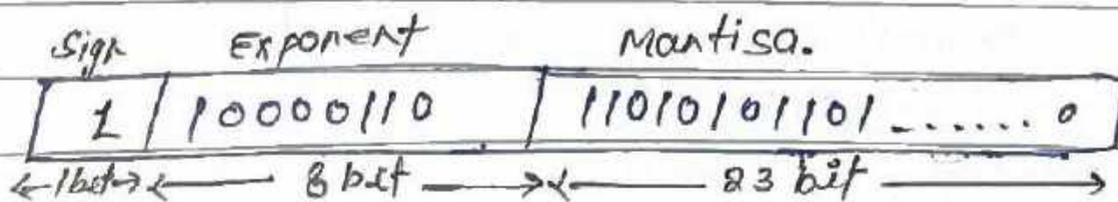

(0.00001101)₂


Normalized Form $\rightarrow 0.10101 \times 2^6$

$$\begin{aligned} \text{Exponent} &= E + 127 \\ &= -6 + 127 \\ &= 121 \end{aligned}$$

2	121	1
2	60	0
2	30	0
2	15	1
2	7	1
2	3	1
1		

Exponent = 1111001

Mantissa = 10101

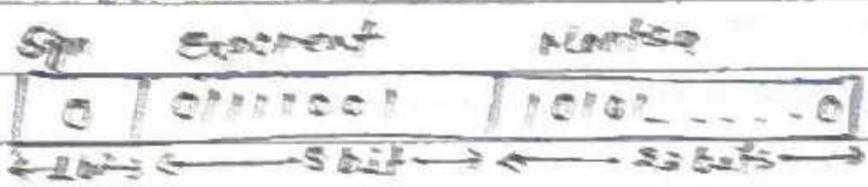

Double Precision

(-250)₁₀

2	250	0
2	125	1
2	62	0
2	31	1
2	15	1
2	7	1
2	3	1
1		


$$\begin{aligned} \text{Exponent} &= E + 1023 \\ &= 7 + 1023 \\ &= 1030 \end{aligned}$$

2	1030	0
2	515	1
2	257	1
2	128	0
2	64	0
2	32	0
2	16	0
2	8	0
2	4	0
2	2	0
1		

(-250)₁₀ \rightarrow (11111010)₂

Normalized Form (1.1111010 $\times 2^7$)

Exponent = 1000000110
Mantissa = 1111010

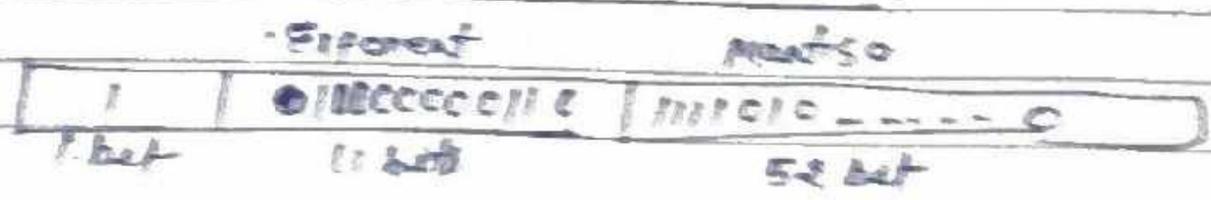


$1.00010100 \times 2^{-10}$

Exponent = $E' + 1023$

= $-10 + 1023$

Exponent = 1013

2	1013	1
2	506	0
2	253	1
2	126	0
2	63	1
2	31	1
2	16	0
2	8	0
2	4	0
2	2	0
1		

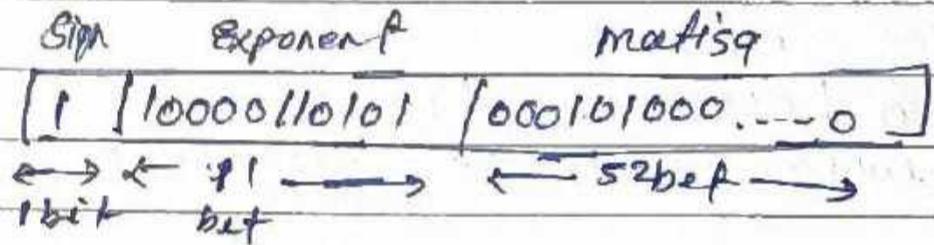

Exponent 10000110101

Mantissa